

## Measuring systems

### Problem set n° 7

#### Exercise 1 (Acquisition and Nyquist sampling theorem)

We would like to acquire and convert the following analog signal:

$$u(t) = A \cdot \cos(2000\pi t) + B \cdot \sin(6000\pi t) + C \cdot \cos(12000\pi t) \quad \text{with } A = 3V, B = 5V, C = 10V.$$

- What is the minimum sampling frequency required for a correct acquisition of the signal?
- If the signal  $u(t)$  is acquired with a sampling rate  $F_s = 5000 \text{ samples/sec}$ , what is the discrete signal  $u(n)$  that will be obtained? [ $t = n \cdot \Delta t_{\text{sampling}}$ ]. What is the corresponding cut-off frequency that the reconstruction filter should have?
- In case we use  $F_s = 5000 \text{ samples/sec}$ , what is the analog signal that we can reconstruct from the samples? Comment on the results.
- (ONLY IN CASE WE HAD TIME TO COVER A/D RESOLUTION DURING THE LECTURES) If we use an A/D converter to digitalize the signal, what is the minimum required full scale range (minimum integer value)? What is the corresponding resolution if the converter has 8 bits?

#### Exercise 2 - OPTIONAL (Extrinsic noise and an asymmetric circuit from the previous chapter)

We would like to amplify and measure the RMS value of the **AC voltage source**  $\underline{U}_s$  with internal resistance  $R_s$  and frequency  $f_s$ . For this, we use an amplifier with internal resistance  $R_i$  and gain  $A$ . Capacitive coupling "cable-ground"  $C_{c-g}$  and "network-cable"  $C_{n-c}$  are influencing the measurement. A voltage is obtained at the output of the amplifier  $\underline{U}_m$ , including parasitics and the signal from the source, which is measured using a voltmeter with internal resistance  $R_i$  (see Figure 1).

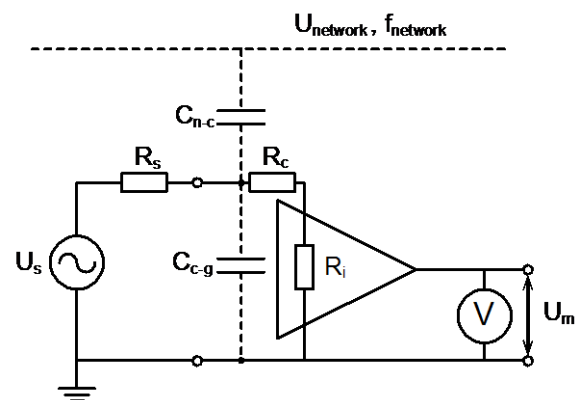


Figure 1: Capacitive coupling for an asymmetric circuit

- Give the expression of the parasitic voltage  $\underline{U}_{m,n}$  measured by the voltmeter, caused by the source and the power line network. Consider that the input of the amplifier is isolated from the output.
- Calculate  $|\underline{U}_{m,n}|$  and SNR in dB at the amplifier output.
- Propose two combined solutions to reduce noise and draw the circuit.

Data:

$$A = 10$$

$$C_{n-c} = 10 \text{ pF}$$

$$C_{c-g} = 1 \text{ pF}$$

$$U_{\text{network}} = 230 \text{ V}$$

$$U_{s,eff} = 1 \text{ V}$$

$$R_i = 10 \text{ M}\Omega$$

$$R_w = 15 \Omega$$

$$R_s = 10 \text{ k}\Omega$$

$$f_{\text{network}} = 50 \text{ Hz}$$

$$f_s = 50 \text{ Hz}$$