

## Problem 1

Consider the logic network defined as:

$$k = ad$$

$$n = c + k$$

$$m = (ab)'$$

$$f = m + n$$

Inputs are  $\{a, b, c, d\}$  and output is  $\{f\}$ . Assume  $CDC_{in} = ab$ . Compute  $CDC_{out}$ .

## Problem 2

Consider the logic network above. Compute the ODC sets for all internal and input vertices assuming that the outputs are fully observable.