

Problem 1


For the following functions:

$$\begin{aligned} F &= acde + acfg + bde + bfg + acd'h + bd'f \\ G &= acde + acf'g + bde + bf'g + aef' + ce h \end{aligned} \tag{1}$$

- (a) Compute all kernels and co-kernels of F and G .
- (b) Extract a multiple-cube sub-expression common to F and G .
- (c) Draw the network graph using the result obtained in (b).

 Problem 2

The smallest number of comparisons to sort 5 numbers is 9. One witness for this bound is the following sorter network:



The sorter network guarantees that $\{y_1, \dots, y_5\} = \{x_1, \dots, x_5\}$ and $y_1 \leq \dots \leq y_5$.

1. Use this sorter network to construct an MIG that computes $\langle x_1x_2x_3x_4x_5 \rangle$.
2. How many majority-3 gates are required in a straightforward construction?

Problem 3

Consider the logic network defined as:

$$\begin{aligned}c &= (a + b)'; & d &= ab'; & e &= (ab)'; & f &= (ae)'; & g &= (be)'; \\o_1 &= c + d; & o_2 &= (fg)'; & h &= o_1 \oplus o_2;\end{aligned}$$

- (a) Draw the logic network graph.
- (b) Write the Tseytin encoding for all gates in the network.
- (c) Write the CNF formula that can be used to check the equivalence of subnetworks o_1 and o_2 .

Problem 4

Consider the logic network defined as:

$$\begin{aligned}k &= a'; & e &= kb; & g &= (bc)'; & f &= (g + e)'; \\h &= a \odot b; & i &= f \oplus d; & j &= d + s; & x &= ei; & y &= (h + j)'\end{aligned}$$

Inputs are $\{a, b, c, d, s\}$ and outputs are $\{x, y\}$.

Assume that NAND, NOR, XOR, XNOR delay is 2 unit and AND, INV, OR delay is 1 unit. The data ready time of signal d is 4 ($t_d = 4$) The data ready time of other signals is 0. The required data time at outputs is 7.

- (a) Draw the logic network graph.
- (b) Determine the data ready time and the slacks for all nodes.
- (c) Find the topological critical paths.
- (d) Are the topological critical paths statically/dinamically sensitizable?

Problem 5

 


Figure 1: Sequential logic network

Consider the sequential logic network $G(V,W,d)$ in Fig. 1. Each vertex represents a combination logic circuit, whose weight corresponds to its logic delay. The weight of each edge corresponds to the number of registers between two vertices.

- Draw the constraint graph modeling to search for a legal retiming with a cycle-time of 17 units.
- Use Bellman-Ford method to find the retiming factor with the constraint graph.
- Compute the retiming vector \mathbf{r} and redraw the retimed network graph.