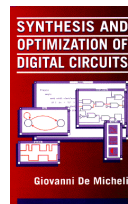


# *Libraries and Mapping*

**Giovanni De Micheli**  
***Integrated Systems Centre***  
***EPF Lausanne***



---

This presentation can be used for non-commercial purposes as long as this note and the copyright footers are not removed

© Giovanni De Micheli – All rights reserved

# Module 1

---

## ◆ Objective

### ▲ Libraries

### ▲ Problem formulation and analysis

### ▲ Algorithms for library binding based on structural methods

# Library binding

---

- ◆ **Given an unbound logic network and a set of library cells**
  - ▲ **Transform into an interconnection of instances of library cells**
  - ▲ **Optimize delay**
    - ▼ (under area or power constraints)
  - ▲ **Optimize area**
    - ▼ Under delay and/or power constraints
  - ▲ **Optimize power**
    - ▼ Under delay and/or area constraints
- ◆ **Library binding is called also technology mapping**
  - ▲ **Redesigning circuits in different technologies**

# Major approaches

---

## ◆ Rule-based systems

- ▲ Generic, handle all types of cells and situations
- ▲ Hard to obtain circuit with specific properties
- ▲ Data base:
  - ▼ Set of pattern pairs
  - ▼ Local search: detect pattern, implement its best realization

## ◆ Heuristic algorithms







- ▲ Typically restricted to single-output combinational cells
- ▲ Library described by cell functionality and parameters

## ◆ Most systems use a combination of both approaches:

- ▲ Rules are used for I/Os, high buffering requirements, ...

# Examples

---

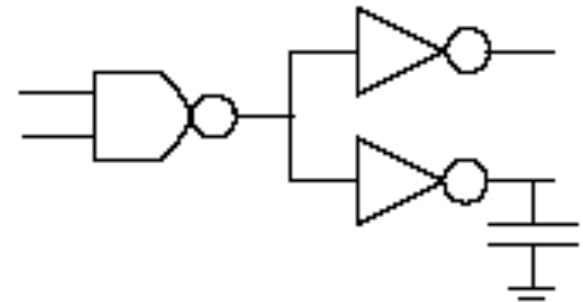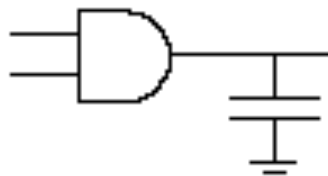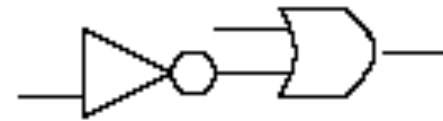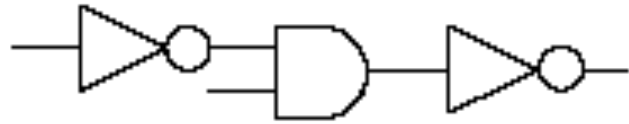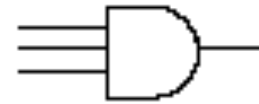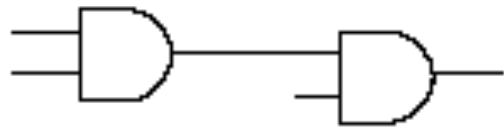

# Library binding: issues

---

## ◆ Matching:

- ▲ A cell matches a sub-network when their terminal behavior is the same
- ▲ Tautology problem
- ▲ *Input-variable* assignment problem

## ◆ Covering:

- ▲ A cover of an unbound network is a partition into sub-networks which can be replaced by library cells.
- ▲ Binate covering problem

# Assumptions

---

- ◆ **Network granularity is fine**

  - ▲ **Decomposition into base functions:**

  - ▲ **2-input AND, OR, NAND, NOR**


- ◆ **Trivial binding**

  - ▲ **Use base cells to realize decomposed network**


  - ▲ **There exists always a trivial binding:**

    - ▼ **Base-cost solution...**


# Example

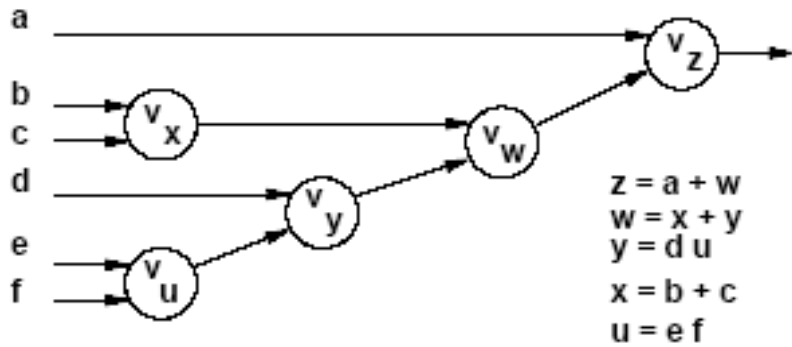


(a)

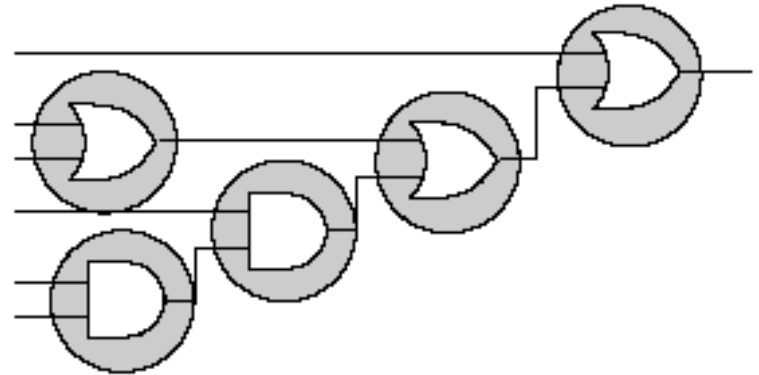

(b)

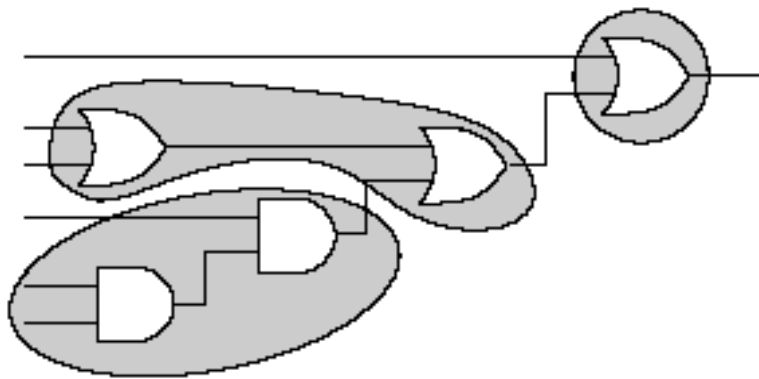

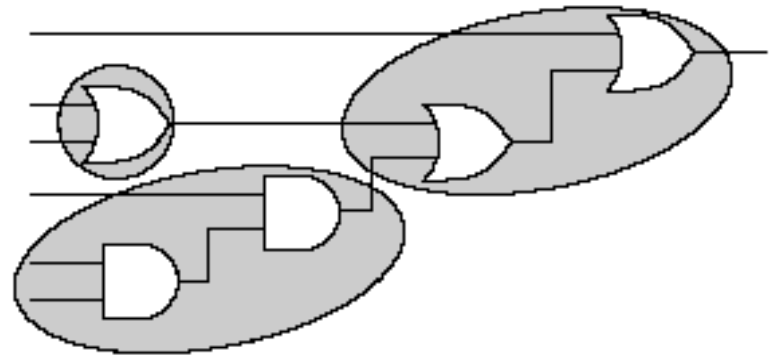


(c)



(d)





# Example

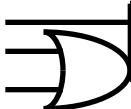Library	Cost
 AND2	4
 OR2	4
 OA21	5

$$x = b + c$$

$$y = ax$$

$$z = xd$$

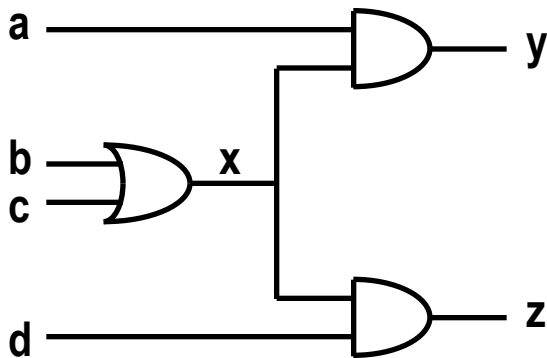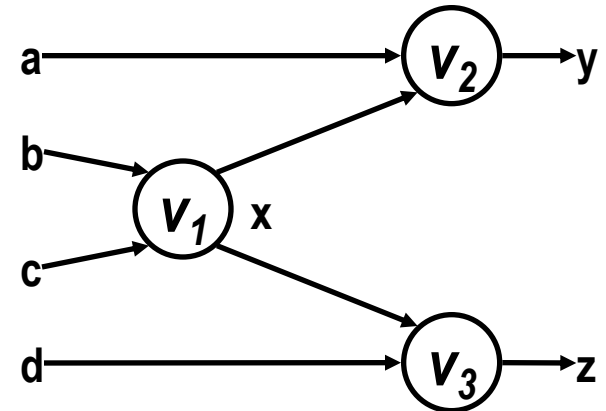


$$m_1: \{v_1, \text{OR2}\}$$

$$m_2: \{v_2, \text{AND2}\}$$

$$m_3: \{v_3, \text{AND2}\}$$

$$m_4: \{v_1, v_2, \text{OA21}\}$$

$$m_5: \{v_1, v_3, \text{OA21}\}$$

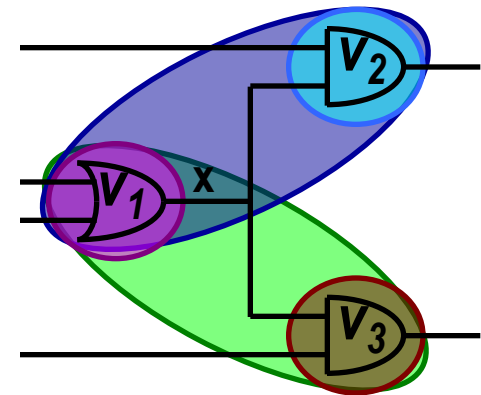

# Example

## ◆ Vertex covering:

▲ Covering  $v_1 : ( m_1 + m_4 + m_5 )$

▲ Covering  $v_2 : ( m_2 + m_4 )$

▲ Covering  $v_3 : ( m_3 + m_5 )$

## ◆ Input compatibility:

▲ Match  $m_2$  requires  $m_1$


▼  $( m'_2 + m_1 )$

▲ Match  $m_3$  requires  $m_1$

▼  $( m'_3 + m_1 )$
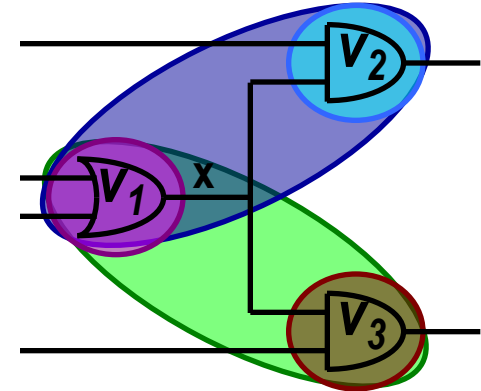
## ◆ Overall binate covering clause

▲  $( m_1 + m_4 + m_5 ) ( m_2 + m_4 ) ( m_3 + m_5 ) ( m'_2 + m_1 ) ( m'_3 + m_1 ) = 1$



# Heuristic approach to library binding

---

## ◆ Split problem into various stages:

### ▲ Decomposition

- ▼ Cast network and library in standard form
- ▼ Decompose into base functions
- ▼ Example, **NAND2** and **INV**

### ▲ Partitioning

- ▼ Break network into cones
- ▼ Reduce to many **multi-input, single-output** networks


### ▲ Covering

- ▼ Cover each sub-network by library cells


## ◆ Most tools use this strategy

### ▲ Sometimes stages are merged


# Decomposition

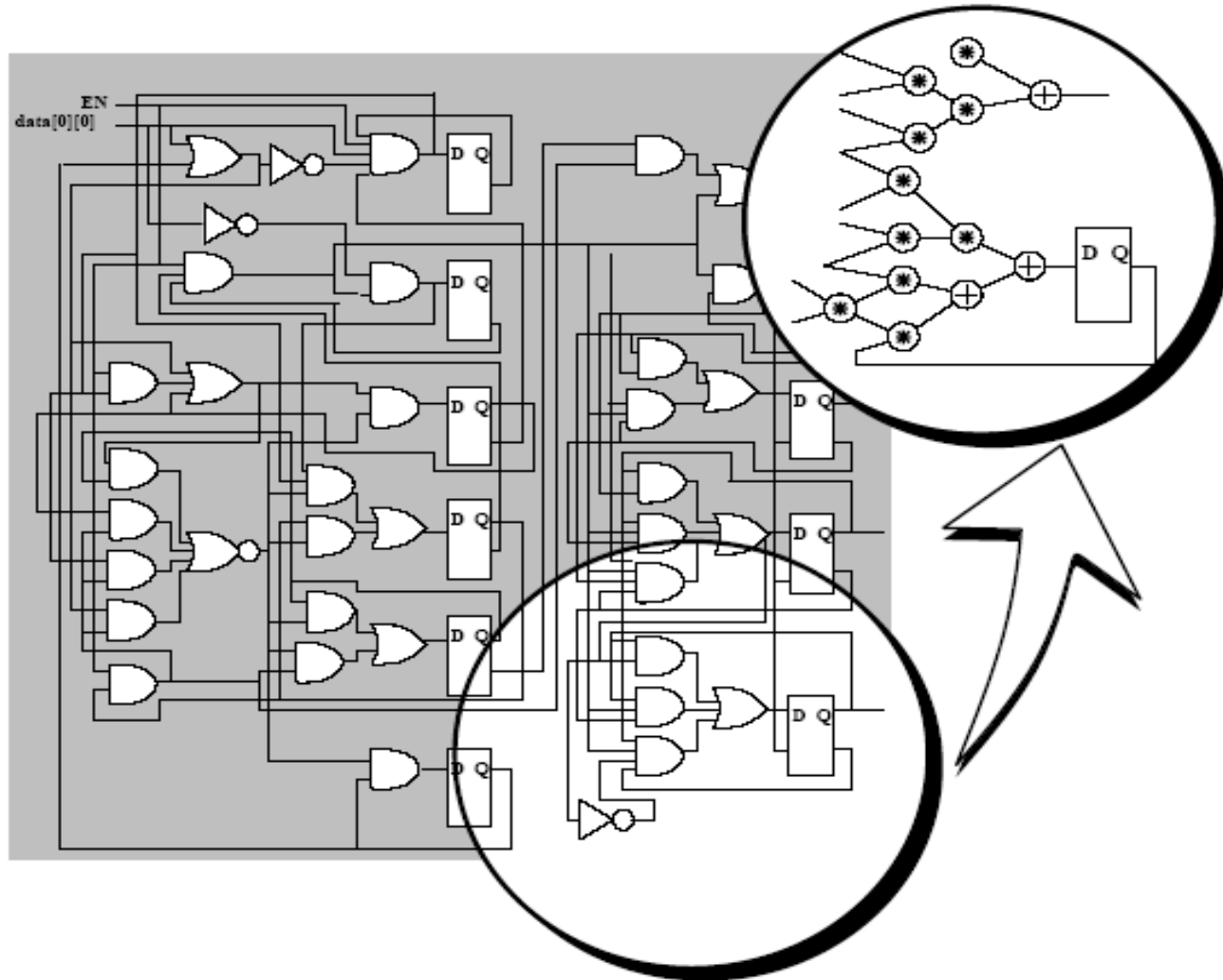

# Partitioning

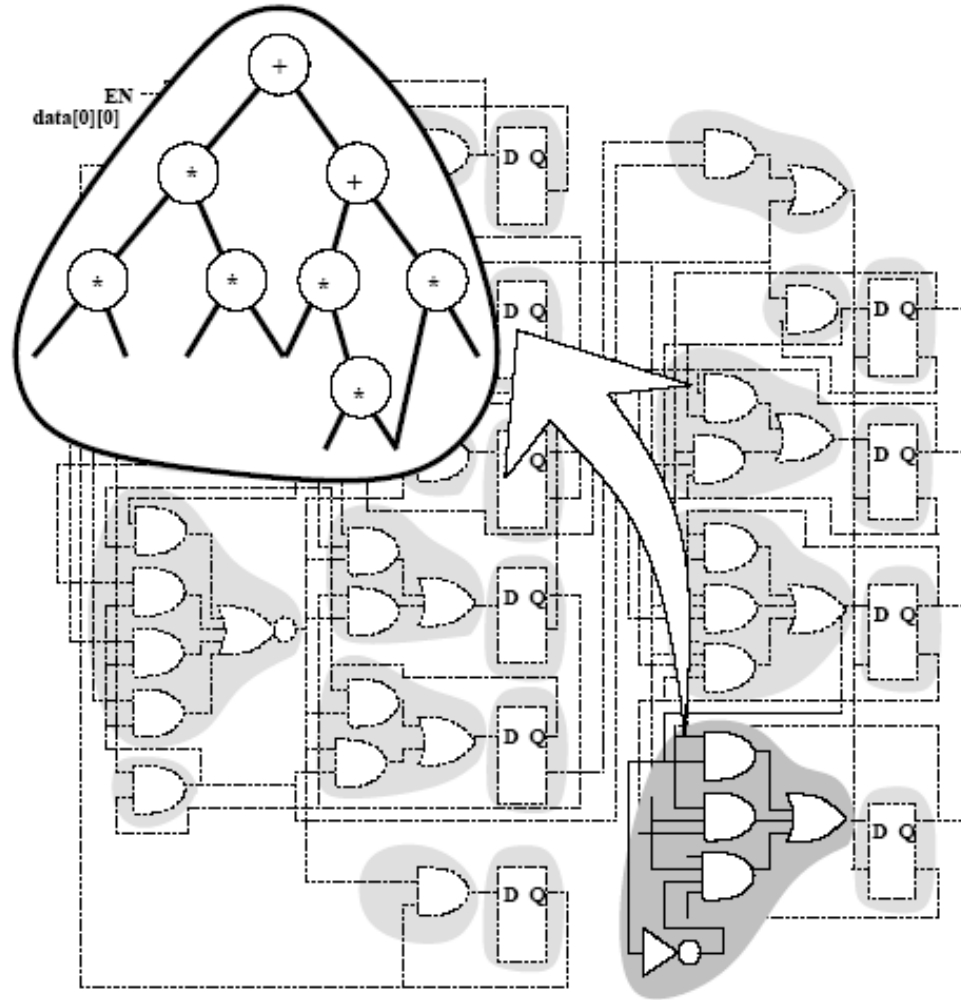

# Covering

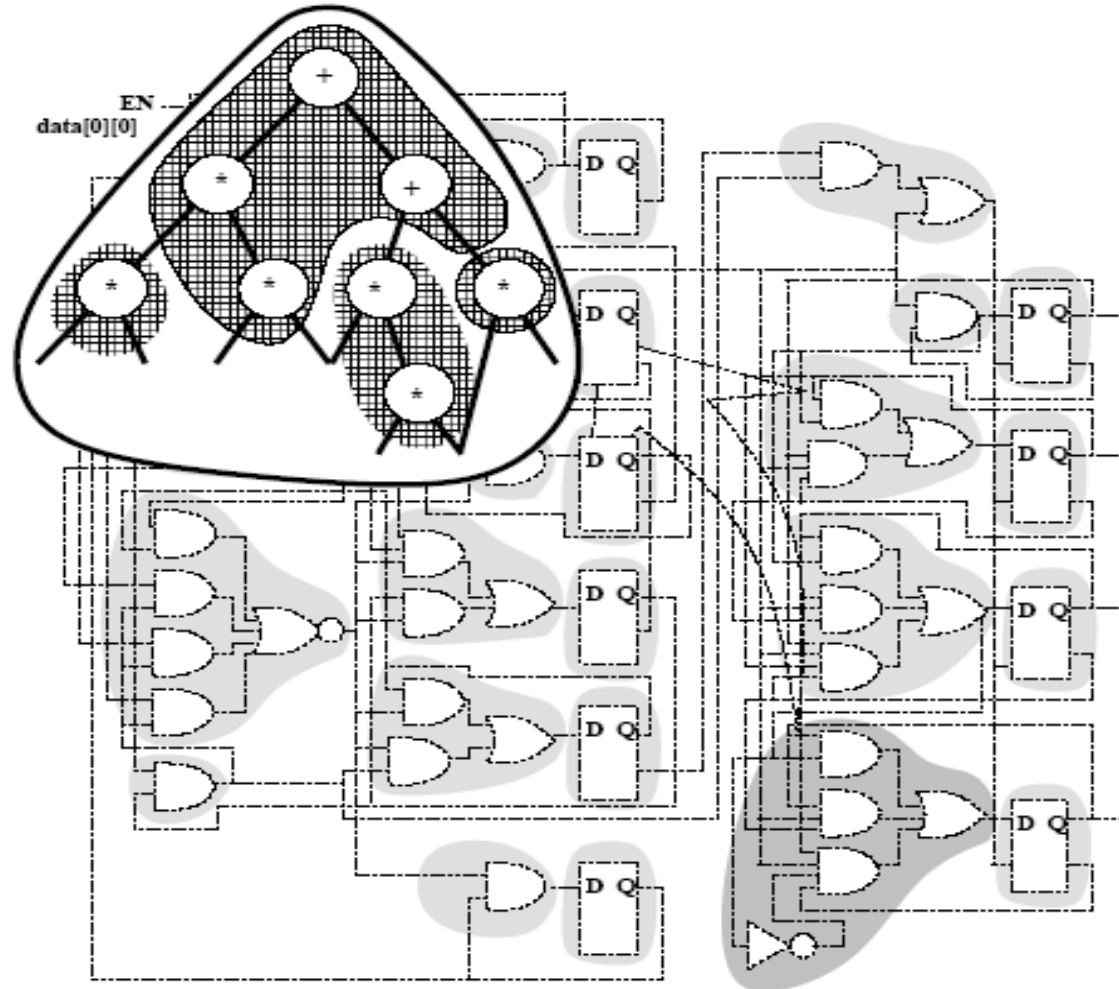

# Heuristic algorithms

---

## ◆ Structural approach

### ▲ Model functions by patterns

▼ Example: tree, dags

### ▲ Rely on pattern matching techniques

## ◆ Boolean approach

### ▲ Use Boolean models

### ▲ Solve the tautology problem

▼ Use BDD technology

### ▲ More powerful

# Example

- ◆ Boolean vs. structural matching

- ◆  $f = xy + x'y' + y'z$



- ◆  $g = xy + x'y' + xz$

- ◆ Function equality is a tautology

  - ▲ Boolean match





- ◆ Patterns may be different

  - ▲ Structural match may not exist

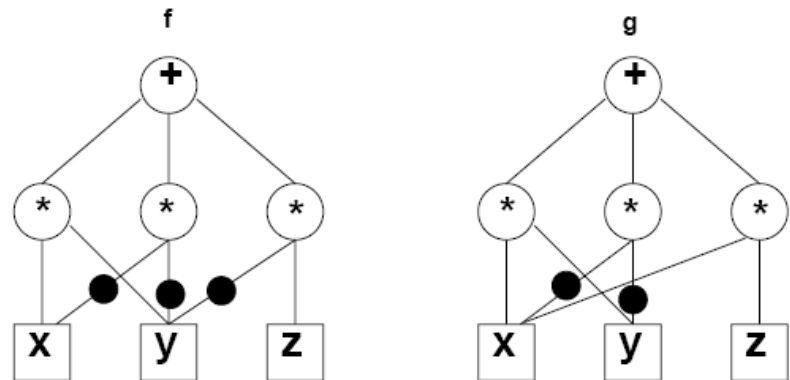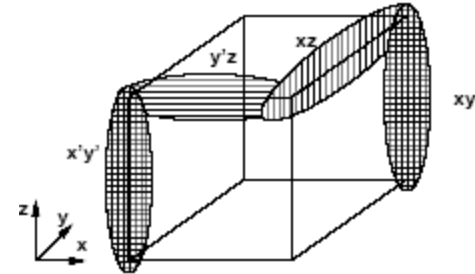




# Example

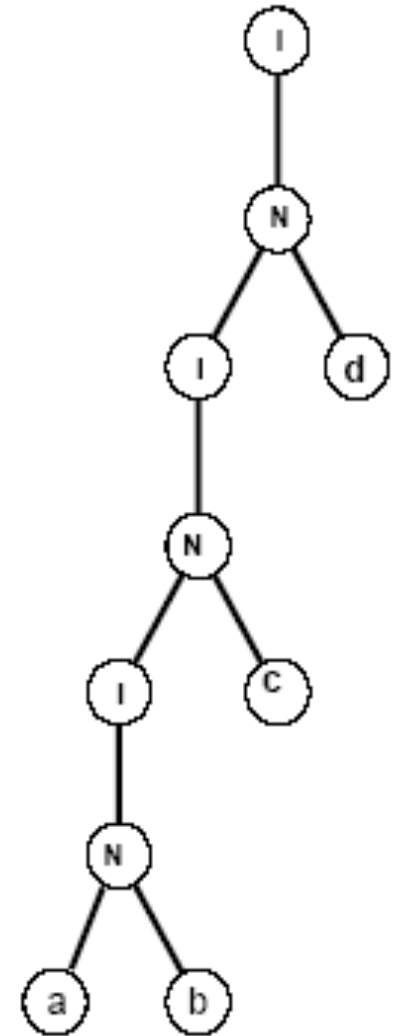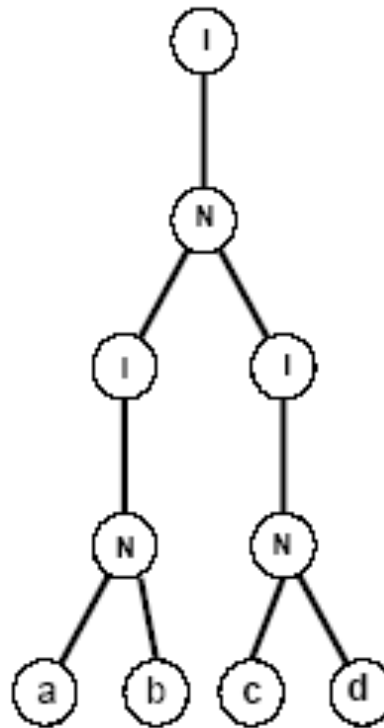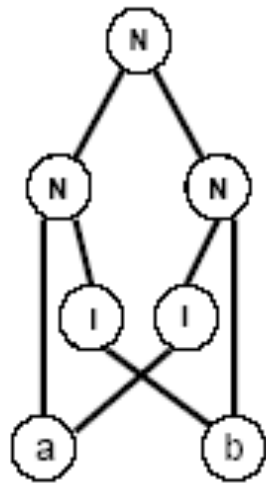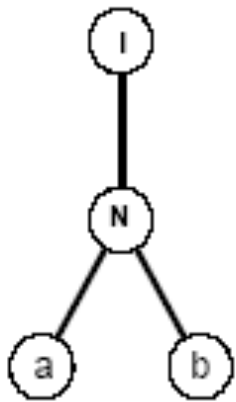

# Example


## SUBJECT TREE

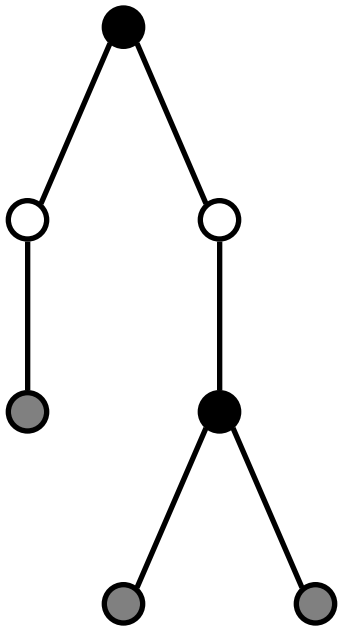


## PATTERN TREES




cost = 2  
INV

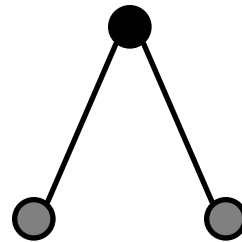

cost = 3  
NAND

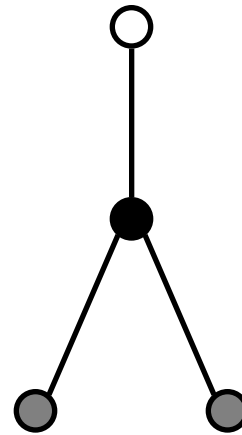


cost = 4  
AND

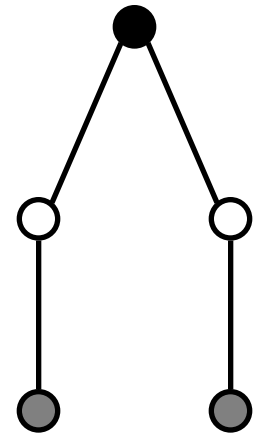

cost = 5  
OR

# Example: Lib

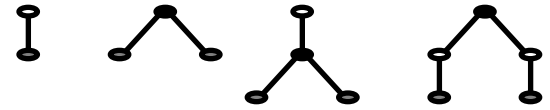

Match of s: t1  
cost = 2






Match of t: t1  
cost = 2+3 = 5

Match of t: t3  
cost = 4

Match of r: t2  
cost = 3+2+4 = 9

Match of r: t4  
cost = 5+3 = 8

Match of u: t2  
cost = 3

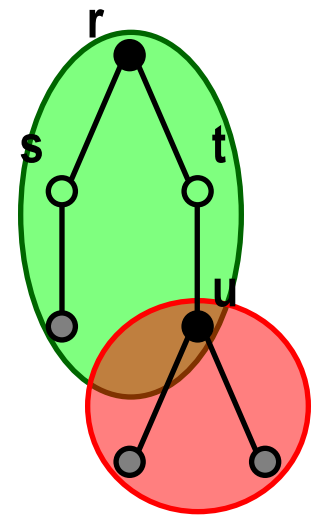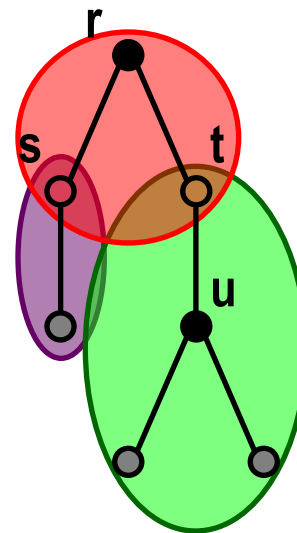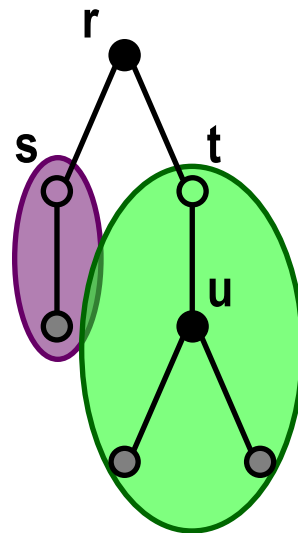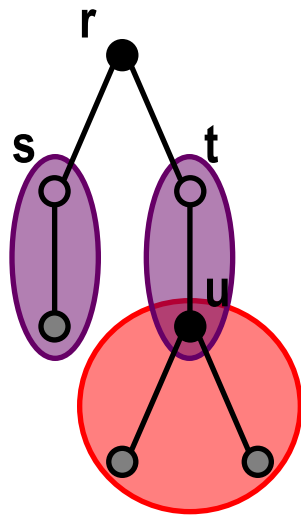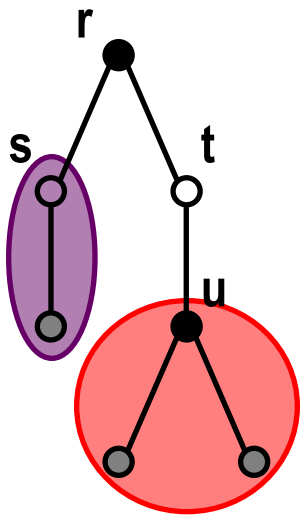

# Tree covering

---

- ◆ **Dynamic programming**

- ▲ Visit subject tree bottom up

- ◆ **At each vertex**

- ▲ **Attempt to match:**

- ▼ Locally rooted subtree to all library cell

- ▼ Find best match and record

- ▲ **There is always a match when the base cells are in the library**

- ◆ **Bottom-up search yields and optimum cover**

- ◆ **Caveat:**

- ▲ Mapping into trees is a distortion for some cells

- ▲ Overall optimality is weakened by the overall strategy of splitting into several stages

# Different covering problems

---

## ◆ Covering for minimum area:

- ▲ Each cell has a fixed area cost (label)

- ▲ Area is additive:

  - ▼ Add area of match to cost of sub-trees

## ◆ Covering for minimum delay:

- ▲ Delay is fanout independent


  - ▼ Delay computed with (max, +) rules

  - ▼ Add delay of match to highest cost of sub-trees

- ▲ Delay is fanout dependent

  - ▼ Look-ahead scheme is required

# Simple library

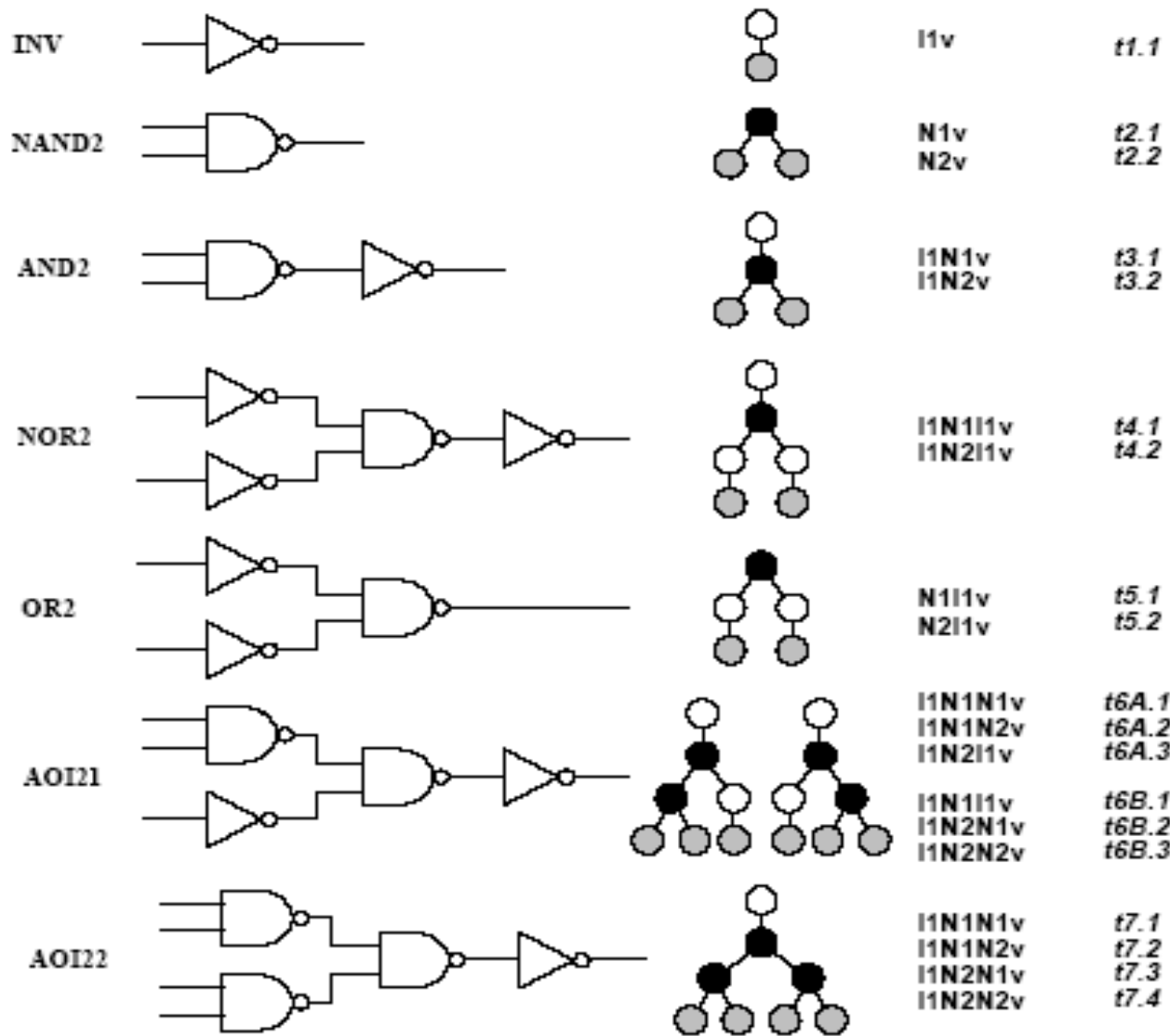

# Example – minimum area cover

◆ Area cost: INV:2 NAND2:3 AND2: 4 AOI21: 6

Network	Subject graph	Vertex	Match	Gate	Cost
		x	t2	NAND2(b,c)	3
		y	t1	INV(a)	2
		z	t2	NAND2(x,d)	3+3 = 6
		w	t2	NAND2(y,z)	3+6+ 2 = 11
		o	t1	INV(w)	2+11 = 13
			t3	AND2(y,z)	6 + 4 + 2 = 12
	t6B	AOI21(x,d,a)	6 + 3 = <b>9</b>		

# Example – minimum delay cover

- ◆ Fixed delays: **INV:2** **NAND2:4** **AND2: 5** **AOI21: 10**
- ◆ All inputs are stable at time 0, except for  $t_d = 6$

Network	Subject graph	Vertex	Match	Gate	Cost
		x	t2	NAND2(b,c)	4
		y	t1	INV(a)	2
		z	t2	NAND2(x,d)	6+4 = 10
		w	t2	NAND2(y,z)	10 + 4 = 14
		o	t1	INV(w)	14 + 2 = 16
			t3	AND2(y,z)	10 + 5 = 15
			t6B	AOI21(x,d,a)	10 + 6 = 16



# Minimum-delay cover for load-dependent delays

---

## ◆ Model

- ▲ Gate delay is  $d = \alpha + \beta \text{ cap\_load}$
- ▲ Capacitive load depends on the driven cells (fanout cone)
- ▲ There is a finite (possibly small) set of capacitive loads

## ◆ Algorithm

- ▲ Visit subject tree bottom up
- ▲ Compute an array of solutions for each possible load
- ▲ For each input to a matching cell, the best match for the corresponding load is selected

## ◆ Optimality

- ▲ Optimum solution when all possible loads are considered
- ▲ Heuristic: group loads into bins

# Example – minimum delay cover

- ◆ Delays: **INV**:1+load    **NAND2**: 3+load    **AND2**: 4+load    **AOI21**: 9+load
- ◆ All inputs are stable at time 0, except for  $t_d = 6$
- ◆ All loads are 1

Same as before !

Network	Subject graph	Vertex	Match	Gate	Cost
		x	t2	NAND2(b,c)	4
		y	t1	INV(a)	2
		z	t2	NAND2(x,d)	6+4 = 10
		w	t2	NAND2(y,z)	10 + 4 = 14
		o	t1	INV(w)	14 + 2 = 16
			t3	AND2(y,z)	10 + 5 = <b>15</b>
			t6B	AOI21(x,d,a)	10 + 6 = 16

# Example – minimum delay cover

---

- ◆ Delays: **INV**: 1+load   **NAND2**: 3+load   **AND2**: 4+load   **AOI21**: 9+load
- ◆ All inputs are stable at time 0, except for  $t_d = 6$
- ◆ All loads are 1 (for cells seen so far)
- ◆ Add new cell **SINV** with delay  $1 + \frac{1}{2} \text{load}$  and load 2
- ◆ The sub-network drives a load of 5

# Example – minimum delay cover

Network	Subject graph	Vertex	Match	Gate	Cost			
					Load=1	Load=2	Load=5	
		x	t2	NAND2(b,c)	4	5	8	
		y	t1	INV(a)	2	3	6	
		z	t2	NAND2(x,d)	10	11	14	
		w	t2	NAND2(y,z)	14	15	18	
		o	t1	INV(w)			20	
			t3	AND2(y,z)			19	
			t6B	AOI21(x,d,a) SINV(w)			20	
								18.5

# Module 2


---

## ◆ Objectives

- ▲ Boolean covering
- ▲ Boolean matching
- ▲ Simultaneous optimization and binding
- ▲ Extensions to Boolean methods
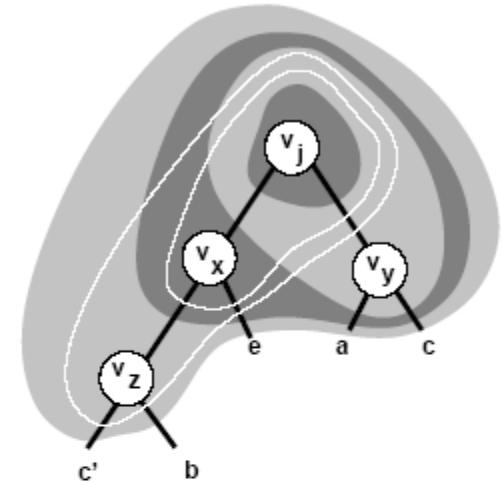
# Boolean covering

- ◆ Decompose network into base functions
- ◆ Partition network into cones
- ◆ Apply bottom-up covering to each cone
  - ▲ When considering vertex  $v$ :
    - ▼ Construct clusters by local elimination
    - ▼ Limit the depth of the cluster by limiting the support of the function
    - ▼ Associate several functions with vertex  $v$
    - ▼ Apply matching and record cost



$$\begin{aligned}f_{j,1} &= xy; \\f_{j,2} &= x(a + c); \\f_{j,3} &= (e + z)y; \\f_{j,4} &= (e + z)(a + c); \\f_{j,5} &= (e + c' + d)y; \\f_{j,6} &= (e + c' + d)(a + c); \end{aligned}$$

# Boolean matching

## $P$ -equivalence

---

### ◆ Cluster function $f(x)$

- ▲ Sub-network behavior

### ◆ Pattern function $g(y)$

- ▲ Cell behavior

### ◆ $P$ -equivalence

- ▲ Is there a permutation operator  $P$ , such that  $f(x) = g(Px)$  is a tautology?

### ◆ Approaches:

- ▲ Tautology check over all input permutations
- ▲ Multi-rooted pattern ROBDD capturing all permutations

# Input/output polarity assignment

---

- ◆ ***NPN*** classification of logic functions

- ◆ ***NPN***-equivalence

- ▲ There exist a permutation operator  $P$  and complementation operators  $N_i$  and  $N_o$ , such that  $f(x) = N_o g ( P N_i x )$  is a tautology

- ◆ **Variations:**

- ▲ ***N***-equivalence

- ▲ ***PN***-equivalence




# Boolean matching

## ◆ Pin assignment problem:


▲ Map cluster variables  $x$  to pattern variables  $y$

▲ Characteristic equation:  $A(x,y) = 1$

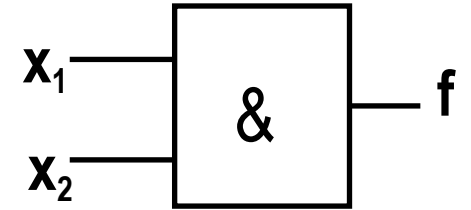

## ◆ Pattern function under variable assignment:

▲  $g_A(x) = S_y ( A(x,y) g(y) )$

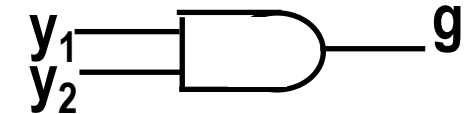

## ◆ Tautology problem

▲  $f(x) = g_A(x)$

▲  $\forall_x f(x) = S_y ( A(x,y) g(y) )$

# Example

◆ Cluster terminals:  $x$  -- cell terminals:  $y$

◆ Assign  $x_1$  to  $y'_2$  and  $x_2$  to  $y_1$

◆ Characteristic equation


$$\blacktriangle A(x_1, x_2, y_1, y_2) = (x_1 \oplus y_2) (x_2 \oplus \bar{y}_1)$$

◆ AND pattern function

$$\blacktriangle g = y_1 y_2$$

◆ Pattern function under assignment
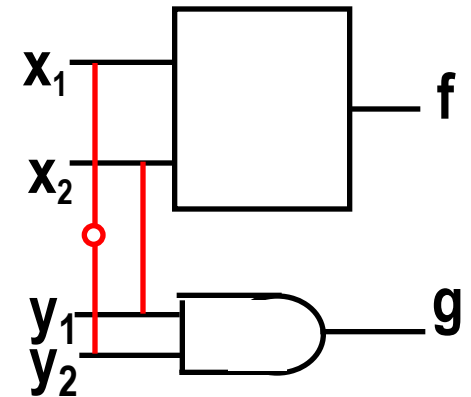
$$\blacktriangle S_{y_1 y_2} A g = S_{y_1 y_2} ((x_1 \oplus y_2) (x_2 \oplus \bar{y}_1) y_1 y_2) = x_2 x'_1$$



# Signatures and filters

---

- ◆ Capture some properties of Boolean functions
- ◆ If signatures do not match, there is no match
- ◆ Signatures are used as filters to reduce computation
- ◆ Signatures:
  - ▲ Unateness
  - ▲ Symmetries
  - ▲ Co-factor sizes
  - ▲ Spectra

# Filters based on unateness and symmetries

---

- ◆ Any pin assignment must associate:
  - ▲ Unate variables in  $f(x)$  with unate variables in  $g(y)$
  - ▲ Binate variables in  $f(x)$  with binate variables in  $g(y)$
- ◆ Variables or group of variables:
  - ▲ That are interchangeable in  $f(x)$  must be interchangeable in  $g(y)$

# Example

---

## ◆ Cluster function: $f = abc$

▲ Symmetries  $\{ \{ a,b,c \} \}$

▲ Unate

## ◆ Pattern functions

▲  $g_1 = a + b + c$

▼ Symmetries  $\{ \{ a,b,c \} \}$

▼ Unate

▲  $g_2 = ab + c$

▼ Symmetries  $\{ \{ a,b \}, \{ c \} \}$

▼ Unate

▲  $g_3 = abc' + a' b' c$

▼ Symmetries  $\{ \{ a,b,c \} \}$

▼ Binate

# Concurrent optimization and library binding

---


## ◆ Motivation

- ▲ Logic simplification is usually done prior to binding
- ▲ Logic simplification and substitution can be combined with binding

## ◆ Mechanism

- ▲ Binding induces some *don't care* conditions
- ▲ Exploit *don't cares* as degrees of freedom in matching

# Example

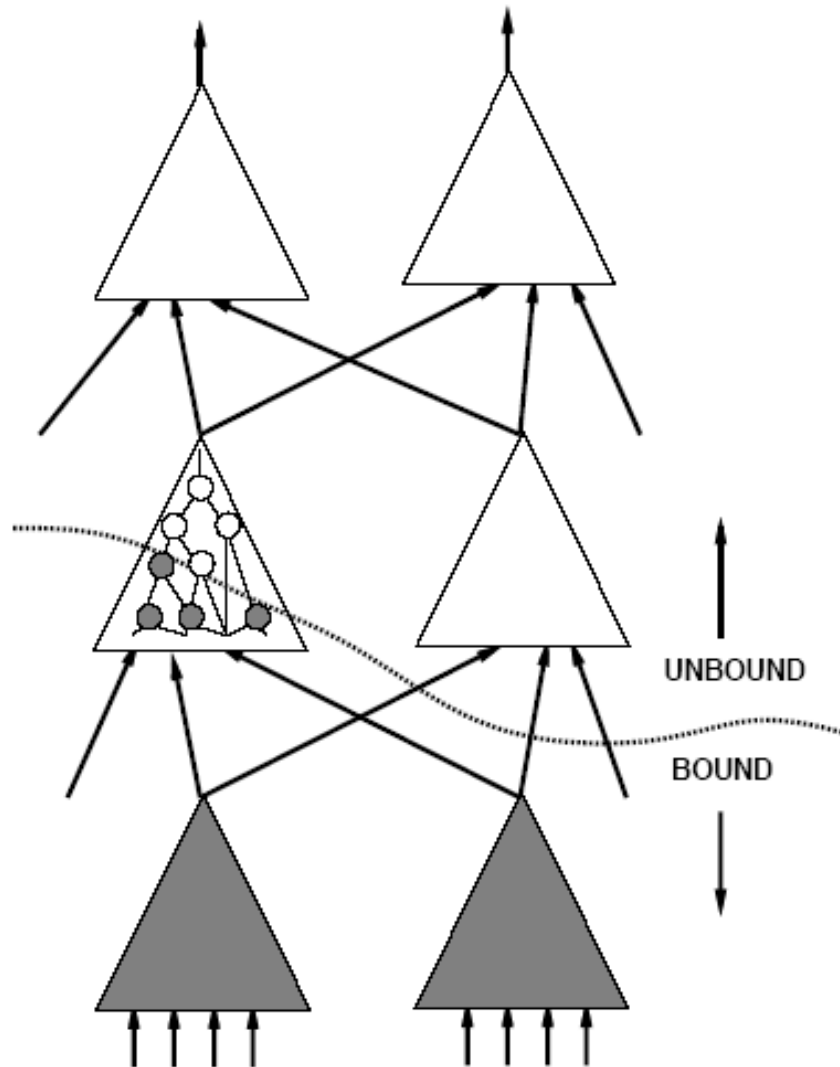

# Boolean matching with *don't care* conditions

---

◆ Given  $f(x)$ ,  $f_{DC}(x)$  and  $g(y)$

▲  $g$  matches  $f$ , if  $g$  is equivalent to  $h$ , where:

$$f \cdot f'_{DC} \leq h \leq f + f_{DC}$$



◆ Matching condition:

$$\forall_x ( f_{DC}(x) + f(x) \oplus \bigoplus_y ( A(x,y) g(y) ) )$$




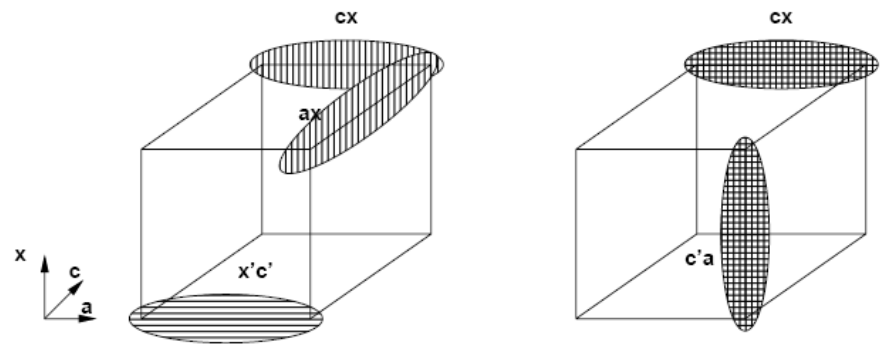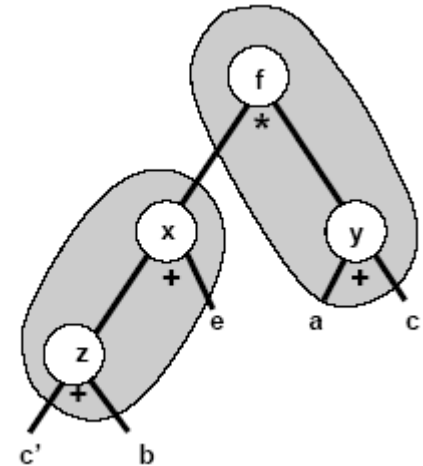
# Example

- ◆ Assume  $v_x$  is bound to an  $OR3(c', b, e)$
- ◆ Don't care set includes  $x \oplus (c' + b + e)$
- ◆ Consider  $f_j = x(a+c)$  with  $CDC = x'c'$
- ◆ No simplification.
  - ▲ Mapping into  $AOI$  gate.
- ◆ Matching with DCs.
  - ▲ Map to a  $MUX$  gate.



# Example

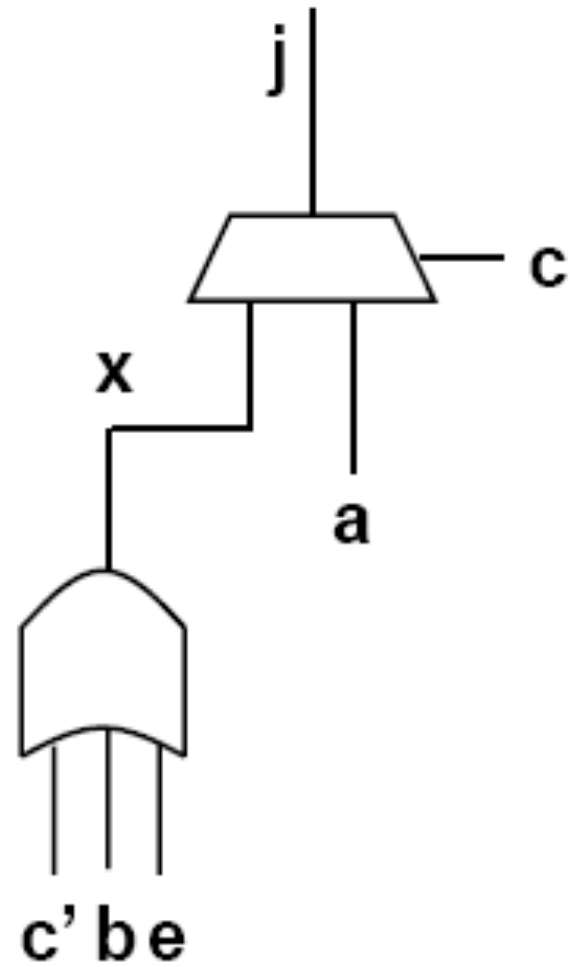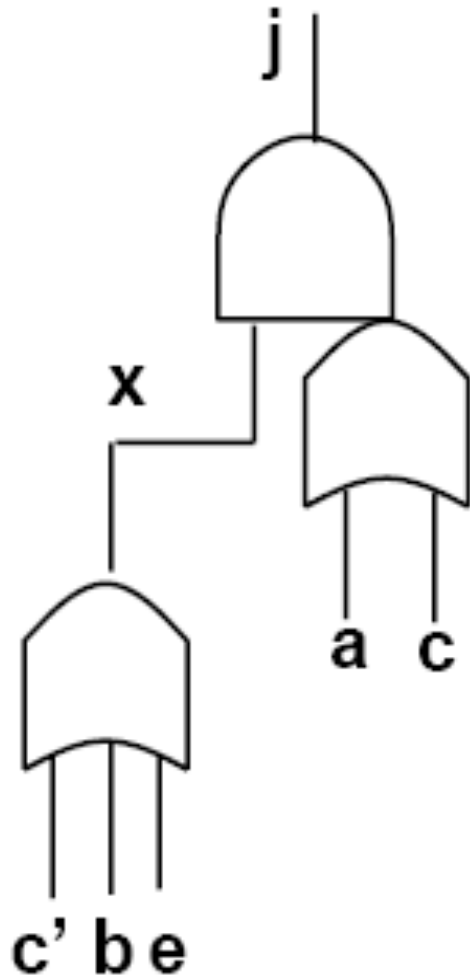

# Extended matching

---

## ◆ Motivation:

- ▲ Search implicitly for best pin assignment
- ▲ Make a single test, determining matching and assignment

## ◆ Technique:

- ▲ Construct BDD model of cell and assignments

## ◆ Visual intuition:

- ▲ Imagine to place **MUX** function at cell inputs
- ▲ Each cell input can be routed to any cluster input (or voltage rail)
- ▲ Input polarity can be changed:
  - ▼ NP-equivalence (extensible to NPN)
- ▲ Cell and cluster may differ in size

## ◆ Cell and multiplexers are described by a composite function **$G(x,c)$**

- ▲ Pin assignment is determining  **$c$**



# Example

◆  $g = y_1 + y_2 y_3'$

◆  $y_1(c,x) = (c_0 c_1 x_1 + c_0 c_1' x_2 + c_0' c_1 x_3) \oplus c_2$

◆  $G = y_1(c,x) + y_2(c,x) y_3(c,x)'$

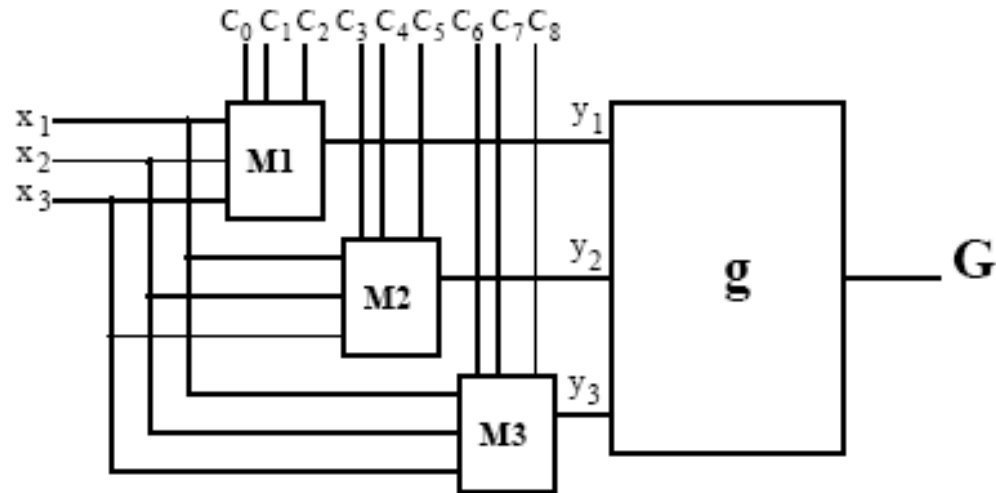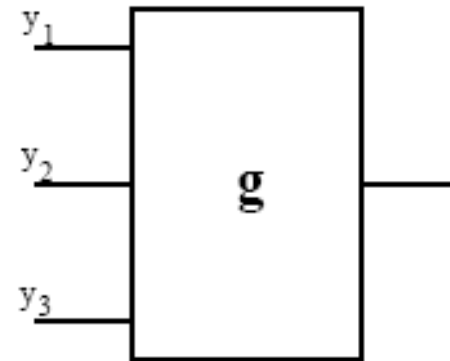◆ An EXOR gate can be placed at the gate output to support NPN-equivalence check



# Extended matching modeling

---

## ◆ Model composite functions with ROBDDs

▲ Assume  $n$ -input cluster and  $m$ -input cell

▲ For each cell input:

▼  $\lceil \log_2 n \rceil$  variables for pin permutation

▼ One variable for input polarity

▲ Total size of  $\mathbf{c}$ :  $m(\lceil \log_2 n \rceil + 1)$

▲ One additional variable for output polarity

◆ A match exists if there is at least one value of  $\mathbf{c}$  satisfying

$$M(\mathbf{c}) = \forall_x [ G(\mathbf{x}, \mathbf{c}) \oplus f(\mathbf{x}) ]$$

# Example



◆ Cell:  $g = x' y$

◆ Cluster:  $f = wz'$

◆  $G(a,b,c,d) = (c \oplus (za + wa'))' (d \oplus (zb + wb'))$

◆  $F \oplus G = (wz) \oplus (c \oplus (za + wa'))' (d \oplus (zb + wb'))$

◆  $M(c) = ab'c'd' + a'bcd$

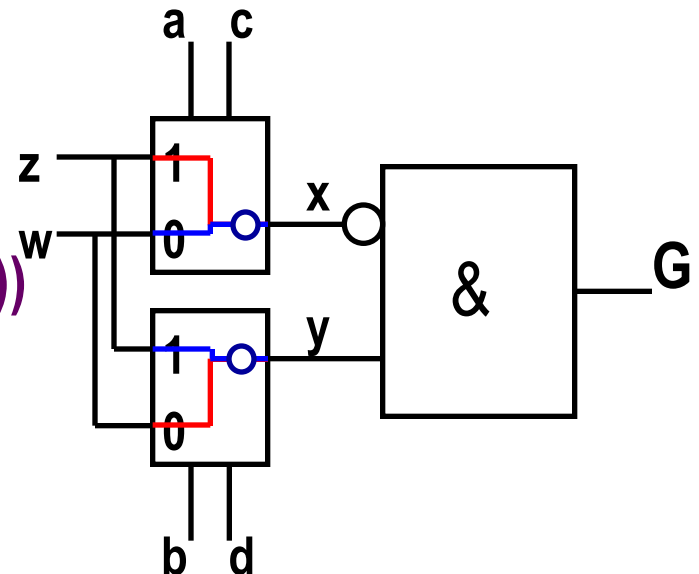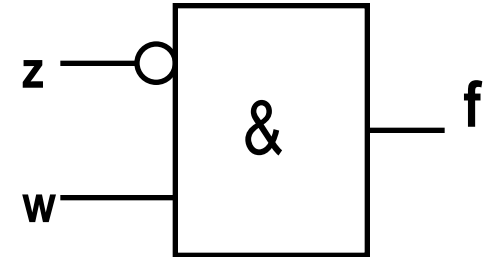


# Extended matching

---

- ◆ Extended matching captures implicitly all possible matches
- ◆ No extra burden when exploiting *don't care* sets
- ◆  $M(c) = \forall_x [ G(x,c) \oplus f(x) + f_{DC}(x) ]$
- ◆ Efficient BDD representation
- ◆ Extensions:
  - ▲ Support multiple-output matching
  - ▲ Full library representation
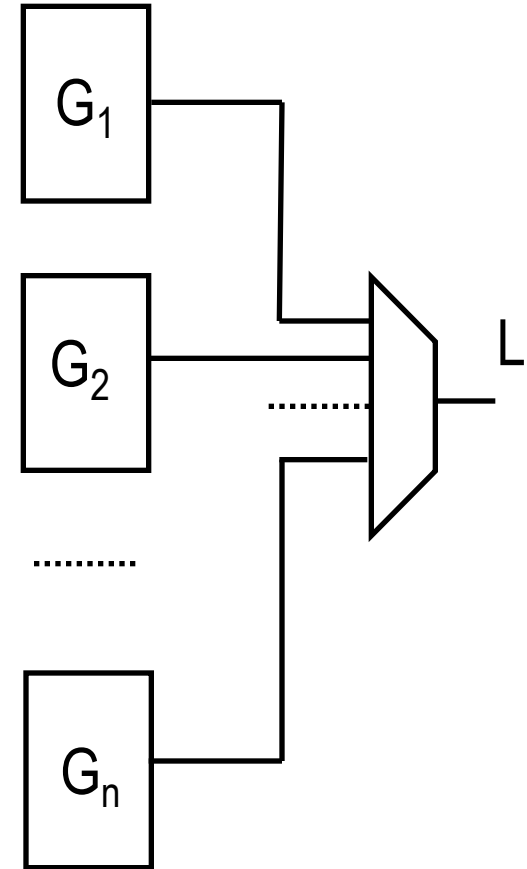
# Full library model

- ◆ Represent full library with  $L(x,c)$ 
  - ▲ One single (large) BDD
- ◆ Visual intuition
  - ▲ All composite cells connected to a MUX
- ◆ Compare cluster to library  $L(x,c)$ 
  - ▲  $M(c) = \forall_x [ L(x,c) \oplus f(x) + f_{DC}(x) ]$
  - ▲ Vector  $c$  determines:
    - ▼ Feasible cell matches
    - ▼ Feasible pin assignments
    - ▼ Feasible output polarity





# Summary

---

- ◆ **Library binding is a key step in synthesis**
- ◆ **Most systems use some rules together with heuristic algorithms that concentrate on combinational logic**
  - ▲ **Best results are obtained with Boolean matching**
  - ▲ **Sometimes structural matching is used for speed**
- ◆ **Library binding is tightly linked to buffering and to physical design**