

# Low-power radio design for the IoT

## Exercise 3 (18.03.2021)

Christian Enz

Swiss Federal Institute of Technology (EPFL), Lausanne, Switzerland

### Problem 1 Nonlinearity and Time Variance

A list of input-output equations for several systems are given below. The instantaneous input is  $x(t)$  and the instantaneous output is  $y(t)$ .

- a)  $2y(t) = 5x(t) + 7$
- b)  $2y(t) = 5x^2(t) + x(t)$
- c)  $2t y(t) = 5x(t) + 7$
- d)  $\frac{dy(t)}{dt} + 2y(t) = 3x(t)$
- e)  $\frac{d^2y(t)}{dt^2} + 3y(t)\frac{dy(t)}{dt} = 5x(t)$

- Classify each system as time invariant or time variant, linear or nonlinear and with memory or memoryless.

### Problem 2 Third-Order Input Intercept Point

Consider the scenario shown in Fig. 1, where  $\omega_3 - \omega_2 = \omega_2 - \omega_1$  and the band-pass filter (BPF) provides an attenuation of 17 dB at  $\omega_2$  and 37 dB at  $\omega_3$ .

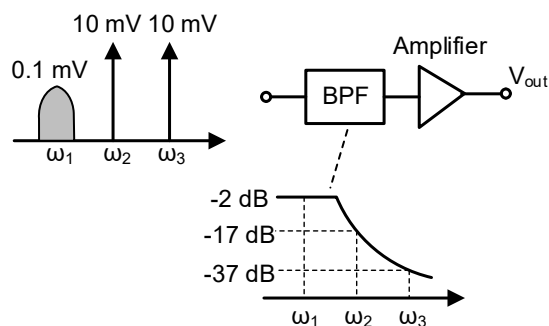


Figure 1: Cascade of BPF and amplifier.

- Compute the  $A_{IIP3}$  of the amplifier such that the intermodulation product falling at  $\omega_1$  is 20 dB below the desired signal.
- Suppose an amplifier with a voltage gain of 10 dB and  $A_{IIP3} = 3.979$  dBm precedes the band-pass filter. Calculate the  $A_{IIP3}$  of the overall chain (neglect the second order nonlinearities and the nonlinearity of the BPF).

### Problem 3 Cascade of Nonlinear Stages

The circuit in Fig. 2 is a cascade of two identical common-source stages loaded by a resistor,  $R_D$ .

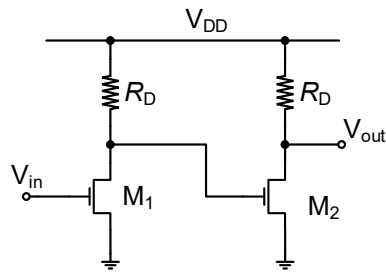


Figure 2: Cascade of common source stages.

- Assume that each transistor operates in saturation and SI and determine the  $A_{IIP3}$  of the cascade.

## Solutions to Exercise 3 (18.03.2021)

### Problem 1 Nonlinearity and Time Variance

- Classify each system as time invariant or time variant, linear or nonlinear and memoryless.

- a)  $2y(t) = 5x(t) + 7$ : time invariant, nonlinear and memoryless  
 b)  $2y(t) = 5x^2(t) + x(t)$ : time invariant, nonlinear and memoryless  
 c)  $2ty(t) = 5x(t) + 7$ : time variant, nonlinear and memoryless  
 d)  $\frac{dy(t)}{dt} + 2y(t) = 3x(t)$ : time invariant, linear and with memory  
 e)  $\frac{d^2y(t)}{dt^2} + 3y(t)\frac{dy(t)}{dt} = 5x(t)$ : time invariant, non linear and with memory

### Problem 2 Third-Order Input Intercept Point

- Compute the  $A_{IIP3}$  of the amplifier such that the intermodulation product falling at  $\omega_1$  is 20 dB below the desired signal.

At the output of the BPF we have

$$\begin{aligned} -2 \text{ dB} &= 10^{-0.1} = 0.794 \rightarrow A_{sig} = 0.1 \text{ mV} \cdot 0.7943 = 79.43 \text{ } \mu\text{V} \\ -17 \text{ dB} &= 10^{-0.85} = 0.1413 \rightarrow A_2 = 10 \text{ mV} \cdot 0.1413 = 1.413 \text{ mV} \\ -37 \text{ dB} &= 10^{-1.85} = 0.0141 \rightarrow A_3 = 10 \text{ mV} \cdot 0.0141 = 0.141 \text{ mV} \end{aligned} \quad (1)$$

At the output of the amplifier, the problem imposes to have the following condition

$$\begin{aligned} 20 \log |\alpha_1 \cdot A_{sig}| - 20 \text{ dB} &= 20 \log \left| \frac{3}{4} \alpha_3 \cdot A_2^2 A_3 \right| \\ \rightarrow |\alpha_1 \cdot 79.43 \text{ } \mu\text{V}| &= \left| \frac{30}{4} \alpha_3 \cdot (1.413 \text{ mV})^2 \cdot 0.141 \text{ mV} \right| \end{aligned} \quad (2)$$

From the latter, we can compute the  $A_{IIP3}$  as

$$A_{IIP3} = \sqrt{\frac{4 |\alpha_1|}{3 |\alpha_3|}} = \sqrt{\frac{4}{3} \cdot \frac{30}{4} \cdot \frac{(1.413 \text{ mV})^2 \cdot 0.141 \text{ mV}}{79.43 \text{ } \mu\text{V}}} = 5.95 \text{ mV} = 10 \log \left( \frac{(5.95 \text{ mV})^2}{1 \text{ mV}} \right) = -34.5 \text{ dBm}, \quad (3)$$

- Suppose an amplifier with a voltage gain of 10 dB and  $A_{IIP3} = 500 \text{ mV}$  precedes the band-pass filter. Calculate the  $A_{IIP3}$  of the overall chain (neglect the second order nonlinearities and the nonlinearity of the BPF).

Only considering the first and third order terms, the output of the first amplifier,  $y_1(t)$ , can be written as

$$y_1(t) = \alpha_1 x(t) + \alpha_3 x^3(t). \quad (4)$$

In the same way, the output of the second amplifier,  $y_2(t)$ , can be written as

$$y_2(t) = \beta_1 y_1(t) + \beta_3 y_1^3(t). \quad (5)$$

If we replace Equation (4) into Equation (5), we then obtain

$$y_2(t) = \beta_1 (\alpha_1 x(t) + \alpha_3 x^3(t)) + \beta_3 (\alpha_1 x(t) + \alpha_3 x^3(t))^3(t). \quad (6)$$

If we limit the expression for  $y_2(t)$  to the first and third order terms we have

$$y_2(t) = \alpha_1 \beta_1 x(t) + (\alpha_3 \beta_1 + \alpha_1^3 \beta_3) x^3(t). \quad (7)$$

As seen in the slides, this leads to the following formula for the cascaded stages

$$\frac{1}{IIP3_{tot}^2} \approx \frac{1}{IIP3_1^2} + \frac{\alpha_1^2}{IIP3_2^2} \quad (8)$$

Once evaluated the latter results into

$$\frac{1}{IIP3_{tot}^2} \approx \frac{1}{(500 \text{ mV})^2} + \frac{10}{(5.95 \text{ mV})^2} \rightarrow IIP3_{tot}^2 = 1.881 \text{ mV} \quad (9)$$

### Problem 3 Cascade of Nonlinear Stages

- Assume that each transistor operates in saturation and SI and determine the  $A_{IIP3}$  of the cascade.

For the MOS transistor biased in saturation and SI we have

$$I_D = \frac{\beta}{2n} \cdot (V_G - V_{T0} - n \cdot V_S)^2, \quad (10)$$

where  $V_S$  is equal to zero, since the source of both transistors is connected to the bulk and to the ground. Then, by analyzing the circuit we obtain

$$V_{out} = V_{DD} - R_D \cdot \frac{\beta}{2n} \cdot (V_x - V_{T0})^2 \quad (11)$$

and

$$V_x = V_{DD} - R_D \cdot \frac{\beta}{2n} \cdot (V_{in} - V_{T0})^2 \quad (12)$$

where  $V_x$  is the voltage at the gate of  $M_2$  and at the drain of  $M_1$ . By replacing Equation (12) into Equation (11), we obtain

$$V_{out} = V_{DD} - R_D \cdot \frac{\beta}{2n} \cdot \left[ V_{DD} - R_D \cdot \frac{\beta}{2n} \cdot (V_{in} - V_{T0})^2 - V_{T0} \right]^2. \quad (13)$$

After some manipulations, this expression results into

$$V_{out} = V_{DD} - R_D \cdot \frac{\beta}{2n} \cdot \left[ (V_{DD} - V_{T0})^2 + R_D^2 \cdot \left( \frac{\beta}{2n} \right)^2 \cdot (V_{in} - V_{T0})^4 - 2R_D \cdot \left( \frac{\beta}{2n} \right) \cdot (V_{DD} - V_{T0}) \cdot (V_{in} - V_{T0})^2 \right]. \quad (14)$$

From Equation (14) is possible to extract the first order terms of  $V_{in}$ , leading to

$$\left[ 4(V_{DD} - V_{T0}) \cdot \left( \frac{\beta}{2n} \right) R_D V_{T0} - 4 \left( \frac{\beta}{2n} \right)^2 R_D^2 V_{T0}^3 \right] \cdot V_{in}. \quad (15)$$

On the other hand, the third order term of  $V_{in}$  is equal to

$$\left[ -4 \left( \frac{\beta}{2n} \right)^2 R_D^2 V_{T0} \right] \cdot V_{in}^3. \quad (16)$$

Finally, the  $A_{IIP3}$  can be expressed as

$$A_{IIP3} = \sqrt{\frac{4 |\alpha_1|}{3 |\alpha_3|}} = \sqrt{\frac{4}{3} \cdot \frac{4(V_{DD} - V_{T0}) \cdot \left( \frac{\beta}{2n} \right) R_D V_{T0} - 4 \left( \frac{\beta}{2n} \right)^2 R_D^2 V_{T0}^3}{4 \left( \frac{\beta}{2n} \right)^2 R_D^2 V_{T0}}}. \quad (17)$$