

Low-power radio design for the IoT

Exercise 5 (25.03.2021)

Christian Enz

Swiss Federal Institute of Technology (EPFL), Lausanne, Switzerland

Problem 1 Common Source Analysis

The circuit in the Figure below is a single MOSFET Common Source (CS) Amplifier.

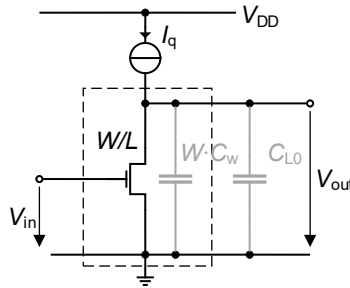


Figure 1: Common Source Amplifier.

- Draw the small-signal equivalent circuit of the CS. Consider the bias current source to be ideal. (*Hint*: split the gate capacitance, C_G , into the intrinsic and the extrinsic parts, C_{Gi} and C_{Ge} , and the load capacitance, C_L , into a constant capacitance and a self-loading capacitance per unit width, C_{L0} and C_w , respectively).
- Derive the expression of the transit frequency, ω_t , by using the small signal equivalent circuit.
- Express ω_t in terms of the inversion coefficient, IC . (*Hint*: introduce the specific frequency, $\omega_{spec} \triangleq \frac{2\mu U_T}{L^2}$, and neglect the velocity saturation ($\lambda_c = 0$)).
- Derive ω_{tspec} , the transit frequency for $IC = 1$ and WI.
- Derive the expression for the unity-gain frequency, ω_u . (*Hint*: neglect the output conductance of the transistor ($g_{ds} = 0$)).
- Express ω_u in terms of the normalized gain-bandwidth (GBW) for a squared transistor biased in WI, $\omega_L \triangleq \frac{I_{spec\Box}}{nU_T C_L}$, and the normalized source transconductance, g_{ms} .

Problem 2 Common Source Design

Once the self loading capacitance per unit width is taken into account, the formulas for the I_D and W/L normalized to $\Omega \triangleq \frac{\omega_u}{\omega_L}$ are

$$\begin{aligned}
 i_b &\triangleq \frac{I_D}{I_{spec\Box}} \cdot \frac{1}{\Omega} = \frac{IC}{g_{ms} - \Theta}; \\
 AR &\triangleq \frac{W}{L} \cdot \frac{1}{\Omega} = \frac{1}{g_{ms} - \Theta},
 \end{aligned} \tag{1}$$

where Θ is equal to $\frac{C_w L}{C_{L0}} \cdot \frac{\omega_u}{\omega_L} = \frac{\omega_u}{\omega_{tspec}}$. Design the CS amplifier, shown in Fig. 1, for the following specifications at room temperature:

$$f_u = 18 \text{ MHz} \quad C_{L0} = 60 \text{ fF} \quad V_{DD} = 1.8 \text{ V} \quad L = 40 \text{ nm} \quad C_w = 0.450 \text{ fF/nm}, \quad (2)$$

and by assuming the following values for the technology parameters

$$I_{spec\Box} = 950 \text{ nA} \quad n = 1.5 \quad V_{T0} = 455 \text{ mV} \quad \lambda_c = 0.4875 \quad L_{sat} = 19.5 \text{ nm}. \quad (3)$$

- Find the IC_{opt} , the value of the inversion coefficient for which the bias current is minimum. Assume no velocity saturation.
- Based on the IC_{opt} , find the values of the bias current, I_q , and the transistor aspect ratio, W/L , to achieve the specified gain-bandwidth, w_u .

Solutions to Exercise 5 (25.03.2021)

Problem 1 Common Source Analysis

- Draw the small-signal equivalent circuit of the CS.

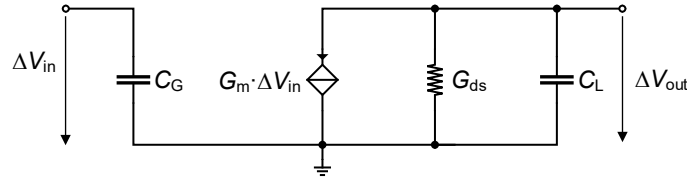


Figure 1: Common Source Amplifier Small Signal Equivalent Circuit.

where

$$\begin{aligned} C_G &\triangleq C_{Gi} + C_{Ge}; \\ C_L &\triangleq C_{L0} + C_w \cdot W. \end{aligned} \quad (1)$$

- Derive the expression of the transit frequency, ω_t , by using the small signal equivalent circuit.

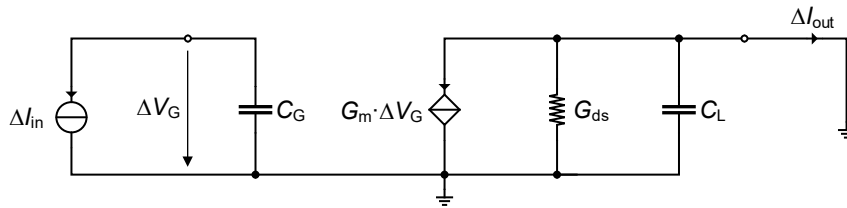


Figure 2: Small Signal Equivalent Circuit to derive ω_t .

So,

$$\begin{aligned} \Delta I_{in} &= sC_G V_G; \\ \Delta I_{out} &= G_m V_G, \end{aligned} \quad (2)$$

which leads to

$$\frac{\Delta I_{out}}{\Delta I_{in}} = \frac{G_m}{sC_G}. \quad (3)$$

By imposing $|\frac{\Delta I_{out}}{\Delta I_{in}}| = 1$, we have

$$\omega_t = \frac{G_m}{C_G}. \quad (4)$$

- Express ω_t in terms of the inversion coefficient, IC .

The term G_m can be written as

$$G_m = \frac{G_{ms}}{n} = \frac{G_{spec}}{n} g_{ms}. \quad (5)$$

while C_G is

$$C_G = C_{Gi} + C_{Ge} = W \cdot L \cdot C_{ox} \left(c_{Gi} + \frac{C_{Ge}}{W \cdot L \cdot C_{ox}} \right), \quad (6)$$

hence

$$\omega_t = \frac{\frac{G_{spec}}{n}}{W \cdot L \cdot C_{ox}} \cdot \frac{g_{ms}}{\left(c_{Gi} + \frac{C_{Ge}}{W \cdot L \cdot C_{ox}}\right)}. \quad (7)$$

Since $G_{spec} = \frac{I_{spec\Box}}{U_T} \cdot \frac{W}{L}$ and $I_{spec\Box} = 2n\mu C_{ox} U_T^2$, we obtain beinequation

$$\frac{\frac{G_{spec}}{n}}{W \cdot L \cdot C_{ox}} = \frac{2\mu U_T}{L^2} = \omega_{spec}, \quad (8)$$

and so

$$\omega_t = \omega_{spec} \cdot \frac{g_{ms}}{c_{Gi} + \frac{C_{Ge}}{W \cdot L \cdot C_{ox}}}. \quad (9)$$

By replacing g_{ms} we obtain

$$\omega_t = \omega_{spec} \cdot \frac{\frac{1}{2}(\sqrt{4IC} + 1) - 1}{c_{Gi} + \frac{C_{Ge}}{W \cdot L \cdot C_{ox}}}. \quad (10)$$

- Derive ω_{tspec} , the transit frequency for $IC = 1$ and WI.

For bias in WI

$$g_{ms} = IC, \quad (11)$$

hence, for $IC = 1$ we have

$$\omega_{tspec} = \frac{\omega_{spec}}{c_{Gi} + \frac{C_{Ge}}{W \cdot L \cdot C_{ox}}}. \quad (12)$$

- Derive the expression for the unity-gain frequency, ω_u .

For the CS in Fig. 1, we have

$$A_v = \frac{\Delta V_{out}}{\Delta V_{in}} = -\frac{G_m}{sC_L}. \quad (13)$$

By imposing $|A_v| = 1$, we obtain ω_u

$$\omega_u = \frac{G_m}{C_L}. \quad (14)$$

- Express ω_u in terms of the normalized gain-bandwidth (GBW) for a squared transistor biased in WI, $\omega_L \triangleq \frac{I_{spec\Box}}{nU_T C_L}$, and the normalized source transconductance, g_{ms} .

$$\omega_u = \frac{G_m}{C_L} = \frac{I_{spec\Box}}{nU_T C_L} \cdot \frac{W}{L} \cdot g_{ms} = \omega_L \cdot \frac{W}{L} \cdot g_{ms}. \quad (15)$$

Problem 2 Common Source Design

- Find the IC_{opt} , the value of the inversion coefficient for which the bias current is minimum. Assume no velocity saturation.

$$\Theta = \frac{C_w L}{C_{L0}} \cdot \frac{\omega_u}{\omega_L} = \frac{0.450 \text{ fFnm}^{-1} \cdot 40 \text{ nm}}{60 \text{ fF}} \cdot \frac{2\pi \cdot 18 \text{ MHz}}{\frac{950 \text{ nA}}{1.5 \cdot 26 \text{ mV} \cdot (60 \text{ fF} + 0.450 \text{ fF/nm} \cdot 40 \text{ nm})}} = 0.1086 \quad (16)$$

Hence,

$$IC_{opt} \cong 2\Theta + \text{sqrt}(\Theta) = 0.547 \quad (17)$$

- Based on the IC_{opt} , find the values of the bias current, I_q , and the transistor aspect ratio, W/L , to achieve the specified gain-bandwidth, w_u .

By using the formula reported in the text, we obtain

$$\begin{aligned} i_b &= \frac{0.547}{0.3927 - 0.1086} = 1.98254; \\ AR &= \frac{1}{0.3927 - 0.1086} = 3.5205, \end{aligned} \tag{18}$$

and finally

$$\begin{aligned} I_q &= i_b \cdot I_{spec\Box} \cdot \frac{\omega_u}{\omega_L} = 662 \text{ nA}; \\ \frac{W}{L} &= AR \cdot \frac{\omega_u}{\omega_L} = 1.275 \rightarrow W = 51 \text{ nm}. \end{aligned} \tag{19}$$