

# Low-power radio design for the IoT

## Exercise 8 (06.05.2021)

Christian Enz

Swiss Federal Institute of Technology (EPFL), Lausanne, Switzerland

### Problem 1 The Common-Gate LNA

The schematic of the common-gate LNA is shown in Figure 1. Assume that the transistors are biased in saturation and that they are fabricated in a deep-submicron technology so that channel-length modulation is not negligible.

 


Figure 1: Common-Gate LNA

#### 1.1 Small-signal analysis

- Draw the small-signal equivalent circuit.
- Derive the expression for the input impedance of the LNA, looking through the source of transistor  $M_1$ , at resonance.
- Calculate the small signal gain of the circuit assuming input matching.

#### 1.2 Noise analysis

- Draw the small-signal circuit including the noise sources.
- Calculate the noise figure of the LNA.

## Problem 2 Cascode Common Gate LNA

The common-gate LNA presented in the previous problem is now cascoded with a transistor  $M_2$ . The schematic of the cascode common-gate LNA is shown in Figure 2. Assume that the transistors are biased in saturation and that they are fabricated in a deep-submicron technology so that channel-length modulation is not negligible.

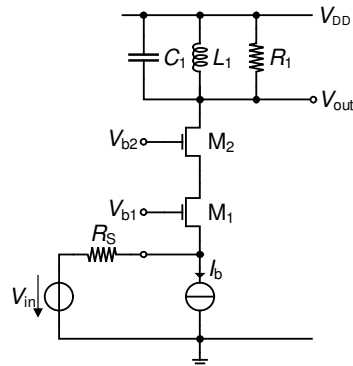


Figure 2: Cascode Common-Gate LNA

### 2.1 Small-signal analysis

- Draw the small-signal equivalent circuit.
- Derive the expression for the input impedance of the LNA, looking through the source of transistor  $M_1$ , at resonance.
- Compare the input impedance with that of the common-gate LNA.
- Calculate the small signal gain of the circuit assuming input matching.

### 2.2 Noise analysis

- Draw the small-signal circuit including the noise sources.
- Calculate the noise contribution of transistor  $M_2$  to the output noise (neglect the channel length modulation of  $M_2$ ).
- Calculate the noise figure of the LNA.

## Solutions to Exercise 8 (06.05.2021)

### Problem 1 Analysis of Common-Gate LNA

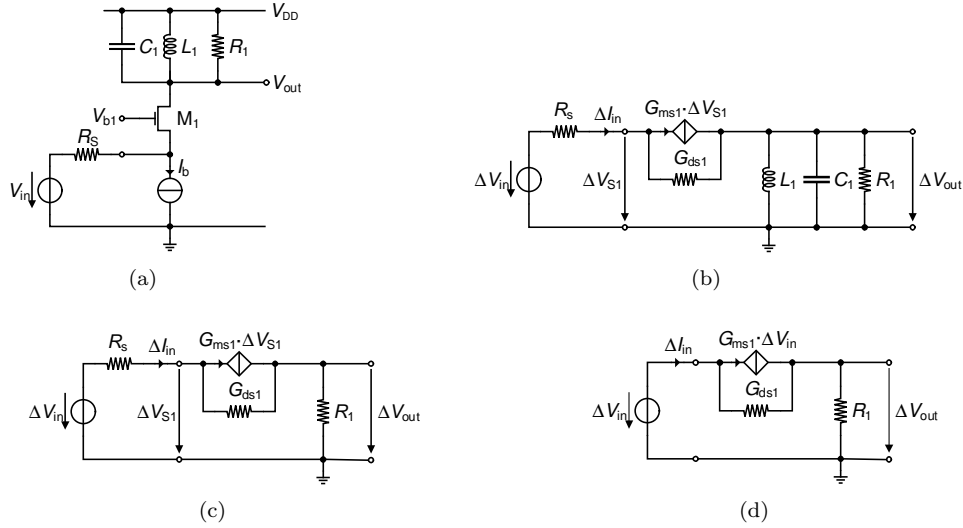


Figure 1: a) Schematic of the common-gate LNA. b) Corresponding small-signal schematic. c) Corresponding small-signal schematic at resonance. d) Small-signal schematic used for input impedance calculation.

#### 1.1 Small Signal Analysis

- Draw the small-signal equivalent circuit.
- Derive the expression for the input impedance of the LNA, looking through the source of transistor  $M_1$ , at resonance.
- Calculate the small signal gain of the circuit assuming input matching.

Fig. 1(b) shows the small-signal schematic of the common-gate LNA. At resonance, the small-signal schematic reduces to that of Fig. 1(c). The input impedance of the circuit looking through the source of  $M_1$ , can then be calculated as

$$Z_{in} \triangleq \left. \frac{\Delta V_{in}}{\Delta I_{in}} \right|_{I_{out}=0} = \frac{1 + R_1 G_{ds1}}{G_{ms1} + G_{ds1}}. \quad (1)$$

Assuming that the intrinsic gain of  $M_1$ ,  $G_{ms1}/G_{ds1}$ , is much greater than unity, (1) reduces to

$$Z_{in} \cong \frac{1}{G_{ms1}} + \frac{R_1}{G_{ms1}/G_{ds1}}. \quad (2)$$

Eq. (2) reveals the impact of the drain conductance on input impedance of the LNA. In modern technologies the intrinsic gain  $G_{ms1}/G_{ds1}$  is quite low (of the order of 10). Thus, the second term in (2) could be comparable to or even exceed the  $1/G_{ms1}$  term, resulting in an increase of the input impedance and making it difficult to match to a  $50 \Omega$  resistance.

The small-signal gain can be calculated from the schematic in Fig. 1(c) resulting in

$$A_v = \frac{\Delta V_{out}}{\Delta V_{in}} = \frac{R_1(G_{ms1} + G_{ds1})}{1 + R_1 G_{ds1} + R_S(G_{ms1} + G_{ds1})} = \frac{G_{ms1} R_1 (1 + G_{ds1}/G_{ms1})}{1 + R_1 G_{ds1} + G_{ms1} R_S (1 + G_{ds1}/G_{ms1})}. \quad (3)$$

For a long-channel device, we can assume that  $G_{ms1} \gg G_{ds1}$ . If additionally it is assumed that  $G_{ms1}R_S \ll 1$  and  $R_1G_{ds1} \ll 1$ , then (3) reduces to

$$A_v \cong G_{ms1} \cdot R_1. \quad (4)$$

For matched input, i.e.,  $Z_{in} = R_S$ , using (1) in (3), we obtain,

$$A_v|_{matched} = \frac{R_1(G_{ms1} + G_{ds1})}{2(1 + R_1G_{ds1})}. \quad (5)$$

If  $R_1$  is comparable to  $1/G_{ds1}$ , then the voltage gain of the common-gate LNA stage is of the order of  $G_{ms1}/4G_{ds1}$ , which is a very low value compared to the value obtained for a long-channel device

$$A_v|_{matched} = \frac{G_{ms1}R_1}{2}. \quad (6)$$

## 1.2 Noise analysis

- Draw the small-signal circuit including the noise sources.
- Calculate the noise figure of the LNA.

 


Figure 2: Small signal schematic showing the noise sources.

The output noise voltage can be calculated from the small-signal schematic including all the noise sources shown in Fig. 2 as

$$V_{nout} = R_{mRs} \cdot I_{nRs} + R_{m1} \cdot I_{n1} + R_{mR1} \cdot I_{nR1}, \quad (7)$$

with

$$R_{mRs} = A_v \cdot R_S, \quad (8a)$$

$$R_{m1} = \frac{R_1}{1 + (G_{ms1} + G_{ds1})R_S + G_{ds1}R_1}, \quad (8b)$$

$$R_{mR1} = -\frac{R_1(1 + (G_{ms1} + G_{ds1})R_S)}{1 + (G_{ms1} + G_{ds1})R_S + G_{ds1}R_1}. \quad (8c)$$

The output thermal noise resistance is then equal to

$$R_{nout} = |R_{mRs}|^2 \cdot \frac{1}{R_S} + |R_{m1}|^2 \cdot G_{n1} + |R_{mR1}|^2 \cdot \frac{1}{R_1}, \quad (9)$$

where  $G_{n1} = \delta_{nD1} \cdot G_{ms1}$ . The input thermal noise resistance is then given by dividing (9) by  $|A_v|^2$ , resulting in

$$R_{nin} = R_S + \frac{\delta_{nD1} \cdot G_{ms1}}{(G_{ms1} + G_{ds1})^2} + \left( \frac{1 + (G_{ms1} + G_{ds1})R_S}{(G_{ms1} + G_{ds1})R_S} \right)^2 \cdot \frac{R_S^2}{R_1}. \quad (10)$$

For a long-channel device  $G_{ms1} \gg G_{ds1}$  and (10) reduces to

$$R_{nin} \cong R_S + \frac{\delta_{nD1}}{G_{ms1}} + \left( 1 + \frac{1}{G_{ms1}R_S} \right)^2 \cdot \frac{R_S^2}{R_1}. \quad (11)$$

The noise factor is then given by

$$F = \frac{R_{nin}}{R_S} = 1 + \frac{\delta_{nD1} \cdot G_{ms1}}{R_S(G_{ms1} + G_{ds1})^2} + \left( \frac{1 + (G_{ms1} + G_{ds1})R_S}{(G_{ms1} + G_{ds1})R_S} \right)^2 \cdot \frac{R_S}{R_1}, \quad (12)$$

which for a long-channel device reduces to

$$F \cong 1 + \frac{\delta_{nD1}}{G_{ms1}R_S} + \left(1 + \frac{1}{G_{ms1}R_S}\right)^2 \cdot \frac{R_S}{R_1}. \quad (13)$$

Under impedance matching  $G_{ms1}R_S = 1$  and (13) reduces to

$$F|_{matched} \cong 1 + \delta_{nD1} + 4 \frac{R_S}{R_1}. \quad (14)$$

## Problem 2 Analysis of the Cascode Common-Gate LNA

### 2.1 Small Signal Analysis

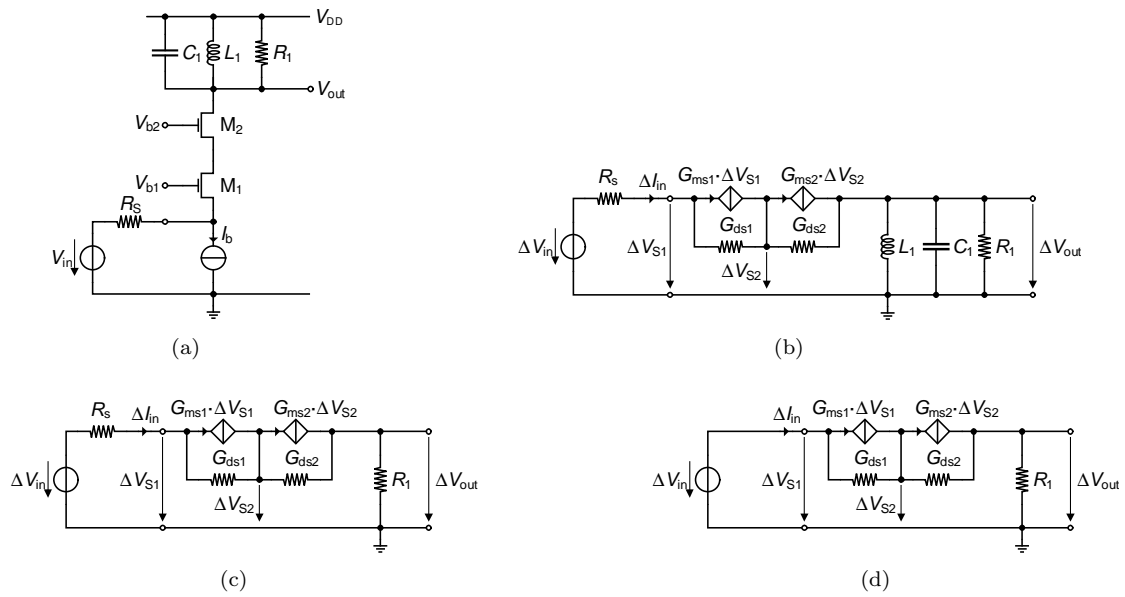


Figure 3: a) Schematic of the common-gate LNA. b) Corresponding small-signal schematic. c) Corresponding small-signal schematic at resonance. d) Small-signal schematic used for input impedance calculation.

### 2.2 Small-signal analysis

- Draw the small-signal equivalent circuit.
- Derive the expression for the input impedance of the LNA, looking through the source of transistor  $M_1$ , at resonance.
- Compare the input impedance with that of the common-gate LNA.
- Calculate the small signal gain of the circuit assuming input matching.

The problem of high input impedance of the common-gate LNA can be alleviated by introducing a cascode transistor as shown in Fig. 3(a). Its small-signal schematic is shown in Fig. 3(b) which at resonance reduces to Fig. 3(c).

The input impedance of the circuit looking through the source of  $M_1$  can easily be calculated from the schematic shown in Fig. 1(d) resulting in

$$Z_{in} \triangleq \left. \frac{\Delta V_{in}}{\Delta I_{in}} \right|_{\Delta I_{out}=0} = \frac{G_{ds1} + G_{ds2} + G_{ms2} + G_{ds1}G_{ds2}R_1}{(G_{ds1} + G_{ms1})(G_{ds2} + G_{ms2})}. \quad (15)$$

Assuming that the intrinsic gain of  $M_1$  and  $M_2$  are much greater than unity, i.e.  $G_{ms1}/G_{ds1} \gg 1$  and  $G_{ms2}/G_{ds2} \gg 1$  results in

$$Z_{in} \cong \frac{1}{G_{ms1}} + \frac{G_{ds1}G_{ds2}R_1}{G_{ms1} \cdot G_{ms2}} \quad (16)$$

The second term in (16) shows that  $R_1$  is divided by the intrinsic gains of two transistors and therefore its effect on input impedance is negligible (compare with (2)). Hence,

$$Z_{in} \cong \frac{1}{G_{ms1}}. \quad (17)$$

The voltage gain assuming again that  $G_{ms1}/G_{ds1} \gg 1$  and  $G_{ms2}/G_{ds2} \gg 1$  is then given by

$$A_v \cong \frac{G_{ms1}R_1}{1 + G_{ms1}R_S}, \quad (18)$$

which turns out to be independent of  $G_{ms2}$ . The small-signal voltage assuming input matching  $Z_{in} = 1/G_{ms1} = R_S$  reduces to

$$A_v \cong \frac{G_{ms1}R_1}{2}. \quad (19)$$

### 2.3 Noise analysis

 


Figure 4: Small signal schematic showing the noise sources.

- Draw the small-signal circuit including the noise sources.
- Calculate the noise contribution of transistor  $M_2$  to the output noise (neglect the channel length modulation of  $M_2$ ).
- Calculate the noise figure of the LNA.

The derivation of the output noise voltage can be simplified by neglecting  $G_{ds2}$  in the schematic of Fig. 4. Note that if we also neglect  $G_{ds1}$ , then the noise coming from  $M_2$  is zero. After solving the Kirkhoff equations and assuming that  $G_{ms1}/G_{ds1} \gg 1$  and  $G_{ds1}R_S \ll 1$ , we get the output noise voltage as

$$V_{nout} \cong \frac{R_1}{1 + G_{ms1}R_S} \cdot I_{n1} + \frac{G_{ds1}R_1}{G_{ms2}(1 + G_{ms1}R_S)} \cdot I_{n2} - R_1 \cdot I_{nR1} + \frac{G_{ms1}R_1R_S}{1 + G_{ms1}R_S} \cdot I_{nRs} \quad (20)$$

The corresponding output noise resistance is then given by

$$R_{nout} \cong \left( \frac{R_1}{1 + G_{ms1}R_S} \right)^2 \cdot G_{n1} + \left( \frac{G_{ds1}R_1}{G_{ms2}(1 + G_{ms1}R_S)} \right)^2 \cdot G_{n2} + R_1^2 \cdot G_1 + \left( \frac{G_{ms1}R_S R_1}{1 + G_{ms1}R_S} \right)^2 \cdot G_S, \quad (21)$$

where  $G_S \triangleq 1/R_S$ ,  $G_1 \triangleq 1/R_1$ . The input-referred noise resistance is given by dividing (21) by the square of the voltage gain (18), resulting in

$$R_{nin} \cong R_S + \frac{G_{n1}}{G_{ms1}^2} + \left( \frac{G_{ds1}}{G_{ms1}G_{ms2}} \right)^2 \cdot G_{n2} + \left( \frac{1 + G_{ms1}R_S}{G_{ms1}} \right)^2 \frac{1}{R_1} \quad (22)$$

$$\cong R_S + \frac{G_{n1}}{G_{ms1}^2} + \left( \frac{1 + G_{ms1}R_S}{G_{ms1}} \right)^2 \frac{1}{R_1}. \quad (23)$$

From (24), we see that, like in a normal cascode, the noise contribution from  $M_2$  is divided by the square of the intrinsic gain of the driver transistor  $M_1$  and can hence be neglected. This is without accounting for the parasitic capacitance at the cascode node which lowers the gain and increases the contribution of  $M_2$  to the input-referred noise. At RF we are mostly interested by the thermal noise coming from  $M_1$  and  $M_2$ . Hence we can replace  $G_{n1}$  and  $G_{n2}$  by  $\delta_{nD1} \cdot G_{ms1}$  and  $\delta_{nD2} \cdot G_{ms2}$ , resulting in

$$R_{nin} \cong R_S + \frac{\delta_{nD1}}{G_{ms1}} + \frac{\delta_{nD2} G_{ds1}^2}{G_{ms1}^2 G_{ms2}} + \left( \frac{1 + G_{ms1} R_S}{G_{ms1}} \right)^2 \frac{1}{R_1} \quad (24)$$

$$\cong R_S + \frac{\delta_{nD1}}{G_{ms1}} + \left( \frac{1 + G_{ms1} R_S}{G_{ms1}} \right)^2 \frac{1}{R_1}. \quad (25)$$

The corresponding noise factor is then given by

$$F \triangleq \frac{R_{nin}}{R_S} \cong 1 + \frac{\delta_{nD1}}{G_{ms1} R_S} + \frac{\delta_{nD2} G_{ds1}^2}{G_{ms1}^2 G_{ms2} R_S} + \frac{(1 + G_{ms1} R_S)^2}{G_{ms1}^2 R_S R_1} \quad (26)$$

$$\cong 1 + \frac{\delta_{nD1}}{G_{ms1} R_S} + \frac{(1 + G_{ms1} R_S)^2}{G_{ms1}^2 R_S R_1}. \quad (27)$$

Under matched condition  $Z_{in} = 1/G_{ms1} = R_S$  we have

$$F|_{matched} \cong 1 + \delta_{nD1} + \frac{\delta_{nD2} G_{ds1}^2}{G_{ms1} G_{ms2}} + \frac{4}{G_{ms1} R_1}. \quad (28)$$