

# Low-power radio design for the IoT

## Exercise 9 (20.05.2021)

Christian Enz

Swiss Federal Institute of Technology (EPFL), Lausanne, Switzerland

### Problem 1 Dual Gate Mixer

Consider the dual-gate mixer shown in Fig. 1. Assume when  $M_1$  is on, it has an on-resistance of  $R_{on1}$ . Also, assume abrupt edges and a 50% duty cycle for the LO, also  $G_{ds1} = G_{ds2} = 0$  and the connection between bulk and source.

- Compute the voltage conversion gain of the circuit. Assume  $M_2$  does not enter the linear region and denote its transconductance by  $g_{m2}$ .
- If  $R_{on1}$  is very small, determine the  $IP_2$  of the circuit. Assume  $M_2$  has an overdrive of  $V_{GS0} - V_{TH}$  in the absence of signals (when it is on).

### Problem 2 Active mixer with load mismatch

Consider the active mixer shown in Fig. 2, where LO has abrupt edges and a 50% duty cycle. Also, assume  $G_{ds1} = G_{ds2} = 0$  and the connection between bulk and source. The load resistors exhibit mismatch, but the circuit is otherwise symmetric. Assume  $M_1$  carries a bias current of  $I_{ss}$ .

- Determine the output offset voltage.
- Determine the  $IP_2$  of the circuit in terms of the overdrive and bias current of  $M_1$ .

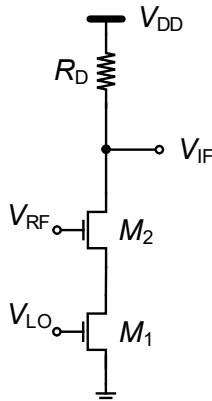


Figure 1: Dual-gate mixer

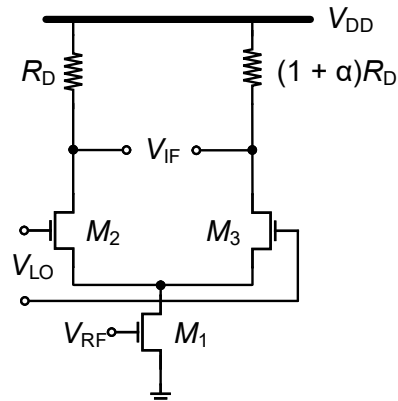


Figure 2: Active mixer with load mismatch

## Solutions to Exercise 9 (20.05.2021)

### Problem 1 Dual-Gate mixer

Consider the dual-gate mixer shown in Fig. 1. Assume when  $M_1$  is on, it has an on-resistance of  $R_{on1}$ . Also, assume abrupt edges and a 50% duty cycle for the LO, also  $G_{ds1} = G_{ds2} = 0$  and the connection between bulk and source.

- Compute the voltage conversion gain of the circuit. Assume  $M_2$  does not enter the linear region and denote its transconductance by  $g_{m2}$ .

The output voltage of the mixer can be written as

$$V_{IF}(t) = I_{RF}(t) \cdot R_D \cdot S_{LO}(t) \quad (1)$$

where  $S_{LO}$  is the square wave toggling between 1 and 0 applied to the gate of  $M_1$ . This square wave can be approximated by its first component and give raise to the following approximation:

$$V_{IF}(t) = I_{RF}(t) \cdot R_D \cdot \frac{2}{\pi} \cos(\omega_{LO}t) \quad (2)$$

The  $I_{RF}$  current can be derived by solving the following small signal equivalent circuit from which

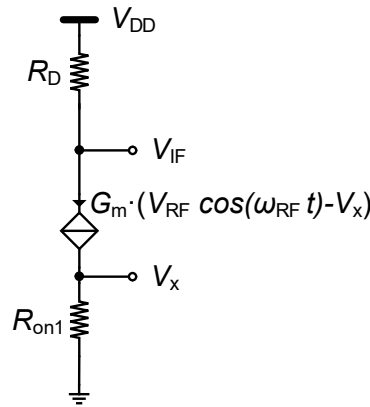


Figure 1: Small signal equivalent of the dual-gate mixer

$$I_{RF}(t) = \frac{G_{m2}}{1 + G_{m2}R_{on1}} V_{RF} \cos(\omega_{RF}t) \quad (3)$$

The output  $V_{IF}$  can be then re-written as

$$V_{IF}(t) = \frac{G_{m2}}{1 + G_{m2}R_{on1}} V_{RF} \cos(\omega_{RF}t) \cdot R_D \cdot \frac{2}{\pi} \cos(\omega_{LO}t) \quad (4)$$

which for the  $\cos((\omega_{RF} - \omega_{LO})t)$  components results into

$$V_{IF}(t) = \frac{G_{m2}}{1 + G_{m2}R_{on1}} V_{RF} \cdot R_D \cdot \frac{1}{\pi} \cos((\omega_{RF} - \omega_{LO})t) \quad (5)$$

Finally, the conversion gain can be expressed as

$$\frac{V_{IFp}}{V_{RFp}} = \frac{1}{\pi} \cdot \frac{G_{m2}}{1 + G_{m2}R_{on1}} \cdot R_D \quad (6)$$

- If  $R_{on1}$  is very small, determine the  $IP_2$  of the circuit. Assume  $M_2$  has an overdrive of  $V_{GS0} - V_{TH}$  in the absence of signals (when it is on).

The total voltage applied to the gate of  $M_2$  to evaluate the  $IP_2$  is equal to

$$V_{RF} = V_m \cos(\omega_1 t) + V_m \cos(\omega_2 t) + V_{GS0} \quad (7)$$

This determines a second order intermodulation component that can be written as

$$I_{IM2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_m^2 \cos((\omega_1 - \omega_2)t) \quad (8)$$

To derive the  $IP_2$ ,  $V_{IIP2}$ , we equate the two expressions

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{IIP2}^2 R_D = \frac{1}{\pi} \cdot \frac{G_{m2}}{1 + G_{m2} R_{on1}} \cdot R_D V_{IIP2} \quad (9)$$

and we obtain, for  $G_{m1} \gg 1/R_{on}$ , the following expression

$$V_{IIP2} = \frac{2}{\pi} (V_{GS0} - V_{th})_2 \quad (10)$$

## Problem 2 Active mixer with load mismatch

Consider the active mixer shown in Fig. 2, where LO has abrupt edges and a 50% duty cycle. Also, assume  $G_{ds1} = G_{ds2} = 0$  and the connection between bulk and source. The load resistors exhibit mismatch, but the circuit is otherwise symmetric. Assume  $M_1$  carries a bias current of  $I_{ss}$ .

- Determine the output offset voltage.

In the circuit in Fig. 2, transistor  $M_1$  produces a small-signal drain current equal to  $g_{m1} V_{RF}$ . With abrupt LO switching,  $M_2$  multiplies  $I_{ss}$  by a square wave toggling between 0 and 1,  $S(t)$ , and  $M_3$  by  $S(t - \frac{T_{LO}}{2})$  because the input pair is differentially driven. It follows that:

$$I_2 = I_{ss} \cdot S(t) \quad (11a)$$

$$I_3 = I_{ss} \cdot S\left(t - \frac{T_{LO}}{2}\right) \quad (11b)$$

It follows:

$$V_{out}(t) = I_3 R_D (1 + \alpha) - I_2 R_D = \underbrace{I_{ss} \alpha R_D S\left(t - \frac{T_{LO}}{2}\right)}_{\text{Offset term}} + \underbrace{I_{ss} R_D \left(S\left(t - \frac{T_{LO}}{2}\right) - S(t)\right)}_{\text{Original term}} \approx \quad (12)$$

$$\approx I_{ss} \alpha R_D \frac{2}{\pi} \cos(\omega_{LO} t) + I_{ss} R_D \frac{4}{\pi} \cos(\omega_{LO} t);$$

where the approximation takes into consideration the fundamental amplitude of the square wave. Therefore the output offset is  $I_{ss} \alpha R_D \frac{2}{\pi}$ .

- Determine the  $IP_2$  of the circuit in terms of the overdrive and bias current of  $M_1$ .

In order to calculate the IP<sub>2</sub> we assume  $M_1$  gate voltage to be:

$$V_{\text{RF}} = V_{\text{ov}} \cos(\omega_1 t) + V_{\text{ov}} \cos(\omega_2 t) + V_{\text{GS0}}; \quad (13)$$

where  $V_{\text{GS0}}$  is the bias gate-source voltage of  $M_1$  and  $V_{\text{ov}}$  is the overdrive voltage. With a square-law device, the second order intermodulation IM<sub>2</sub> product emerges in the current of  $M_1$  as

$$\text{IM}_2 = \frac{1}{2} \mu C_{\text{ox}} \frac{W}{L} V_{\text{m}}^2 \cos((\omega_1 - \omega_2)t) \quad (14)$$

Multiplying this quantity by  $\alpha R_{\text{D}} \frac{2}{\pi}$  yields the direct feed-through to the output:

$$V_{\text{IM2,out}} = \left( \frac{1}{2} \mu C_{\text{ox}} \frac{W}{L} V_{\text{m}}^2 \cos((\omega_1 - \omega_2)t) \right) \alpha R_{\text{D}} \frac{2}{\pi} \quad (15)$$

To calculate the IP<sub>2</sub>, the value of  $V_{\text{ov}}$  must be raised until the amplitude of  $V_{\text{IM2,out}}$  becomes equal to the amplitude of the main downconverted components. This amplitude is simply given by  $(2/\pi)g_{m1}R_{\text{D}}V_{\text{ov}}$ . Thus

$$\begin{aligned} \frac{1}{2} \mu C_{\text{ox}} \frac{W}{L} V_{\text{m}}^2 \alpha R_{\text{D}} \frac{2}{\pi} &= \frac{2}{\pi} g_{m1} R_{\text{D}} V_{\text{IIP2}} \\ &= \frac{2}{\pi} \mu C_{\text{ox}} \frac{W}{L} V_{\text{ov1}} R_{\text{D}} V_{\text{IIP2}} \end{aligned} \quad (16)$$

where  $g_{m1} = \mu C_{\text{ox}}(W/L)V_{\text{ov1}}$ . Finally,

$$V_{\text{IIP2}} = \frac{\alpha V_{\text{ov1}}}{2} \quad (17)$$