

Low-power radio design for the IoT

Exercise 4 (24.03.2022)

Christian Enz

Swiss Federal Institute of Technology (EPFL), Lausanne, Switzerland

Problem 1 Low-power Common Source RF Design

The circuit in the Figure below is a single MOSFET Common Source (CS) Amplifier.

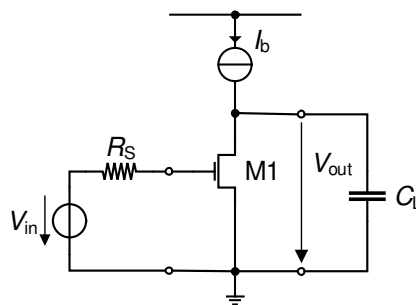


Figure 1: Common Source Amplifier.

- Find the optimum inversion coefficient of the common-source amplifier shown in ?? for maximizing the following figure-of-merit

$$FoM \triangleq \frac{\omega_u}{(F-1) \cdot I_b}. \quad (1)$$

- Calculate the bias current required to achieve a gain-bandwidth $f_u = 10 \text{ GHz}$ for a load capacitance $C_L = 10 \text{ fF}$ with $\lambda_c = 0.25$.
- Calculate the resulting noise factor F for a source impedance $R_S = 50 \Omega$.
- How can you reduce this noise factor?

Problem 2 Common Source Design

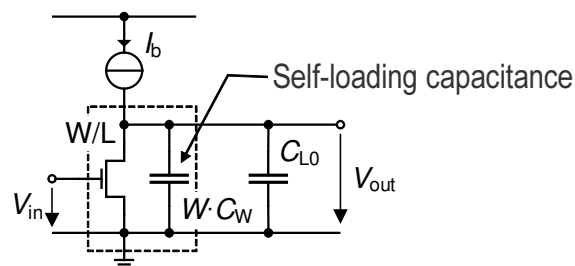


Figure 2: Common source amplifier including the self-loading capacitance.

The normalized bias current and aspect ratio for the CS amplifier

$$\begin{aligned} i_b &\triangleq \frac{I_D}{I_{spec\Box}} \cdot \frac{1}{\Omega} = \frac{IC}{g_{ms} - \Theta}; \\ AR &\triangleq \frac{W}{L} \cdot \frac{1}{\Omega} = \frac{1}{g_{ms} - \Theta}, \end{aligned} \quad (2)$$

where $\Omega \triangleq \frac{\omega_u}{\omega_L}$ and Θ is equal to $\frac{C_w L}{C_{L0}} \cdot \frac{\omega_u}{\omega_L} = \frac{\omega_u}{\omega_{t\text{spec}}}$.

Design the CS amplifier, shown in Fig. 2, for the following specifications at room temperature:

$$f_u = 18 \text{ MHz} \quad C_{L0} = 60 \text{ fF} \quad V_{DD} = 1.8 \text{ V} \quad L = 40 \text{ nm} \quad C_w = 0.450 \text{ fF/nm}, \quad (3)$$

and by assuming the following values for the technology parameters

$$I_{\text{spec}\square} = 950 \text{ nA} \quad n = 1.5 \quad V_{T0} = 455 \text{ mV} \quad \lambda_c = 0.4875 \quad L_{\text{sat}} = 19.5 \text{ nm}. \quad (4)$$

- Find the IC_{opt} , the value of the inversion coefficient for which the bias current is minimum. Assume no velocity saturation.
- Based on the IC_{opt} , find the values of the bias current, I_q , and the transistor aspect ratio, W/L , to achieve the specified gain-bandwidth, ω_u .

Problem 1: Low-power common source RF design

$$fF \equiv 10^{-15} \cdot F$$

$$K \equiv \frac{J}{1.38 \cdot 10^{-23}}$$

$$k_B \equiv 1.38 \cdot 10^{-23} \cdot \frac{J}{K}$$

$$q \equiv 1.6 \cdot 10^{-19} \cdot C$$


$$T := 300 \cdot K$$

$$U_T := \frac{k_B \cdot T}{q}$$


$$U_T = 25.875 \cdot \text{mV}$$


$$\lambda_c := 0.25$$
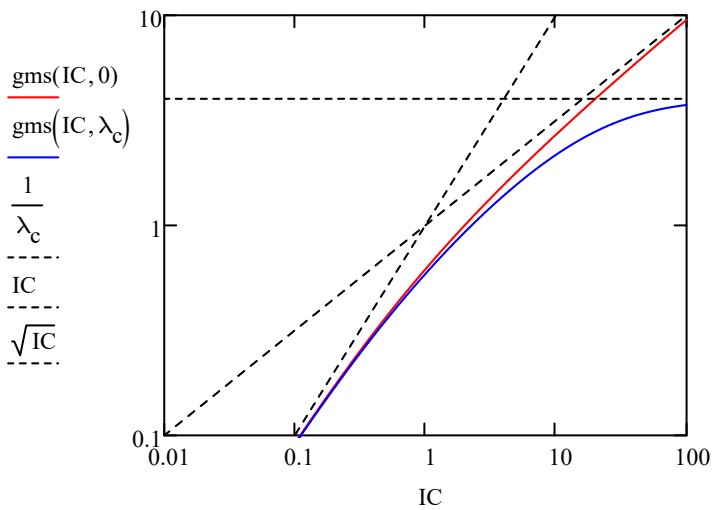
$$gms(IC, \lambda_c) := \frac{\sqrt{(\lambda_c \cdot IC + 1)^2 + 4 \cdot IC} - 1}{\lambda_c \cdot (\lambda_c \cdot IC + 1) + 2}$$


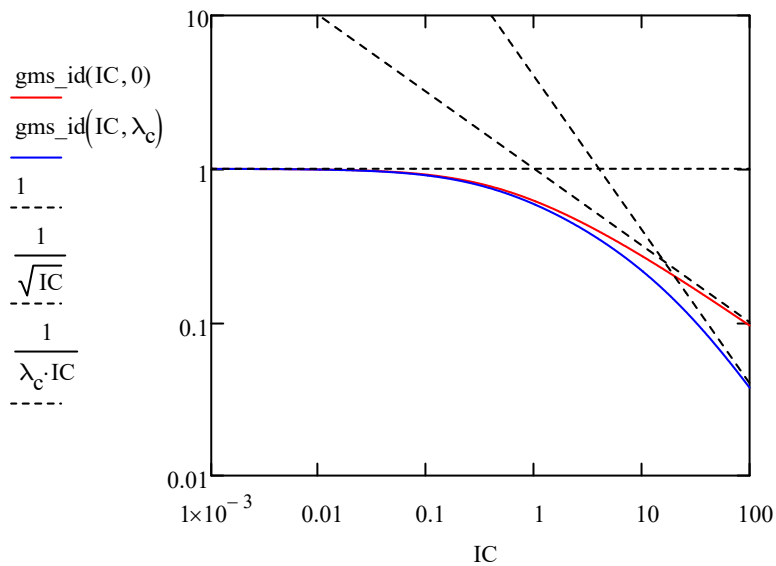
$$gms_id(IC, \lambda_c) := \frac{gms(IC, \lambda_c)}{IC}$$



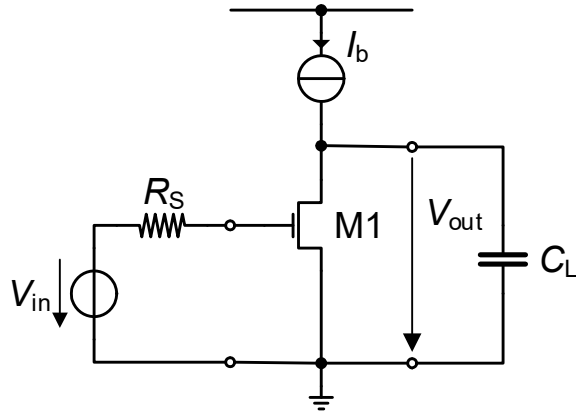

$$\text{FoM} = \frac{\omega_u}{(F-1) \cdot I_b} = \frac{R_S}{\gamma_{nD}} \cdot \frac{G_m \cdot \omega_t}{I_b}$$

$$n := 1.3$$

$$\lambda_c := 0.25$$

$$I_{C_{\text{opt}}} := \frac{1}{\frac{4}{\lambda_c^3}}$$

$$I_{C_{\text{opt}}} = 6.35$$

$$C_L := 20 \cdot \text{fF}$$

$$f_u := 10 \cdot \text{GHz}$$

$$\omega_u := 2 \cdot \pi \cdot f_u$$

$$G_m := \omega_u \cdot C_L$$

$$G_m = 1.257 \frac{\text{mA}}{\text{V}}$$

$$I_b := \frac{G_m \cdot n \cdot U_T}{\text{gms_id}(I_{C_{\text{opt}}}, \lambda_c)}$$

$$I_b = 152.283 \mu\text{A}$$

$$\gamma_{nD} := n \cdot \frac{2}{3}$$

$$R_S := 50 \cdot \Omega$$

$$F := 1 + \frac{\gamma_{nD}}{G_m \cdot R_S}$$

$$F = 14.793$$

Problem 2: Common source design for given GBW

$$fF \equiv 10^{-15} \cdot F$$

$$K \equiv \frac{J}{1.38 \cdot 10^{-23}}$$

$$k_B \equiv 1.38 \cdot 10^{-23} \cdot \frac{J}{K}$$


$$q \equiv 1.6 \cdot 10^{-19} \cdot C$$

$$T := 300 \cdot K$$


$$U_T := \frac{k_B \cdot T}{q}$$

$$U_T = 25.875 \cdot mV$$
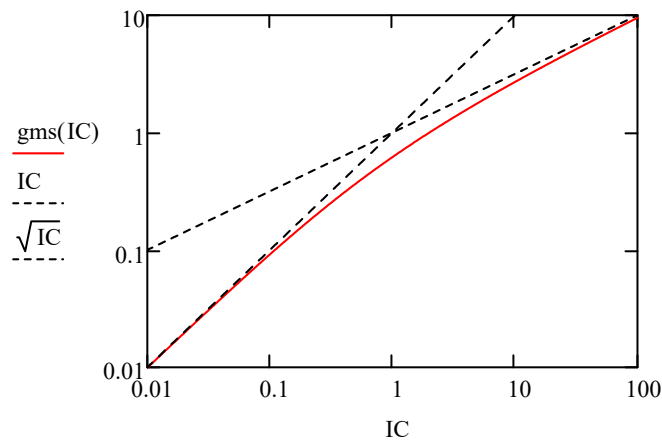
$$g_{ms}(IC) := \frac{\sqrt{4 \cdot IC + 1} - 1}{2}$$


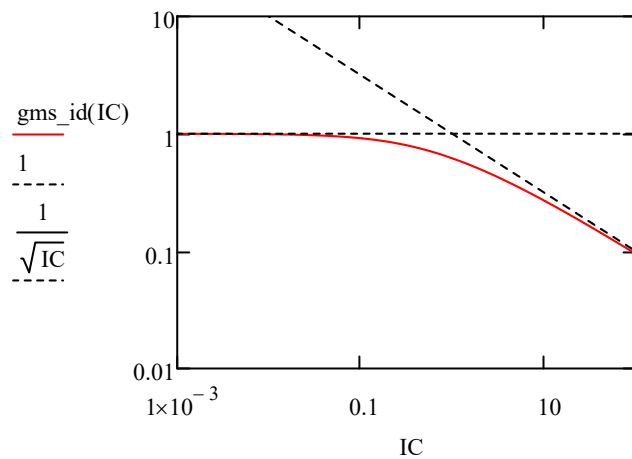
$$g_{ms_id}(IC) := \frac{g_{ms}(IC)}{IC}$$



$$i_b = \frac{I_b}{I_{specsq}} \cdot \frac{1}{\Omega}$$

$$\Omega = \frac{\omega_u}{\omega_L}$$

$$\omega_u = \frac{G_m}{C_L}$$

$$\omega_L = \frac{I_{specsq}}{n \cdot U_T \cdot C_{L0}}$$

$$\Theta = \frac{\omega_u}{\omega_w}$$



$$\omega_w = \frac{I_{specsq}}{n \cdot U_T \cdot C_W \cdot L}$$

$$AR = \frac{W}{L} \cdot \frac{1}{\Omega}$$

$$i_b(IC, \Theta) := \frac{IC}{gms(IC) - \Theta}$$

$$i_b(1, 0.1) = 1.93$$
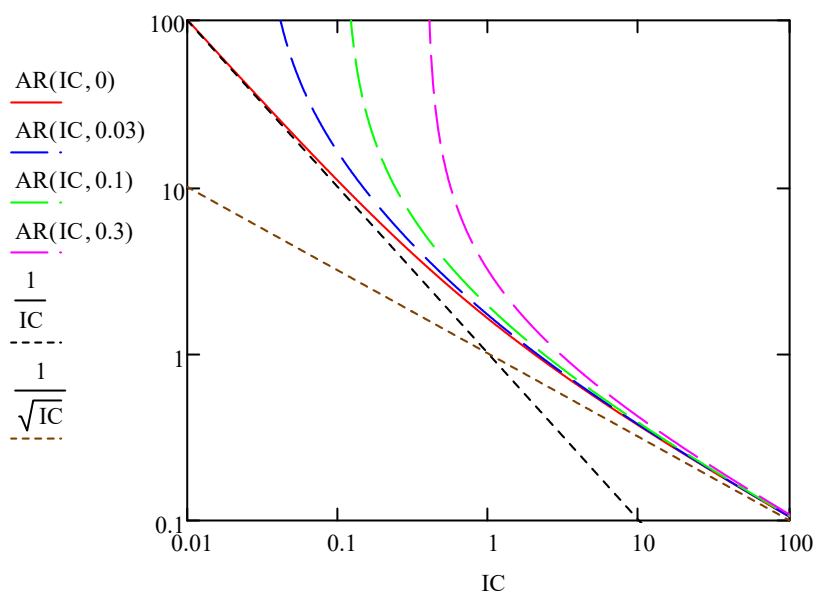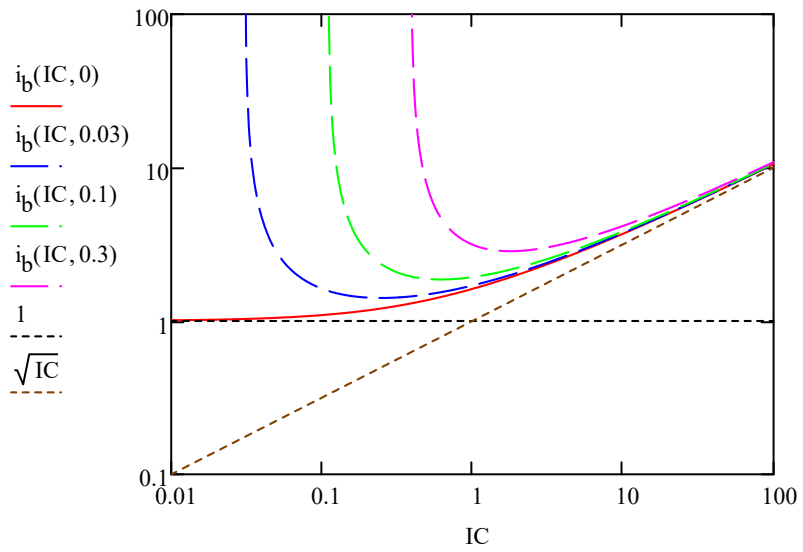
$$AR(IC, \Theta) := \frac{1}{gms(IC) - \Theta}$$



$$IC_{opt}(\Theta) := 2 \cdot \Theta \cdot (1 + \Theta) + (1 + 2 \cdot \Theta) \cdot \sqrt{\Theta \cdot (1 + \Theta)}$$

$$IC_{opt}(\Theta) := \left[\sqrt{\Theta \cdot (1 + \Theta)} + \Theta + \frac{1}{2} \right]^2 - \frac{1}{4}$$

$$IC_{\text{opt}}(0.1) = 0.618$$

$$i_{\text{bopt}}(\Theta) := i_b(IC_{\text{opt}}(\Theta), \Theta)$$



$$i_{\text{bopt}}(\Theta) := 1 + 2 \cdot \Theta + 2 \cdot \sqrt{\Theta \cdot (1 + \Theta)}$$

$$AR_{\text{opt}}(\Theta) := AR(IC_{\text{opt}}(\Theta), \Theta)$$

$$AR_{\text{opt}}(\Theta) := \frac{1}{\sqrt{\Theta \cdot (1 + \Theta)}}$$

$$IC_{\text{lim}}(\Theta) := \Theta \cdot (1 + \Theta)$$


$$IC_{\text{lim}}(0.1) = 0.11$$

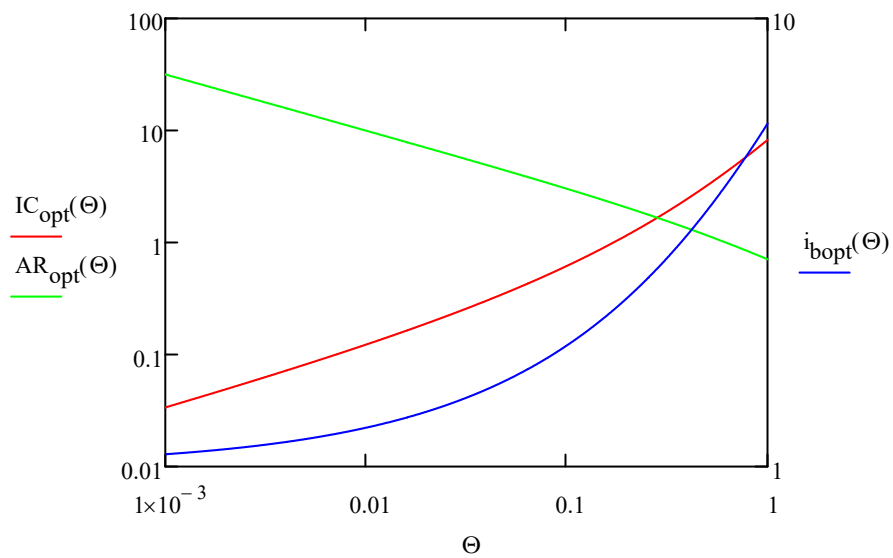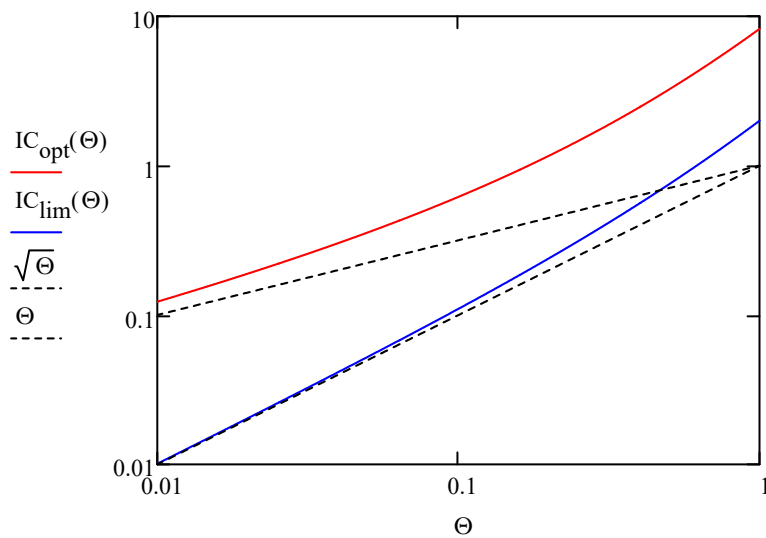


The effective optimum bias current is then given by

$$i_{\text{bias}} = \frac{I_b}{I_{\text{specsq}}} = \Omega \cdot i_b = \kappa \cdot \Theta \cdot i_b \quad \kappa = \frac{\omega_w}{\omega_L} = \frac{C_{L0}}{C_W \cdot L}$$
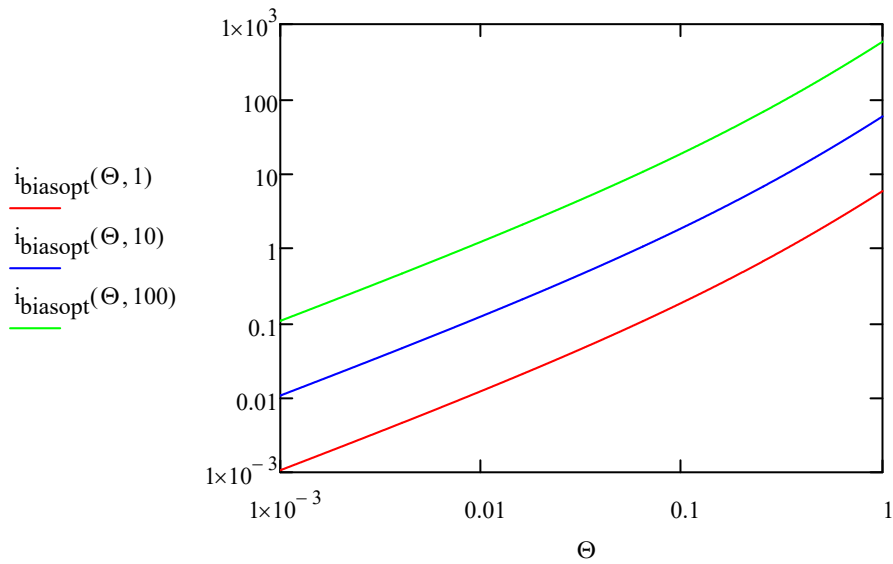
$$i_{\text{biasopt}}(\Theta, \kappa) := \kappa \cdot \Theta \cdot i_{\text{bopt}}(\Theta)$$


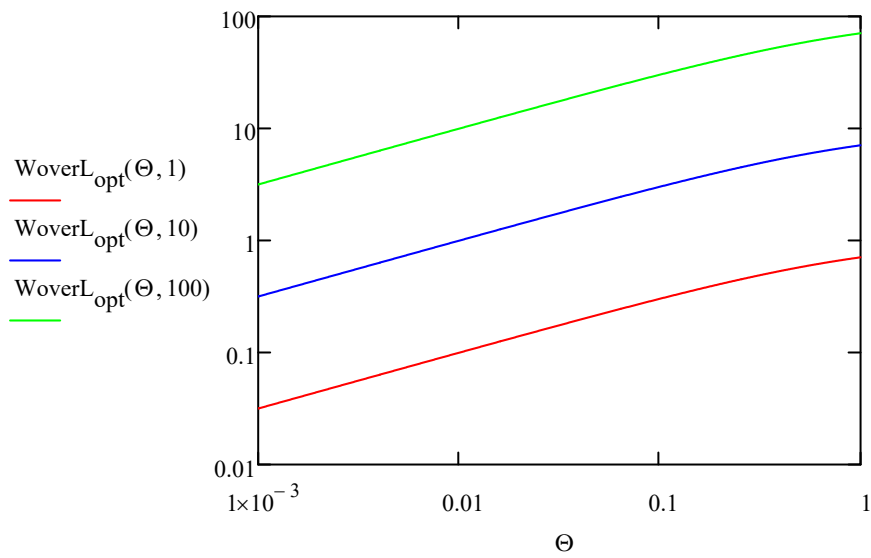
$$\text{WoverL}_{\text{opt}}(\Theta, \kappa) := \kappa \cdot \Theta \cdot \text{AR}_{\text{opt}}(\Theta)$$



2) Design example in 40nm CMOS technology

$$I_{\text{specsq}} := 950 \cdot \text{nA}$$

$$n := 1.5$$

$$n = 1.5$$

$$nU_T := n \cdot U_T$$

$$nU_T = 38.813 \cdot \text{mV}$$

$$C_W := 0.45 \cdot \frac{\text{fF}}{\mu\text{m}}$$

$$f_u := 10 \cdot \text{GHz}$$

$$\omega_u := 2 \cdot \pi \cdot f_u$$

$$L_{\text{min}} := 40 \cdot \text{nm}$$

$$L := L_{\text{min}}$$

$$C_{L0} := 60 \cdot \text{fF}$$

$$\omega_L := \frac{I_{\text{specsq}}}{nU_T \cdot C_{L0}}$$

$$\frac{\omega_L}{2 \cdot \pi} = 64.926 \cdot \text{MHz}$$

$$\Omega_n := \frac{\omega_u}{\omega_L}$$

$$\Omega_n = 154.021$$

$$\omega_w := \frac{I_{\text{specsq}}}{nU_T \cdot C_W \cdot L}$$

$$\frac{\omega_w}{2 \cdot \pi} = 216.421 \cdot \text{GHz}$$

$$\Theta := \frac{\omega_u}{\omega_w}$$

$$\Theta = 0.046$$

$$I_{C_{\text{op}}} := I_{C_{\text{opt}}}(\Theta)$$

$$I_{C_{\text{op}}} = 0.337$$

$$i_{\text{bop}} := i_{\text{bopt}}(\Theta)$$

$$i_{\text{bop}} = 1.532$$

$$\kappa = \frac{\omega_w}{\omega_L} = \frac{C_{L0}}{C_W \cdot L}$$

$$C_W \cdot L = 0.018 \cdot \text{fF}$$

$$\kappa := \frac{C_{L0}}{C_W \cdot L}$$

$$\kappa = 3.333 \times 10^3$$

$$\frac{\omega_w}{\omega_L} = 3.333 \times 10^3$$

$$i_{\text{bop}} := i_{\text{biasopt}}(\Theta, \kappa)$$

$$i_{\text{bop}} = 235.982$$

$$I_{\text{bias}} := I_{\text{specsq}} \cdot i_{\text{biasopt}}(\Theta, \kappa)$$

$$I_{\text{bias}} = 224.183 \cdot \mu\text{A}$$

$$W_{\text{overL}} := W_{\text{overL}_{\text{opt}}}(\Theta, \kappa)$$

$$W_{\text{overL}} = 700.52$$

$$W_{\text{opt}} := W_{\text{overL}} \cdot L$$

$$W_{\text{opt}} = 28.021 \cdot \mu\text{m}$$

$$G_{\text{m}} := \frac{I_{\text{specsq}}}{nU_{\text{T}}} \cdot W_{\text{overL}} \cdot g_{\text{ms}}(I_{\text{C}_{\text{op}}})$$

$$G_{\text{m}} = 4.562 \times 10^3 \cdot \frac{\mu\text{A}}{\text{V}}$$

$$C_{\text{Ltot}} := C_{\text{L0}} + W_{\text{opt}} \cdot C_{\text{W}}$$

$$C_{\text{Ltot}} = 72.609 \cdot \text{fF}$$

$$\frac{G_{\text{m}}}{2 \cdot \pi \cdot C_{\text{Ltot}}} = 10 \cdot \text{GHz}$$