

# Low-power radio design for the IoT

## Exercise 11 (12.05.2022)

Christian Enz

Swiss Federal Institute of Technology (EPFL), Lausanne, Switzerland

### Problem 1 Pierce Oscillator

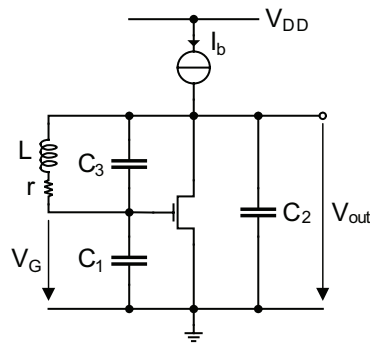


Figure 1: Pierce oscillator.

Design the Pierce oscillator shown in Fig. 1 for the following specifications:

$$f_0 = 2.4 \text{ GHz}, \quad C_2 = 1 \text{ pF}, \quad C_3 = 1 \text{ pF}, \quad Q_L = 10, \quad \mathcal{L}(\Delta\omega = 1 \text{ MHz}) = -112.37 \text{ dBc} \cdot \text{Hz}^{-1}$$

- Find the inductance value.
- Find the critical transconductance value.
- Find the critical current value assuming the transistor is biased in weak inversion (take  $n = 1.3$ ).
- Find the output oscillation amplitude  $\hat{V}_{\text{out}}$  for the given phase noise specification. Assume first that the transistor is biased in weak inversion and that the noise excess factor  $\gamma$  is equal to 1.2. Then repeat the calculus assuming that the transistor is biased in strong inversion and that the noise excess factor  $\gamma$  is equal to 0.89.
- Find the bias current  $I_b$  for the specified amplitude assuming the transistor is biased in weak inversion (take  $n = 1.3$ ).
- Find the bias current  $I_b$  for the specified amplitude assuming the transistor is biased in strong inversion with  $V_G - V_{T0} = 300 \text{ mV}$ .

## Problem 2 Complementary cross-coupled oscillator

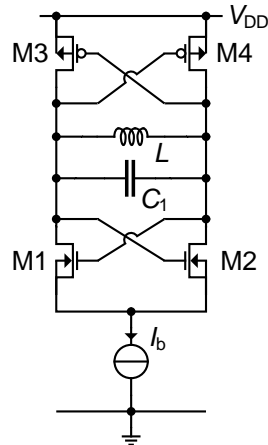


Figure 2: Complementary cross-coupled oscillator

### 2.1 Oscillator analysis

Fig. 2 shows a complementary cross-coupled oscillator. In the first part of the problem we will derive expressions for quantities that will be used in the second part. All transistors are biased in weak inversion and have transconductances equal to  $G_m$ . Quality factor of the inductor is  $Q_L$ .

- Draw the small signal equivalent circuit.
- Derive the expression for the impedance seen from the inductor  $Z_c$ , and find  $R_c = -\Re Z_c$  and  $X_c = -\Im Z_c$ .
- Derive the expression for the oscillation frequency  $\omega_0$ .
- Derive the expression for the  $G_{\text{mcrit}}$ .

### 2.2 Oscillator design

The derived expressions will now be used to design the oscillator with the following specifications:

$$f_0 = 2.4 \text{ GHz}, \quad C = 0.5 \text{ pF}, \quad Q_L = 10, \quad V_{\text{out}} = 325 \text{ mV}, \quad U_T = 25 \text{ mV}, \quad n = 1.3$$

Again, assume that all transistors are biased in weak inversion.

- Find the inductance value for the given oscillation frequency.
- Find the value of  $G_{\text{mcrit}}$ .
- Calculate the bias current needed to achieve the desired amplitude of the output voltage  $V_{\text{out}}$ . You can assume here that the condition  $V_{\text{out}} \gg 2nU_T$  is fulfilled.