

Embedded Systems

"System On Programmable Chip"

Programmable interface design

Parallel port Design

Odometry - PWM

René Beuchat

Laboratoire d'Architecture des Processeurs

rene.beuchat@epfl.ch

Design of a Parallel Port

Example of a development methodology of a programmable parallel port interface

- Processor Interface
- Processor view : registers model
- Interface design
- Realization in VHDL
- Test Bench and simulation

Goal


Programmable **Parallel Input/Output** Interfaces are very common on a SOPC.

They allow access to simple bits of information between the processor and the external world.

The control is done by the processor through registers in the programmable interface.

Each register is seen at a specific address.

Typical SOPC

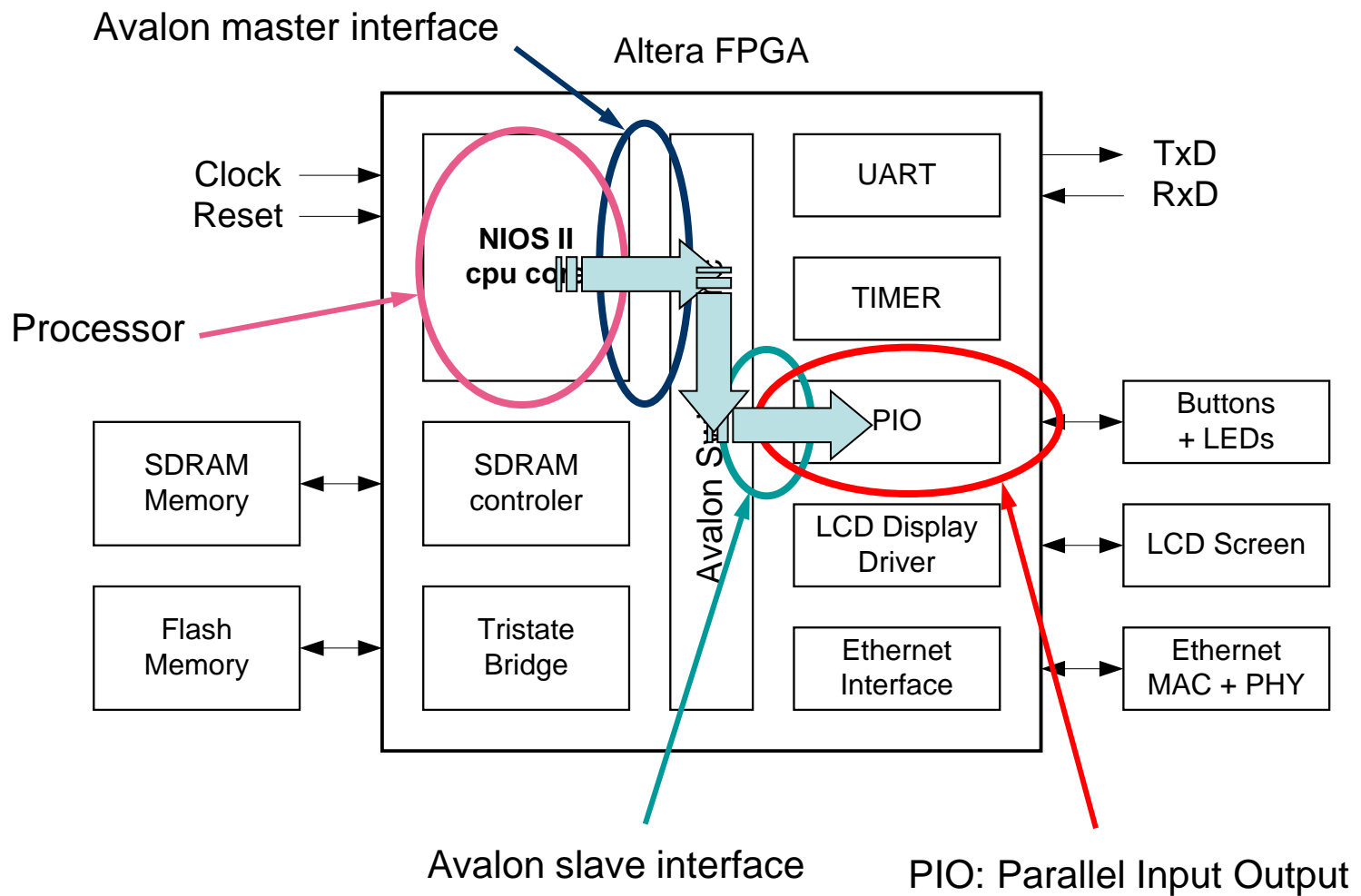

Goal

The objective here is to design one interface for an Avalon bus as a slave module.

The main characteristics of the module are:

- Bidirectional Port,
- Programmable Direction for each bit
- Special features for modifying the port bits

- Realization in VHDL for FPGA (that can be simulate **and** synthesizable)

Avalon Parallel Port, main features

- Realization of the parallel Port on Avalon Bus with:
 - 8 bits port
 - Programmable direction for each bit
 - Write direct to PortPar
 - Function Setbits
 - Function Clrbits

- We have a softcore processor on an Avalon bus in a FPGA.
- In the FPGA a specific parallel port is to be developed, it has to be added on the Avalon with SOPC Builder in the Quartus II environment.

Avalon Slave bus Cycles

- Read and Write Access
- Synchronous
- Separate data bus for read and write access

Slave Avalon Bus Specifications

The Avalon bus provide signals to the module:

- **nReset** Initialization
- **Clk** Clock
- **Address(n..0)** Address, the address is a register number address.
- **ChipSelect** Selection of this module
- **Read** Read access
- **ReadData[7..0]** Data to provide by the module in read access
- **Write** Write access
- **WriteData[7..0]** Data send to the module in write access

Parallel Port Accesses (1)

- 8 bits bidirectional Port,
 - Each pin can be specified as input or output
 - The direction is specified in **RegDir**, (0 : input, 1 : output)
 - The direction can be read back

- The state of the port at the pin level can be read in : **RegPin**


Parallel Port Accesses (2)

- The state value is memorized in a register:
RegPort → Port Register
- To update this register, 3 accesses are available :
 1. **RegPort** : Direct memorized value : '0' or '1'
 2. **RegSet** : The bits specified at '1' level during the write cycle at this address, are saved as '1' in the register, the others bits are not changed
 3. **RegClr** : The bits specified at '1' level during the write cycle at this address, are saved as '0' in the register, the others bits are not changed
- This register can be read back

Parallel Port External interface

- **ParPort** is the signal name for the pins.
- If the direction is output:
 - The value memorized in **RegPort** is Outputted.
- If the direction is input:
 - The output value is 'Z': High impedance (tri-stated)
- In both case the value at the pin interface can be read with an access at **RegPin**

Parallel Port Module on Avalon

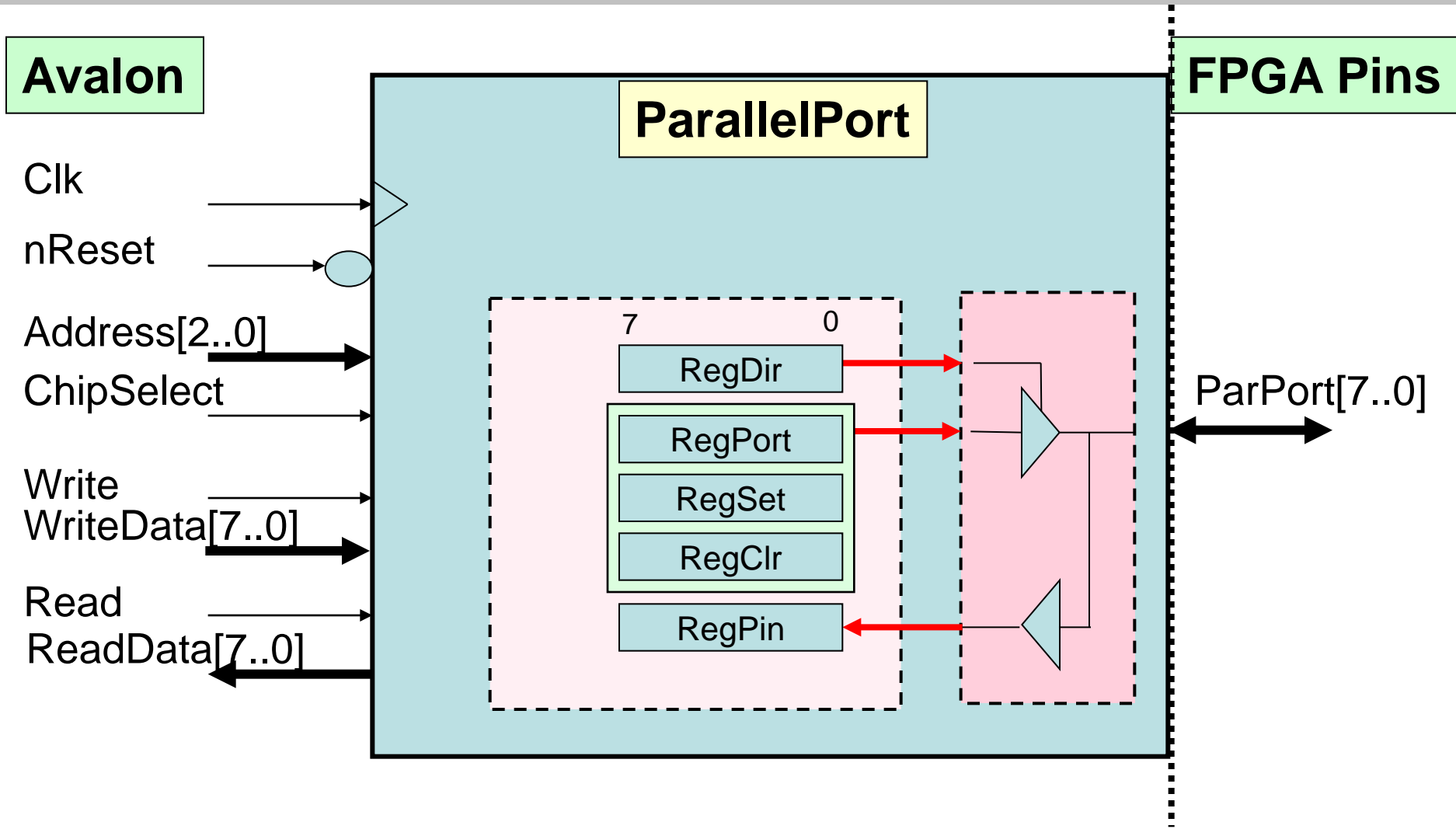

I/O Addresses in the module, access map

Adresses in the module	Write Registers	DataWrite [7..0]	Read Registers	DataRead [7..0]
0	RegDir	→ iRegDir	RegDir	iRegDir →
1	-	Don't care	RegPin	ParPort →
2	RegPort	→ iRegPort	RegPort	iRegPort →
3	RegSet	→ iRegPort	-	0x00
4	RegClr	→ iRegPort	-	0x00
5	-	Don't care	-	0x00
6	-	Don't care	-	0x00
7	-	Don't care	-	0x00

Registers selection

To do :
VHDL entity & architecture

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;
```


Entity

```
ENTITY ParallelPort IS
  PORT(
    -- Avalon interfaces signals
    Clk          : IN      std_logic;
    nReset       : IN      std_logic;

    Address      : IN      std_logic_vector (2 DOWNTO 0);
    ChipSelect   : IN      std_logic;

    Read         : IN      std_logic;
    Write        : IN      std_logic;

    ReadData     : OUT     std_logic_vector (7 DOWNTO 0);
    WriteData    : IN      std_logic_vector (7 DOWNTO 0);

    -- Parallel Port external interface
    ParPort      : INOUT   std_logic_vector (7 DOWNTO 0)
  );
End ParallelPort;
```

Architecture: Internal signals

-- signals for register access

```
signal    iRegDir  :  std_logic_vector (7 DOWNTO 0);  
signal    iRegPort:  std_logic_vector (7 DOWNTO 0);  
signal    iRegPin  :  std_logic_vector (7 DOWNTO 0);
```

ParallelPort Architecture, external interface

```


ARCHITECTURE comp OF ParallelPort IS
... SIGNAL ...
BEGIN
  -- Parallel Port output value
  pPort:
    process(iRegDir, iRegPort)
    begin
      for i in 0 to 7 loop
        if iRegDir(i) = '1' then
          ParPort(i) <= iRegPort(i);
        else
          ParPort(i) <= 'Z';
        end if;
      end loop;
    end process pPort;

  -- Parallel Port Input value
  iRegPin <= ParPort;



  -- others processes..

END comp;

```

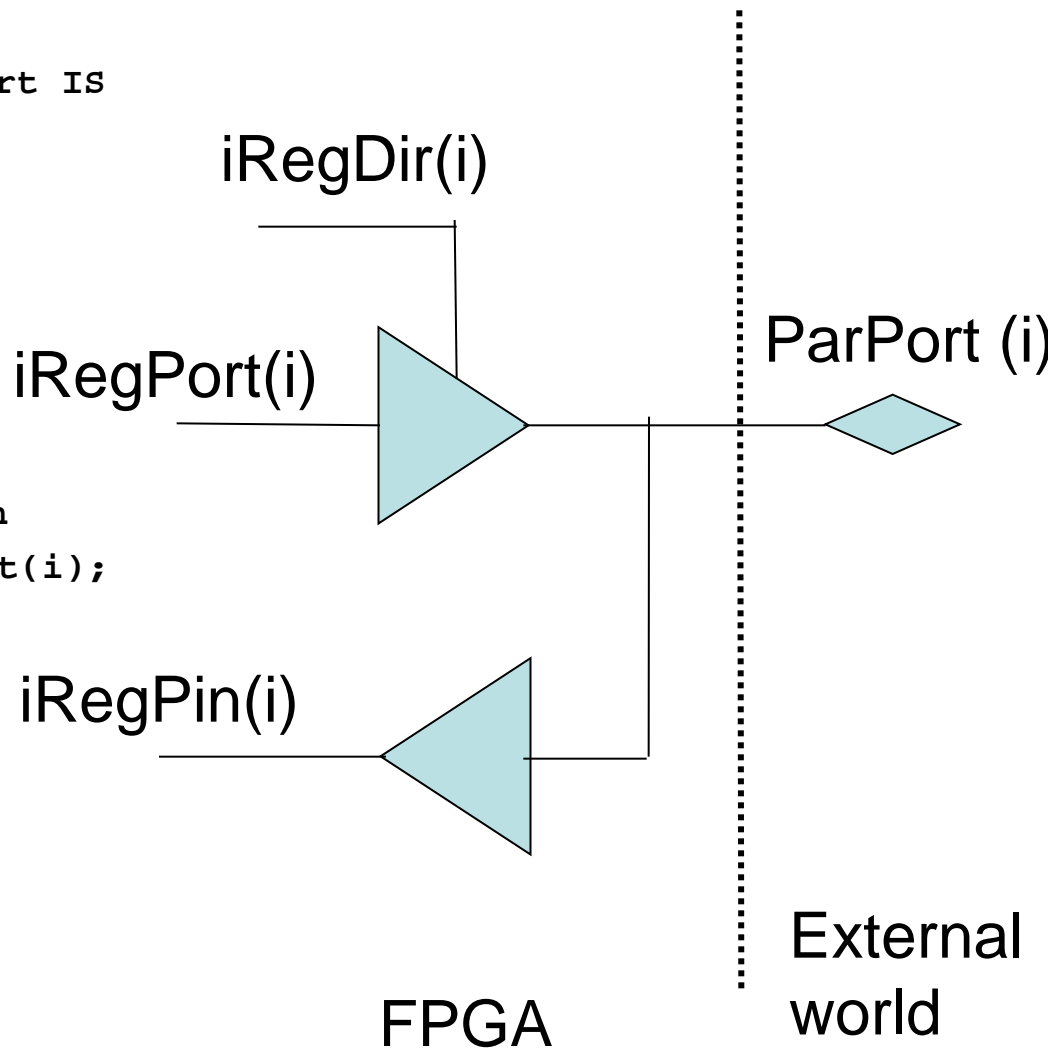

Avalon write slave, 0 wait

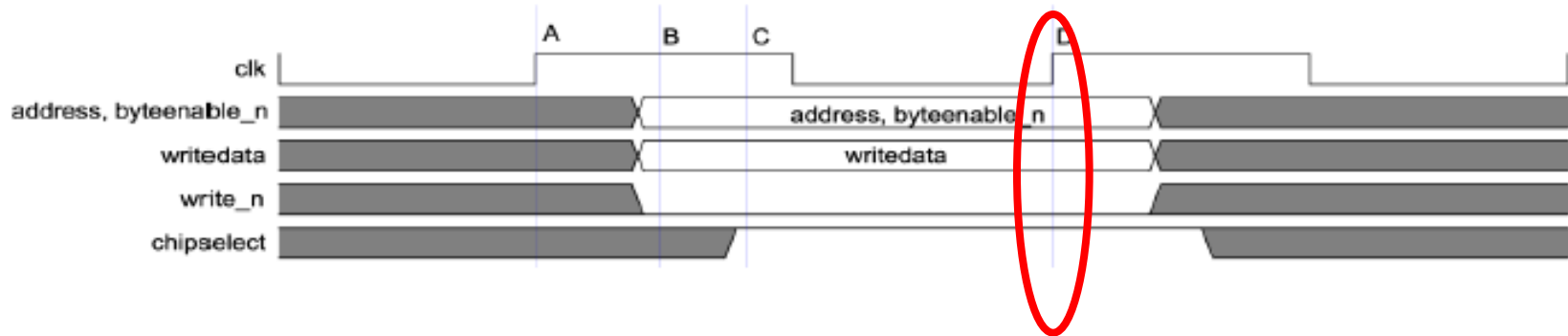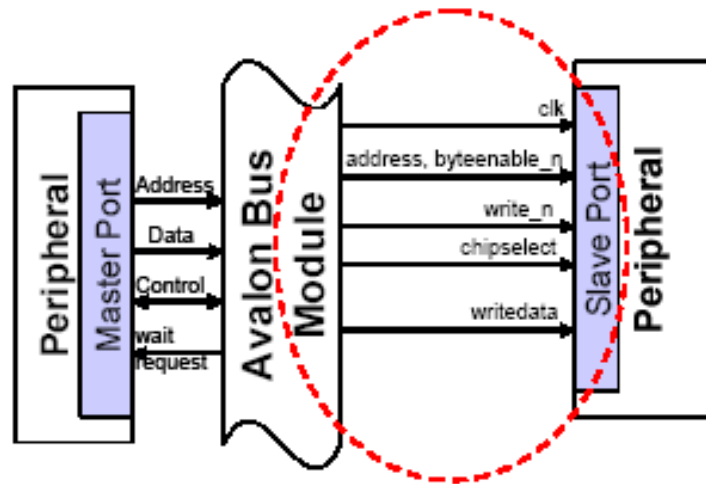

ParallelPort Architecture, registers access

-- Process Write to registers


pRegWr:

```
process(Clk, nReset)
begin
    if nReset = '0' then
        iRegDir <= (others => '0');           -- Input by default
        .....
    elsif rising_edge(Clk) then
        if ChipSelect = '1' and Write = '1' then   -- Write cycle
            case Address(2 downto 0) is
                when "000" => iRegDir <= WriteData ;
                when "010" => iRegPort <= WriteData;
                when "011" => iRegPort <= iRegPort OR WriteData;
                when "100" => iRegPort <= iRegPort AND NOT WriteData;
                when others => null;
            end case;
        end if;
    end if;
end process pRegWr;
```


Avalon slave

read, 0 wait, asynchronous peripheral

<i>This Example Demonstrates</i>	<i>Relevant PTF Parameters</i>
Read transfer from an asynchronous peripheral	Read_Wait_States = "0"
Zero wait states	Setup_Time = "0"
Zero setup	

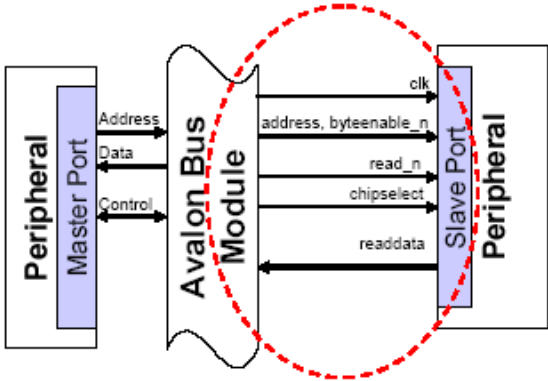

 ReadData available at next rising edge of clk (E)



ParallelPort Architecture, registers access

-- Read Process to registers

pRegRd:

```
process(Clk)
```

```
begin
```

```
  if rising_edge(Clk) then
```

```
    ReadData <= (others => '0');
```

-- default value

```
    if ChipSelect = '1' and Read = '1' then
```

-- Read cycle

```
      case Address(2 downto 0) is
```

```
        when "000" => ReadData <= iRegDir ;
```

```
        when "001" => ReadData <= iRegPin;
```

```
        when "010" => ReadData <= iRegPort;
```

```
        when others => null;
```

```
      end case;
```

```
    end if;
```

```
  end if;
```

```
end process pRegRd;
```

!! Synchronone: 1 wait

Test and implementation

- This module can be now be tested by simulation with a test bench or timing stimulation → **to do as exercise**
 - Read, Write access have to be generated to control the registers and verify the result
- Then a **new component** can be created with **SOPC Builder**
- It can then be integrated in a NIOSII system
- The system can be generated from SOPC
- Compiled by QuartusII after added to a schematic design
- Downloaded on a real system
- Program the NIOSII processor to access the registers (NIOS IDE) and test the full system

Creation in QuartusII / SOPC Builder

1. You need to create a **Project** for **each** programmable interface you developed in QuartusII
2. **Don't use space** in directory/files names
3. When you create a VHDL entity/architecture, the name of the file is the name of the **entity**
4. Entity and architecture are in the same file
5. You create a **new Project** for the full design

Conclusion

- Now you are able to design a specific programmable interface for a bus for Programmable FPGA, here it was the Avalon
- The methodology for this kind of interface is similar for Amba, Wishbone or others internal bus
- The bus generation depend on the used tools, here SOPC Builder do the job !

Conclusion


- You know:
 - The basic use of Avalon synchronous bus
 - The memory map model of a programmable interface
 - To translate this model in VHDL
 - To control pins on a FPGA ('0', '1', 'Z')
 - To implement the interface module in a complete system

Others Programmables Interfaces design exemples

- **PWM:** Pulse Width Modulation
- **Odometer:** Distance / Speed measurement


Pulse Width Modulation

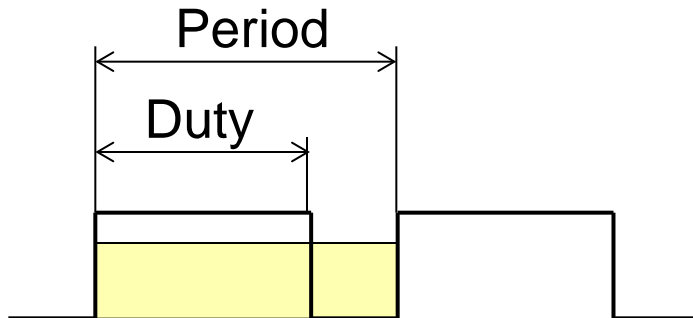- Generation of a continuous pulse train
- Can be used as a D/A converter




- To control a motor, a PWM module with 2 outputs can be used :
 - **PWMA** and **PWMb**
 - They are connected to a DC motor through a H-bridge
 - Depending which output send the PWM signal, the motor turn in one direction or the other.
 - **PWMA** ← PWM, **PWMb** ← Idle → Direction A
 - **PWMA** ← Idle, **PWMb** ← PWM → Direction B

PWM Output control

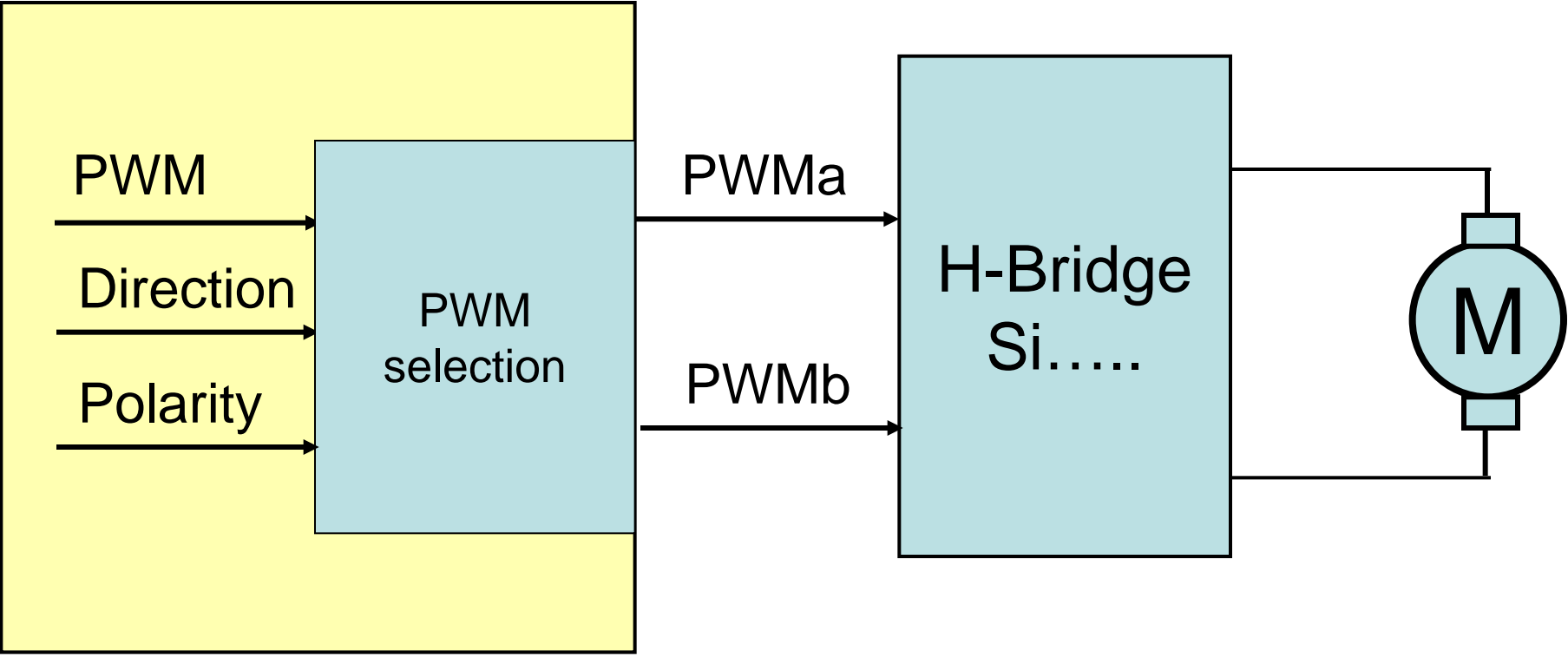

Programmable Interface ... PWM

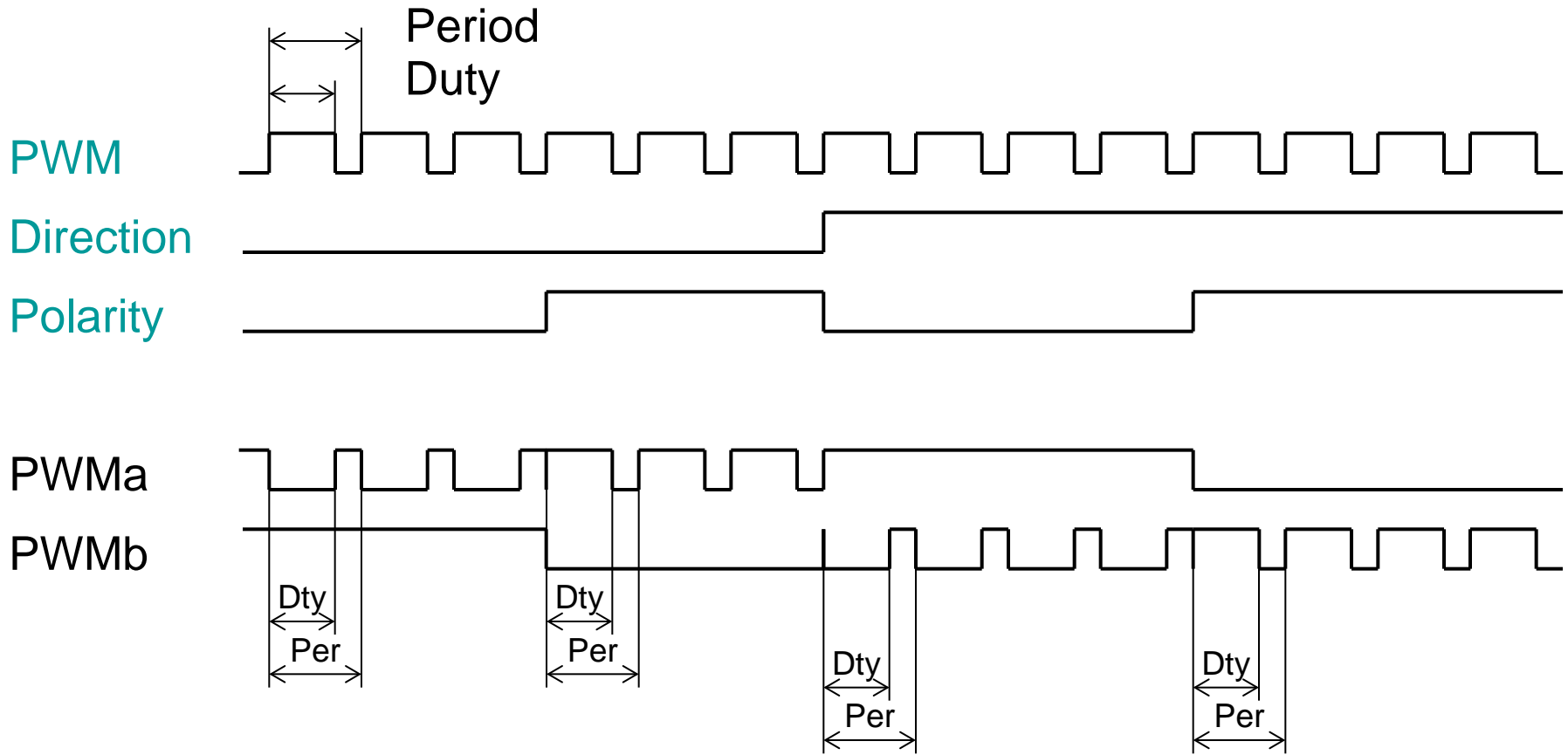

Polarity: Level of the Active part of the PWM
The Idle level is the inverted value of the Polarity



Programmable Interface ... PWM

- We want to be able to program :
 - The period of the PWM signal
 - The active Time (Duty) of the PWM
 - The polarity of the active time ('0') or ('1')
 - Be able to enable/disable the output → a **command register**
 - Direction is the sign of the Duty
 - If the Duty is positive:
 - PWMa is the PWM output, PWBb is in the Idle state
 - If the Duty is negative:
 - PWMb is the PWM output, PWBa is in the Idle state
 - Period value is on 15 bits
 - Duty is on 16 bits signed in cpl'2 → real duty is the $\text{abs}(\text{RegDuty})$
 - The new Duty is to be used only at the end of a Period if the PWM output is enabled

- Propose a register map of this interface
- Create the entity in VHDL
- Implement the Architecture
- Simulate the access
- Create a component with SOPC Builder
- Integrate it in a NIOSII system

Odometer

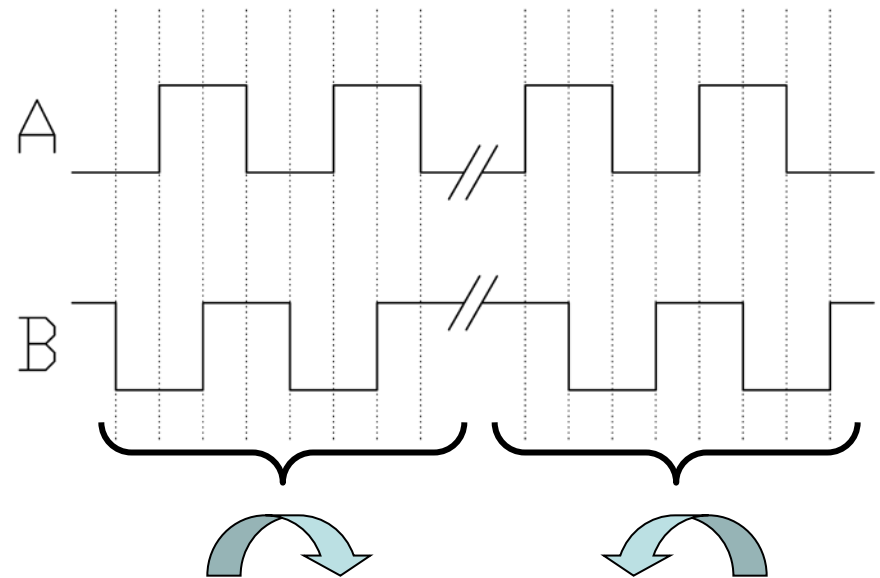 
- A 2 signals system to measure speed and displacement
- Depending on the phase of A and B the direction of the rotation can be determinate



- An odometer module based on this captor has 2 input signals used to increment/decrement a readable counter for distance measurement
- How could we measure the speed ?
 - As: ***speed = distance / time***
 - *Distance* is proportional to the number of pulses (edge)
 1. Counting the time between 2 captor pulses (i.e. 2 rising edge of A)
 2. Counting the number pulses during a fixed time

Programmable Interface ... Odometer

 - @dt a Speed counter is save in a speed register
- Speed counter is Cleared and start counting again
- Speed is proportional to the number of counted Odo pulses between dt
- dt pulses can be generated by a programmable interface



Programmable Interface ... Odometer

- Propose a register model of the programmable interface
- Imagine you have to use it as a software programmer, are you happy with your model ?
 - Yes → OK go on and implement it.
 - No → Correct it until it's a nice proposition
- Implement it in VHDL and test it with simulation

Odometer.. Sampling of input signals

- The **OdoA** and **OdoB** signals are **asynchronous** related to a Clock signal used in a FPGA or a microcontroller
- For a FPGA design, they have to be **synchronized** before use by a synchronous module inside the FPGA.
- At least 2 D Flip-Flop are needed for input synchronization

Odometer.. Sampling of input signals



- If an external asynchronous signal is used inside a synchronous system it needs to be synchronized before use
- Why ?
 1. Metastability problem
 2. At the same clk sampling time (i.e. `rising_edge(Clk)`), all the logic elements using the signal and clocking it need to see it at the same level !!

Odometer.. Sampling of input signals

Metastability problem:

To be correctly sampled by a FF a signal needs to respect 2 very important timings:

  
- ***T_{su}*: Set up time**
- ***T_{hold}*: Hold time**



Odometer.. Sampling of input signals

If the rule is NOT respected:

 
- *The output can be '0' or '1' → good*
- *The output can be in an intermediate level for an undefined time → **metastable level***



Odometer.. Sampling of input signals

- The level of the metastable signal is between the '0' and the '1'.
- The time the metastable signal stay is probabilistic and theoretically could be infinite. Practically it disappears at the next signal sampling.
- Usually a DFF sampling a metastable level would not propagate it. As for this intermediate level, a decision is taken for a '0' or a '1'.
- It could propagate to a next DFF if the level change just at the sampling point to the metastable threshold, the probability is very low but not 0 !
- Thus depending on the hardness of the design to do, more DFF are needed.

 
Manufacturer provides information about the parameters for metastability.




Odometer.. Sampling of input signals

If the rule is NOT respected:

 - *Very bad for 1 DFF → worst if the same signal D is going to more than 1 DFF:*
- *each could see a different input level*




Qa, Qb :
2 DFF output

 

Odometer.. Sampling of input signals


→ At the same clk sampling time (i.e. rising_edge), all the logics using the signal and clocking it need to see it at the same level !!

→ A synchronizing system is necessary

 


Odometer.. Sampling of input signals

 - The first DFF can have a metastable signal as output Q_m
- The second one will **probably** filter it
- For very high reliability system more DFF could be necessary, delay added !!



Odometer.. Sampling of input signals

 → The Qsn signal can be used by all the logic that need it: the level will be the same for all the logic




Odometer.. Sampling of input signals

- Inside the FPGA all the DFF using the same D signal need to use the same Clock.
- Special global lines are available inside a FPGA for that purpose.
- They are limited in number
- If we expect to use a normal signal as a clock for a FF → it's a very bad idea
- We need to use the **Clock Enable** feature of a DFF in a FPGA

Odometer.. Sampling of input signals

 
→ The clock is used only if the CE line is activated ('1')



Odometer.. Sampling of input signals

- What about the Odo Input ?
- We need to detect a rising and falling edge of OdoA and OdoB
- Synchronization followed by logic for edge detection

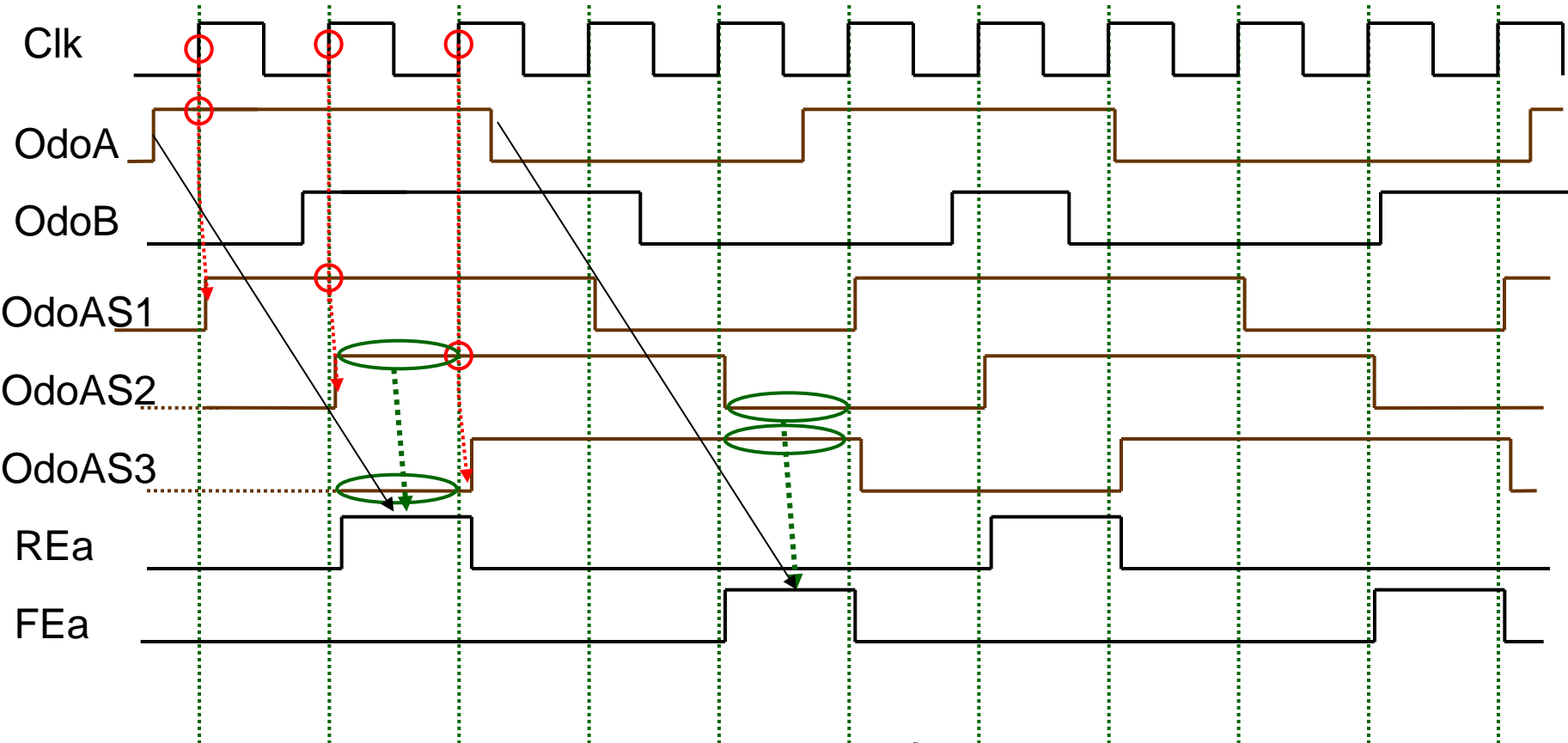
Odometer.. Edge detection of input signals




REa: Rising edge detection on a
FEa: Falling edge detection on a

They can be used
sampled by the Clk

 
Odometer.. Edge detection of input signals




Odometer.. Edge detection A and B

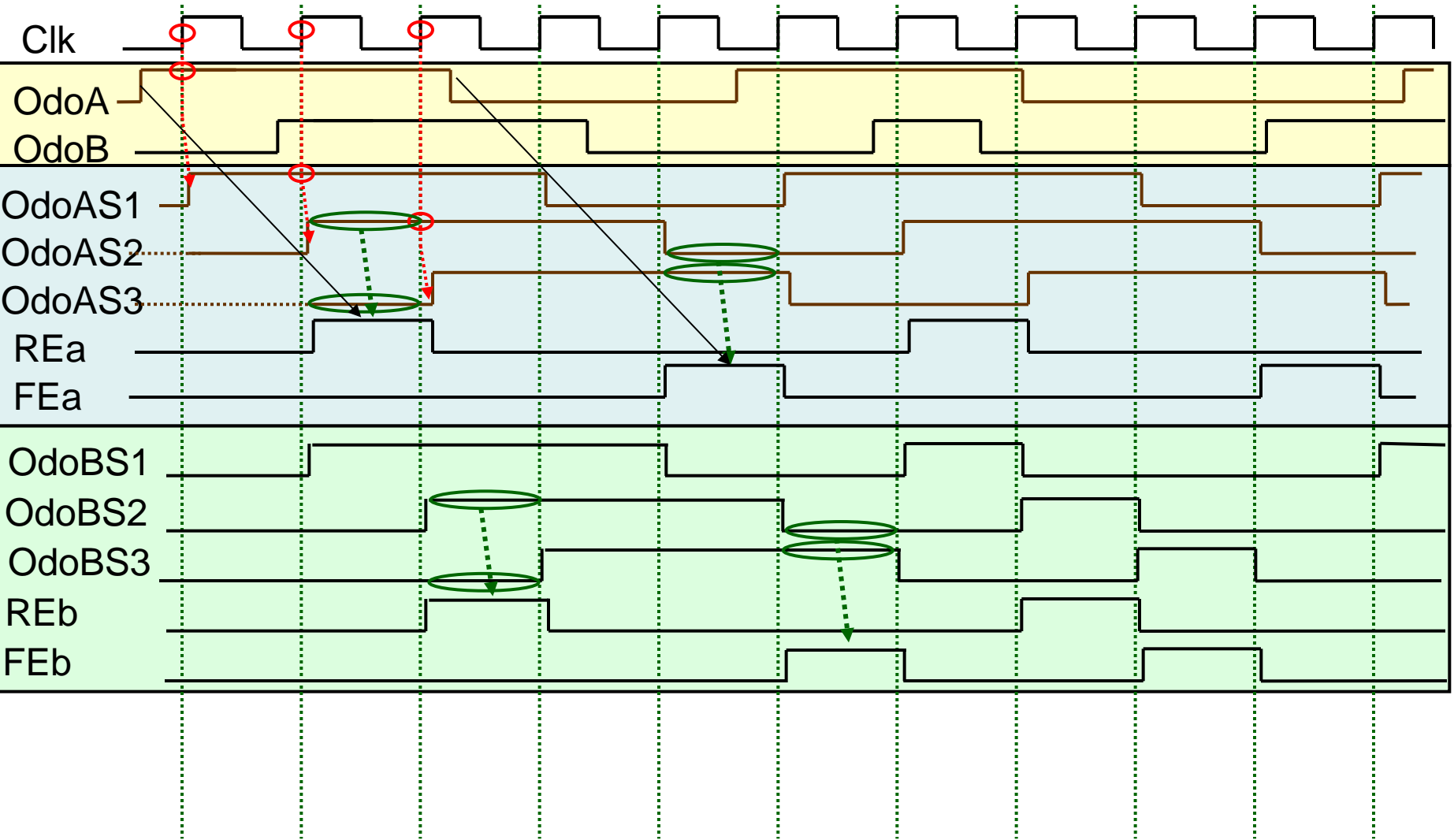

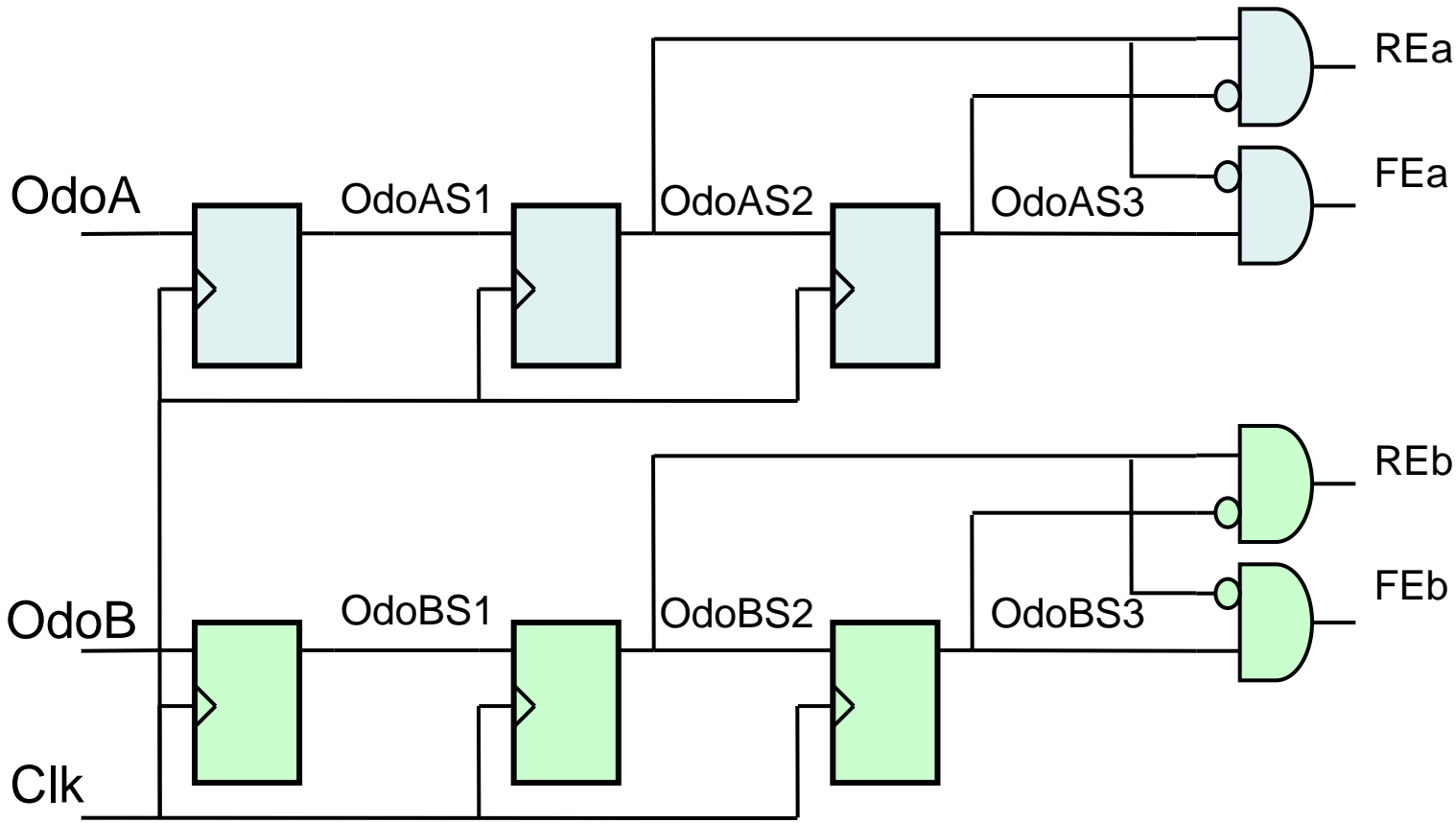
Odometer.. Edge detection of input signals



Odometer.. Edge detection to Counter

 

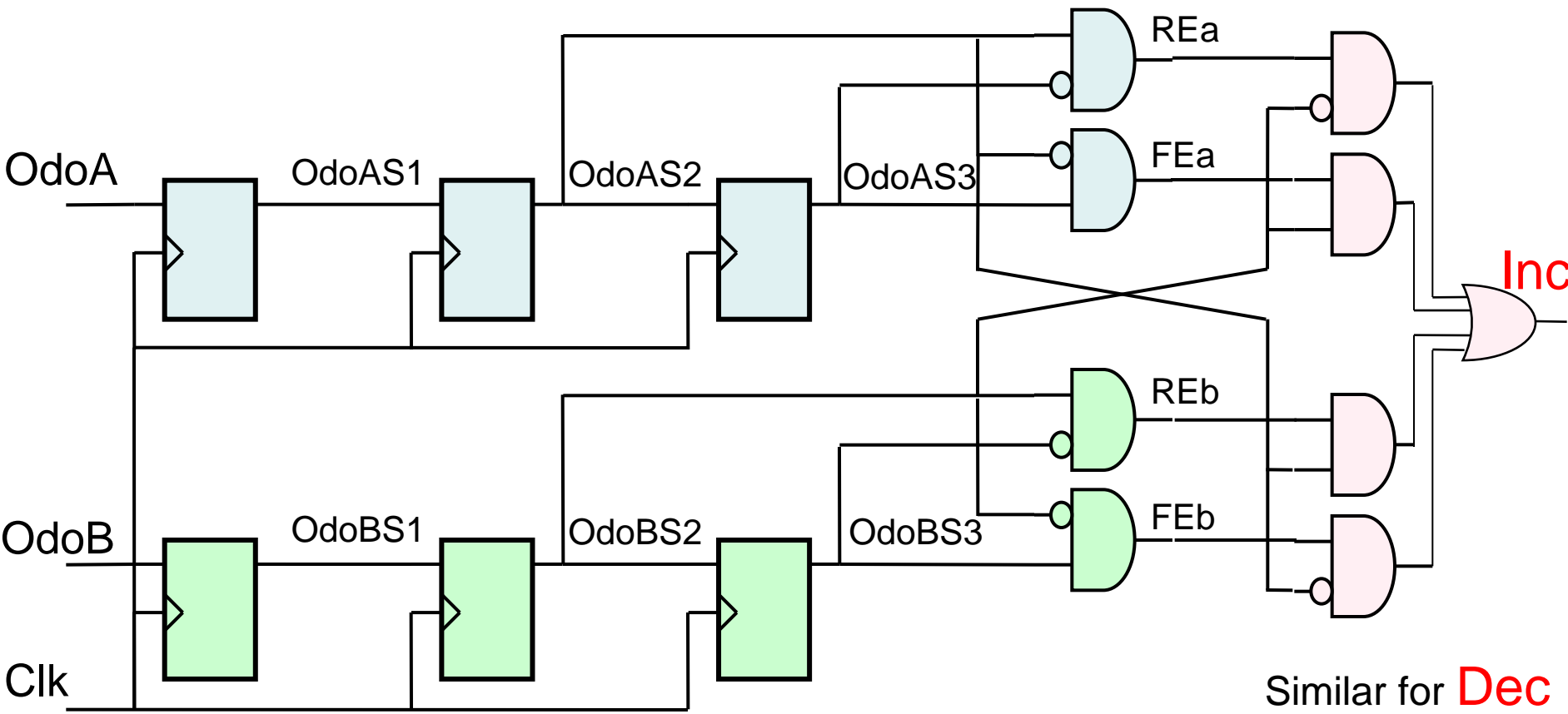Odometer.. Edge detection .. Inc/Dec generation



Odometer.. Sampling of input signals

- Now you can find how to use that to increment/decrement a counter for distance measurement
- And translate in VHDL!!

- Good work !