

# Real Time Embedded Systems

## **"System On Programmable Chip"**

Programmable interface design

## **Specific Counter Design**

René Beuchat

Laboratoire d'Architecture des Processeurs

*rene.beuchat@epfl.ch*

# NIOS II – A specific Avalon Peripherals Counter as exercise

- We want to realize a specific counter with few features only:
  - Reset by command
  - Count on 32 bits
  - Start and stop counting by command
  
  - For an Avalon bus slave interface
  - This simple design could be used as starting point for more complex timer units

# NIOS II – A specific Avalon Peripherals Counter as exercise

- 32 bits counter
- Avalon Bus Slave Interface, 32 bits data
- Command, 3 separate Write access:
  - RzCount
  - StartCounter
  - StopCounter
- Read Counter Value on 32 bits
- Status:
  - Run
- Interrupt (option)
  - Enable Interrupt: Command
  - EOT (EndOfTime (Counter→0)): Status
  - ClearEOT: Status

# NIOS II – A specific Avalon Peripherals Counter as exercise

- **Command**, don't care of data  
just use the Write address :
  - RzCount
  - StartCounter
  - StopCounter
- **Command** register
  - Enable Interrupt Command, 1 bit
- **Status:**
  - Run
  - EOT (EndOfTime (Counter→0)): Status
  - To Clear EOT, write a '1' to Status bit EOT

# NIOS II – A specific Avalon Peripherals

## Counter as exercise

- Address mapping:

Internal Reg. Add	Name	R/W	Size	Function
0	Counter	R	32	Counter value
1	Rz	W	0	Reset Counter
2	Start	W	0	Start Counting
3	Stop	W	0	Stop Counting
4	Command	W/R	8	General Command
5	Status	W/R	8	General Status

# NIOS II – A specific Avalon Peripherals

## Counter as exercise

- Command register:

Command	7	6	5	4	3	2	1	0
Functions	-	-	-	-	-	-	-	<b>IRQEn</b>
@Reset	0	0	0	0	0	0	0	0

- Status register:

Status	7	6	5	4	3	2	1	0
Functions R W	-	-	-	-	-	-	Run	<b>EOT ClrEOT</b>
@Reset	0	0	0	0	0	0	0	0


# NIOS II – A specific Avalon Peripherals Counter as exercise

- More details on Avalon Bus Module:
  - Slave
  - 32 bits counter
  - Read and write Access on 32 bits bus
  - **0 wait Write** access
  - **1 wait Read** access
  - Synchronous to **Clk**
  - **Reset\_n** to initialize the module
  - **IRQ** for interrupt Request

# NIOS II – A specific Avalon Peripherals

## Counter as exercise


### Bloc diagram of the interface

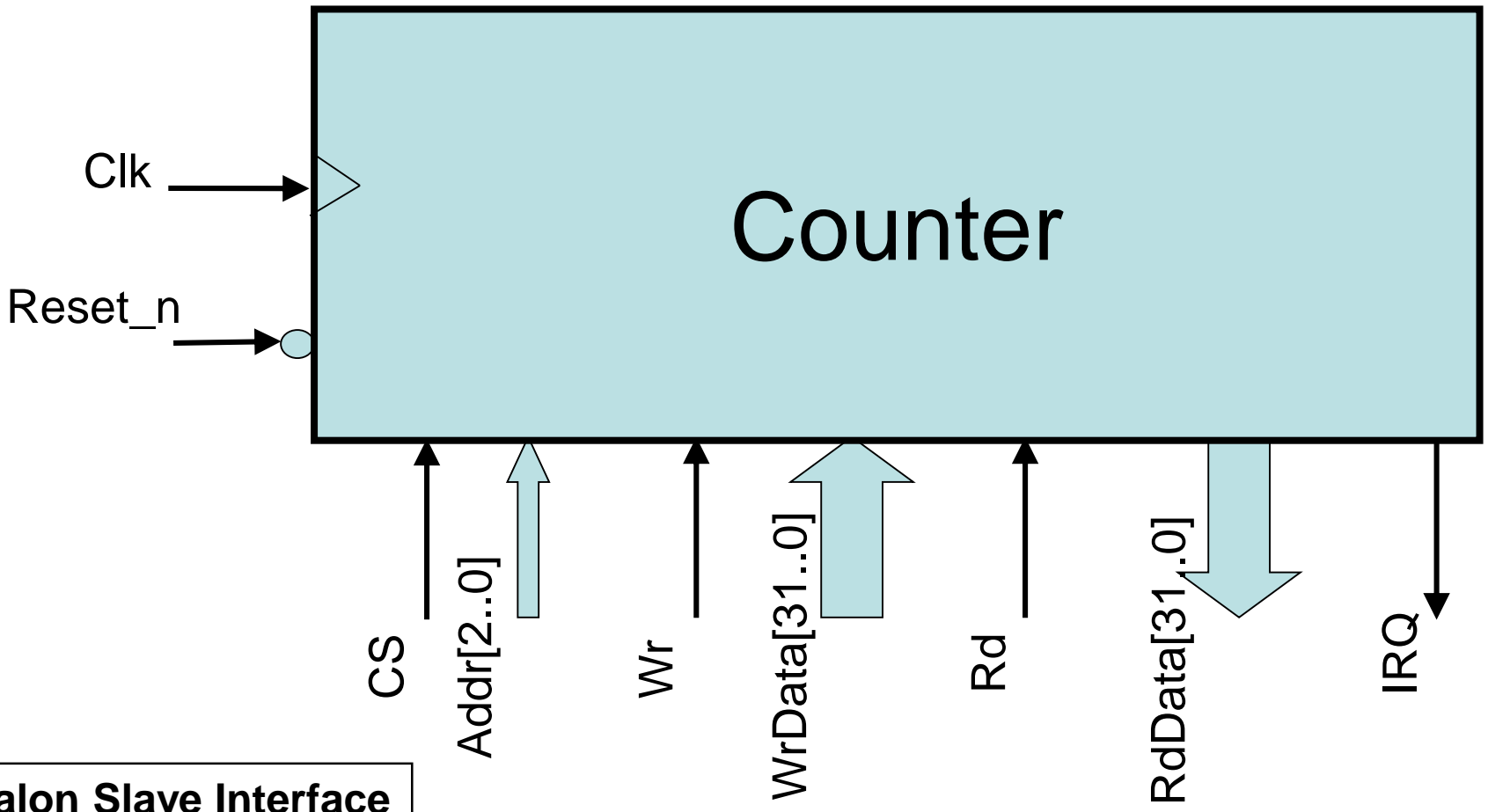




# NIOS II – A specific Avalon Peripherals
 
## Counter as exercise: Base, a 32 bits counter




# NIOS II – A specific Avalon Peripherals
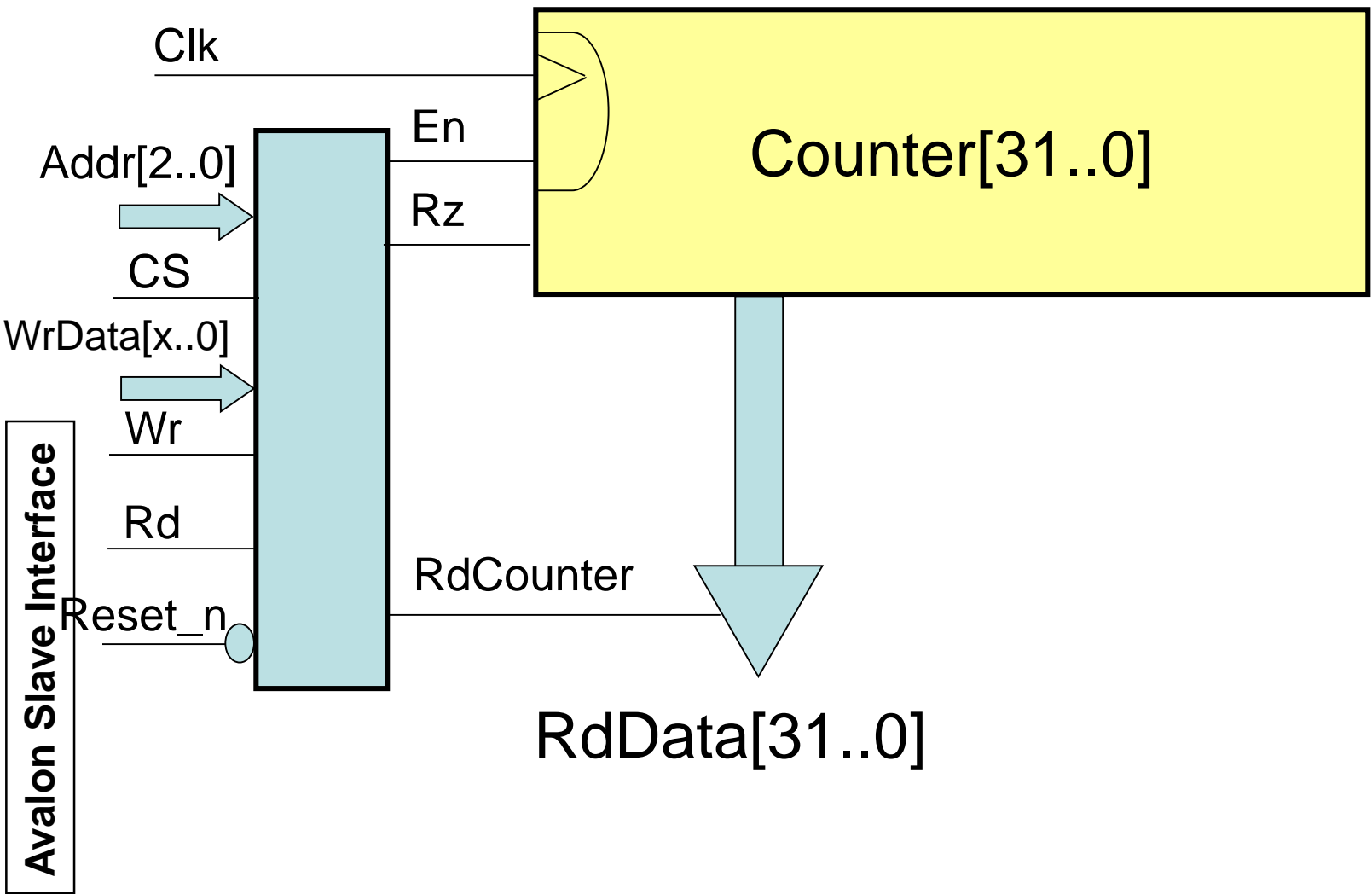
## Counter as exercise: Avalon interface for Read and basic commands



# NIOS II – A specific Avalon Peripherals

## Counter as exercise: IRQ complement

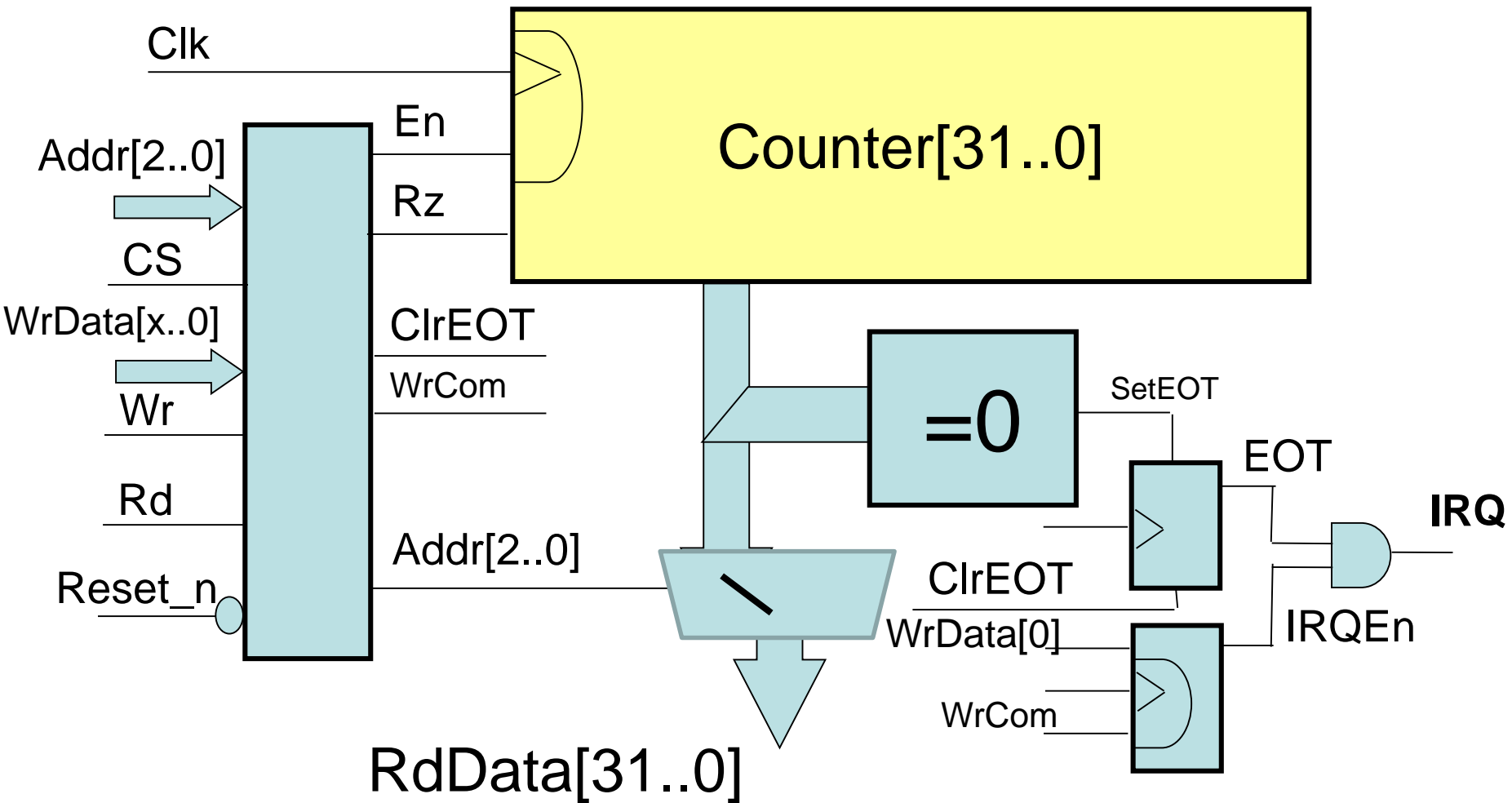

Note: Read Status not represented

# NIOS II – A specific Avalon Peripherals

## Counter as exercise: Library

```
library ieee;  
use ieee.std_logic_1164.all;  
    use ieee.numeric_std.all;
```

Or ~~(but obsolete !!!)~~

```
    use ieee.std_logic_arith.all;  
    use ieee.std_logic_unsigned.all;
```

# NIOS II – A specific Avalon Peripherals

## Counter as exercise: Entity

```
ENTITY Counter IS
  PORT (
    -- Avalon interfaces signals
    Clk          : IN      std_logic;
    nReset       : IN      std_logic;

    Address      : IN      std_logic_vector (2 DOWNTO 0);
    ChipSelect   : IN      std_logic;

    Read         : IN      std_logic;
    Write        : IN      std_logic;

    ReadData     : OUT     std_logic_vector (31 DOWNTO 0);
    WriteData    : IN      std_logic_vector (31 DOWNTO 0);

    -- Interruptions
    IRQ          : OUT     std_logic
  );
End Counter;
```

# NIOS II – A specific Avalon Peripherals

## Counter as exercise: Architecture: Internal signals

-- signals for register access

```
iCounter    : unsigned(31 DOWNT0 0) ;
```

```
iEn         : std_logic;
```

```
iRz         : std_logic;
```

```
iEOT        : std_logic;
```

```
iClrEOT     : std_logic;
```

```
iIRQEn     : std_logic;
```

# NIOS II – A specific Avalon Peripherals

## Counter as exercise: Counter Architecture, Counter

```
ARCHITECTURE comp OF Counter IS
... SIGNAL ...
BEGIN
  -- Counter process, synchronous Reset by command and count if
  -- enabled
  pCounter:
    process(Clk)
    begin
      if rising_edge(Clk) then
        if iRz= '1' then
          iCounter <= (others => '0');      -- Reset Counter → 0
        elsif iEn = '1' then
          iCounter <= iCounter+1;        -- increment
        end if;
      end if;
    end process pCounter;
END comp;
```

# NIOS II – A specific Avalon Peripherals

## Counter as exercise: Counter Architecture, registers access

```
pRegWr:                                     -- Process Write to registers
process(Clk, nReset)
begin
  if nReset = '0' then                     -- asynchronous Reset
    iEn <= '0';                             -- No Count by default
    iRz <= '0';
    iIRQEn <= '0';                          -- No IRQ Enable by default
  elsif rising_edge(Clk) then
    iRz <= '0';                             -- No Reset, as it's just a command
    iClrEOT <= '0' ;
    if ChipSelect = '1' and Write = '1' then -- Write cycle
      case Address(2 downto 0) is
        when "000" => null ;
        when "001" => iRz <= '1';           -- Reset Counter (pulse)
        when "010" => iEn <= '1';           -- Start Run
        when "011" => iEn <= '0';           -- Stop Run
        when "100" => iIRQEn <= WriteData(0);
        when "101" => iClrEOT <= WriteData(0);
        when others => null;
      end case;
    end if;
  end if;
end process pRegWr;
```



# NIOS II – A specific Avalon Peripherals

## Counter as exercise: Counter Architecture, registers access

```
-- Read registers Process need 1 WaitCycle on Avalon
```

```
pRegRd:
```

```
  process (Clk)
```

```
  begin
```

```
    if rising_edge(Clk) then
```

```
      ReadData <= (others => '0');           -- default value
```

```
      if ChipSelect = '1' and Read = '1' then -- Read cycle
```

```
        case Address(2 downto 0) is
```

```
          when "000" => ReadData <= std_logic_vector(iCounter);
```

```
                                -- cast and Read Counter
```

```
          when "100" => ReadData(0) <= iIRQEn;
```

```
          when "101" => ReadData(0) <= iEOT;           -- EOT
```

```
                      ReadData(1) <= iEn; -- Run
```

```
          when others => null;
```

```
        end case;
```

```
      end if;
```

```
    end if;
```

```
  end process pRegRd;
```

# NIOS II – A specific Avalon Peripherals

## Counter as exercise: Counter Architecture, Interrupt

```
-- Interrupt Process , End Of Time activated when counter is @0, reste by a
  command from pRegWr
pInterrupt:
  process(Clk)
  begin
    if rising_edge(Clk) then
      If iCounter = X"0000_0000" then
        iEOT <= '1';          -- Flag End Of Time → '1' when counter =0
      Elsif iClrEOT = '1' then
        iEOT <= '0';          -- Cleared on access by WrStatus(0)
      End if;
    end if;
  end process pInterrupt;

-- IRQ activation
IRQ <= '1' when iEOT ='1' and iIRQEn = '1' and iEn = '1' else
  '0';
```

## NIOS II – A specific Avalon Peripherals Counter as exercise

- From this description and code, it is very easy to add others features as:
- Output Compare function
- Interrupt at specific time
- Reload counter
- Etc...