

---

Exercise Set 2 : Solution  
Quantum Computation

---

**Exercise 1** *Matrix representation of a few gates / circuits*

- (a) The Hilbert space here is  $\mathbb{C}^8$  and its matrix representation in the computational basis  $\{|000\rangle, |001\rangle, |010\rangle, |011\rangle, |100\rangle, |101\rangle, |110\rangle, |111\rangle\}$  is given by

$$CCNOT = \begin{pmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \end{pmatrix}$$

- (b) The matrix representation of this circuit in the computational basis  $\{|00\rangle, |01\rangle, |10\rangle, |11\rangle\}$  of  $\mathbb{C}^4$  is given by

$$NOT_y = \begin{pmatrix} 0 & 1 & 0 & 0 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{pmatrix}$$

- (c) The matrix representation of this circuit (in the same basis) is given by

$$NOT_x = \begin{pmatrix} 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \end{pmatrix}$$


- (d) The matrix representation of this circuit (in the same basis) is given by

$$NOT_x \cdot CCNOT \cdot NOT_x = \begin{pmatrix} 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \end{pmatrix} \cdot \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{pmatrix} \cdot \begin{pmatrix} 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \end{pmatrix} = \begin{pmatrix} 0 & 1 & 0 & 0 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{pmatrix}$$


All the above matrices are permutation matrices, and are also equal to their own inverse.

**Exercise 2** *Fredkin gate*

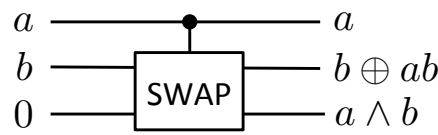
- (a) The AND gate can be represented as follows with only the Fredkin gate :



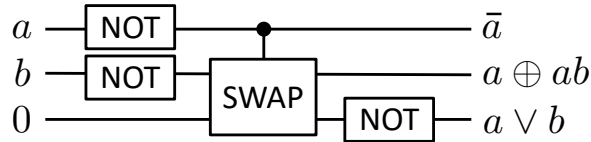
The OR gate is then (using  $a \vee b = \text{NOT}(\text{NOT}(a) \wedge \text{NOT}(b))$ )



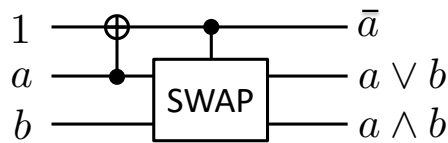Another solution for both AND and OR uses a combination of CSWAP and CNOT :



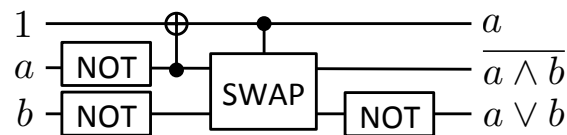
For the OR gate, alternatively, we then have :



- (b) The Fredkin is a controlled SWAP which swap's the last two bits if the first one is equal to 1. Thus we find

$$\text{CSWAP} = \begin{pmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{pmatrix}.$$

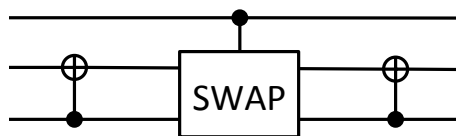- (c) From the matrix representation of Fredkin, we see that to obtain the matrix representation of CCNOT, we have to permute on rows 5,6,7,8. With a bit of thought one can find that the CCNOT gate can be represented as



Another way is by noting that

$$\begin{aligned}\text{CNOT}|x, y\rangle &= |x, x \oplus y\rangle, \\ \text{CCNOT}|x, y, z\rangle &= |x, y, z \oplus xy\rangle, \\ \text{CSWAP}|x, y, z\rangle &= |x, y \oplus x(y \oplus z), z \oplus x(y \oplus z)\rangle.\end{aligned}$$

Thus an input  $|x, y, z\rangle$  becomes  $|x, y \oplus z, z\rangle$  after the first CNOT gate,  $|x, y \oplus z \oplus xy, z \oplus xy\rangle$  after the Fredkin gate and  $|x, y, z \oplus xy\rangle$  after the second CNOT gate.

### Exercise 3 Mach-Zehnder interferometer

- (a) A matrix  $U$  is unitary if  $UU^\dagger = U^\dagger U = I$ . Note that for Hadamard and NOT(X) gates, we have  $HH^\dagger = H^\dagger H = I$ ,  $XX^\dagger = X^\dagger X = I$ . For  $HXH$ , we have

$$HXH(HXH)^\dagger = HXH H^\dagger X^\dagger H^\dagger = HXX^\dagger H^\dagger = HH^\dagger = I$$

With similar computations,  $(HXH)^\dagger HXH = I$ . Thus  $HXH$  is unitary.

- (b) We obtain successively for  $|\varphi\rangle = \alpha_0 |0\rangle + \alpha_1 |1\rangle$  :

$$\begin{aligned}H|\varphi\rangle &= \frac{\alpha_0 + \alpha_1}{\sqrt{2}} |0\rangle + \frac{\alpha_0 - \alpha_1}{\sqrt{2}} |1\rangle \\ XH|\varphi\rangle &= \frac{\alpha_0 + \alpha_1}{\sqrt{2}} |1\rangle + \frac{\alpha_0 - \alpha_1}{\sqrt{2}} |0\rangle \\ HXH|\varphi\rangle &= \frac{\alpha_0 + \alpha_1}{\sqrt{2}} \frac{|0\rangle - |1\rangle}{\sqrt{2}} + \frac{\alpha_0 - \alpha_1}{\sqrt{2}} \frac{|0\rangle + |1\rangle}{\sqrt{2}} = \alpha_0 |0\rangle - \alpha_1 |1\rangle\end{aligned}$$

- (c) The above gives

$$HXH|0\rangle = |0\rangle \quad HXH|1\rangle = -|1\rangle \quad HXH|+\rangle = |-\rangle \quad HXH|-\rangle = |+\rangle$$

### Exercise 4 Production of Bell states

- (a) State (i) is a Bell entangled state (see below).  
 State (ii) is a product state  $= |0\rangle \otimes \frac{1}{\sqrt{2}} (|0\rangle + |1\rangle)$ .  
 State (iii) is an entangled state (cannot be written as  $(\alpha_0 |0\rangle + \alpha_1 |1\rangle) \otimes (\beta_0 |0\rangle + \beta_1 |1\rangle)$ ).  
 State (iv) is a product state  $= \frac{1}{\sqrt{2}} (|0\rangle - |1\rangle) \otimes \frac{1}{\sqrt{2}} (|0\rangle - |1\rangle)$ .  
 State (v) is also a product state  $= \frac{1}{\sqrt{2}} (|0\rangle - |1\rangle) \otimes \frac{1}{\sqrt{2}} (|0\rangle + |1\rangle)$ .

*NB* : An easy criterion for deciding when state

$$|\psi\rangle = \alpha_{00} |00\rangle + \alpha_{01} |01\rangle + \alpha_{10} |10\rangle + \alpha_{11} |11\rangle$$

is a product state is  $\det \begin{pmatrix} \alpha_{00} & \alpha_{01} \\ \alpha_{10} & \alpha_{11} \end{pmatrix} = 0$ .


(b) A direct computation gives

$$\begin{aligned}
(CNOT)(H \otimes I) |x\rangle \otimes |y\rangle &= (CNOT)H |x\rangle \otimes |y\rangle \\
&= (CNOT) \frac{1}{\sqrt{2}} (|0\rangle + (-1)^x |1\rangle) \otimes |y\rangle \\
&= \frac{1}{\sqrt{2}} CNOT |0, y\rangle + \frac{(-1)^x}{\sqrt{2}} CNOT |1, y\rangle \\
&= \frac{1}{\sqrt{2}} |0, y\rangle + \frac{(-1)^x}{\sqrt{2}} |1, \bar{y}\rangle
\end{aligned}$$

More explicitly, we enumerate all the cases :

$$\begin{aligned}
(CNOT)(H \otimes I) |00\rangle &= (CNOT) \frac{1}{\sqrt{2}} (|00\rangle + |10\rangle) = \frac{1}{\sqrt{2}} (|00\rangle + |11\rangle) = |B_{00}\rangle \\
(CNOT)(H \otimes I) |01\rangle &= (CNOT) \frac{1}{\sqrt{2}} (|01\rangle + |11\rangle) = \frac{1}{\sqrt{2}} (|01\rangle + |10\rangle) = |B_{01}\rangle \\
(CNOT)(H \otimes I) |10\rangle &= (CNOT) \frac{1}{\sqrt{2}} (|00\rangle - |10\rangle) = \frac{1}{\sqrt{2}} (|00\rangle - |11\rangle) = |B_{10}\rangle \\
(CNOT)(H \otimes I) |11\rangle &= (CNOT) \frac{1}{\sqrt{2}} (|00\rangle - |11\rangle) = \frac{1}{\sqrt{2}} (|01\rangle - |10\rangle) = |B_{11}\rangle
\end{aligned}$$

(c) The circuit corresponding to  $|B_{xy}\rangle = (CNOT)(H \otimes I)|x\rangle \otimes |y\rangle$  :

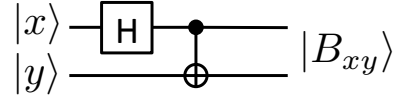

(d) The circuit corresponding to  $|x\rangle \otimes |y\rangle = (H \otimes I)(CNOT)|B_{xy}\rangle$  :

